

Definitions:-

Electrical circuit :- It is a closed path of wires and electrical components which allows a current through it.

Circuit Diagram :- It is a graphical representation of an electric circuit, It shows the components and interconnections of the circuit using symbols.

Resistance :- (R)
Resistance is the measure of the opposition to the current flow. in an electrical circuit
It is represented by the letter 'R'
Unit of Resistance = Ω (ohms)

Resistor :-

Component that offer Resistance.

Conductance : (G)

Conductance is the reciprocal of resistance

$$G = \frac{1}{R}$$

Unit of Conductance is -S (mho)

Unit is Volts (V)

Voltage(V) voltage is the difference in electric potential between two points, that pushes charge

electrons (current) through a conducting loop.

Unit is Amperes (A)

Current(I) Current is the rate of flow of electric charge

Unit is Coulombs (C)

Current is represented by the letter 'I'.

Coulomb is the unit of electric charge.

CHENNAI INSTITUTE OF TECHNOLOGY

Symbols

Resistance/Resistor:-



unit ohms.


Ammeter:-

- * Ammeter is used to measure current
- * It should be connected in series



Voltmeter:-

DC voltage source:-

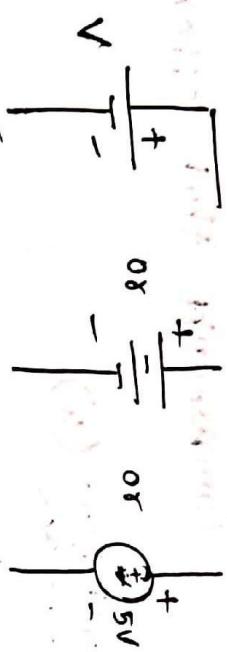

- * Voltmeter is used to measure voltage
- or potential difference between two points



Connection cable:-




Variable Resistor:-

value of the resistor is variable in such kind of resistors.



Basic Components of Electric Circuits:-

- * Branch.
- * Nodes.
- * Loops.

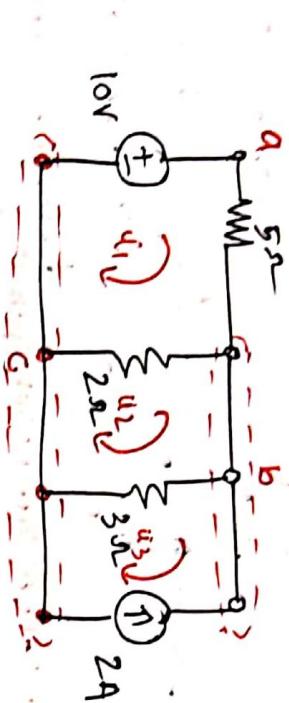

Branches:-

A branch represent a single element such as a voltage source or a resistor.

In the above circuit, 10V - voltage source, 2A - current source, 5Ω , 2Ω , 3Ω Resistors are the branches.

Node:

A Node is a point of connection between two or more branches.

Point a, b, c are nodes of the circuit.


Loop

A loop is a closed path formed by starting at a node, passing through the other nodes and returning to the starting node.

abca \rightarrow forms first loop.

bcb \rightarrow forms second loop / third loop.

e.g:

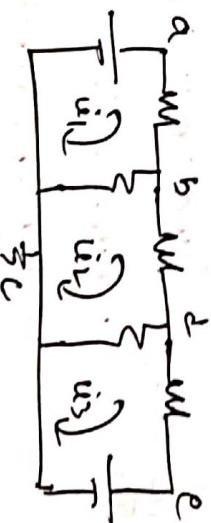


abca \rightarrow 1st loop

bcb \rightarrow 2nd loop

dcda \rightarrow 3rd loop

$u_1, u_2, u_3 \Rightarrow$ are cancel as loop currents.

Series & Parallel Circuits :-

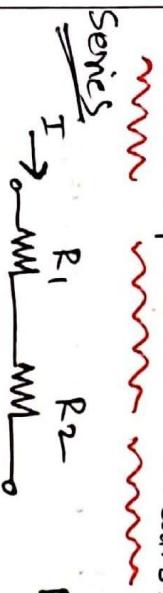

$$R_{eq} = R_1 + R_2$$

Total Resistance or equivalent resistance is the sum of the two resistors or 'n' resistors.

$$R_{eq} = R_1 + R_2 + \dots + R_n$$

for 'n' resistors
connected in series.

e.g.




Same 5A is flowing

in both 10 ohms & 20 ohms

So they are connected in series.

Parallel circuit / shunt circuit.

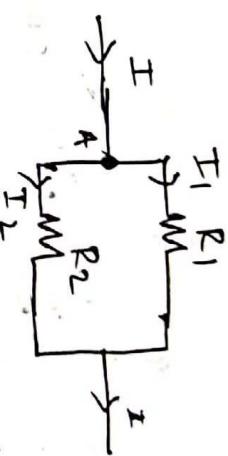

(at point 'A' current gets splitted)
(I2 in R2) are flowing

$$R_{eq} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Resistors R1 & R2 are said to be connected in parallel, because different currents (I1, I2, I3, ... in parallel) are flowing.



$$R_{eq} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$



e.g:-



In this circuit total current enters is 10A, it is splitted

& 7A enters 10 ohm & 3A enters 20 ohm, so, 10 ohm & 20 ohm are in parallel

Ohm's law:-

Ohm's law states that at constant temperature the voltage across a conductor is directly proportional to the current flowing through it.

$$V \propto I$$

$$\boxed{V = IR}$$

V = Voltage

$$\boxed{V = IR} \text{ in volts}$$

I = Current

$$\boxed{I = V/R} \text{ in amp}$$

R = Resistance

$$\boxed{R = V/I} \text{ in ohms.}$$

Problem:-


- ① An electric iron draws 2A at 10V, find its resistance from ohm's law

$$\boxed{R = \frac{V}{I} = \frac{10}{2} = 5\Omega}$$

From ohm's law

$$\boxed{Power (P) = V \times I = 30 \times (6 \times 10^{-3})}$$

$$\boxed{P = 180 \text{ mW}}$$

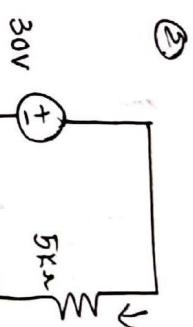

In the circuit shown, calculate the current 'i', conductance 'G' and Power 'P'.

Solution:-

$$\text{Current } i = V/R$$

$$= \frac{30}{5 \times 10^3} \rightarrow (5\Omega = 5 \times 10^3 \Omega \text{ or } 5000\Omega)$$

$$\boxed{G = \frac{1}{R} = \frac{1}{5 \times 10^3}} \text{ (6 milliamps)}$$

Conductance G

$$G = \frac{1}{R} = \frac{1}{5 \times 10^3} = 0.2 \text{ m-siemens}$$

0.2 m-si

(where s is Siemens)

$$\boxed{G = 0.2 \text{ m-si}}$$

$$\boxed{\text{Power (P)}}$$

Kirchoff's Law:-


- * Kirchoff's current law (KCL)
 - * Kirchoff's voltage law (KVL)

Kirchoff's Current Law (KCL)

EC323 Circuit Analysis

Sum of the currents entering a node is equal to the sum of the current leaving the node (or) in other words Algebraic sum of the currents at node is zero.

problem:-

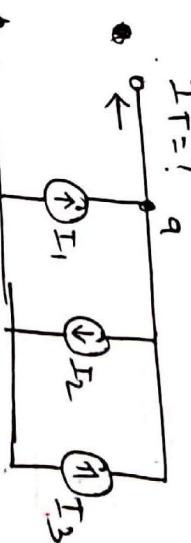

find
IT

$$u_1 + u_2 + u_4 = u_3 + u_5$$

or

Sofus hing
4 + r

wode'a'

I
18

I₃
are

en kring

T 28 IT are leaving


According to KCL $I_1 + I_2 = I_3$

$$I_T = I_1 + I_3 - I_2$$

In the figure above 'A' is the node,

currents entering the node are i_1 , i_2 , i_4 (see the arrow mark for current flowing in i_1).

Mark for
Jerechin)

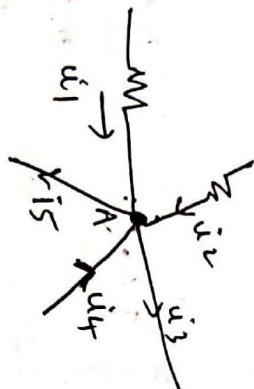


Kirchoff's voltage law (KVL)

Kirchoff's voltage law states that the algebraic sum of all voltages around a closed path or loop is zero.

Or in other words, In a close circuit,

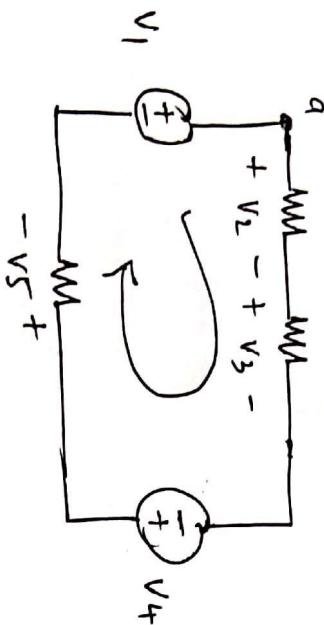Sum of the potential raise = Sum of the potential drops.



lets starts from point 'a' & traverse the loop.

$$+v_2 + v_3 - v_4 + v_5 - v_1 = 0$$

$$v_1 + v_4 = v_2 + v_3 + v_5$$

$v_1 \& v_4$ = Potential raise, $v_2, v_3 \& v_5$ - Potential drops.


Concept to remember:-

If current 'I' flows in to a resistor R_1 then a voltage drop v_1 occurs at the resistor R_1 with the Polarity shown.



Polarity of the voltage depends on the direction of the current entry. whenever

Problems:

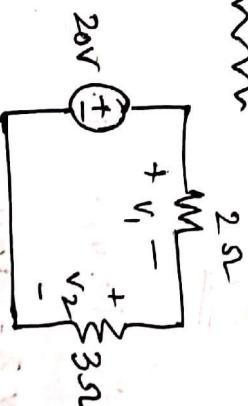

find the voltages v_1 & v_2 for the circuit shown.

Solution:-

To find v_1 & v_2 , we need to find the

current flowing through the resistors.

- * to find the total current we need to find the equivalent resistances of this circuit.
- * Resistance $R_{2\Omega}$ & 3Ω are connected in series (since the same current flows)

$$R_{eq} = 5\Omega \quad (2+3)$$

Total current $i =$

$$\frac{V}{R} = \frac{20}{5} = 4A$$

Voltage drop across 2Ω i.e. $V_1 = I \times R_1$

$$4 \times 2 = \underline{\underline{8V}}$$

Voltage drop across 3Ω i.e. $V_2 = I \times R_2$

$$4 \times 3 = \underline{\underline{12V}}$$


Verification

According to KVL voltage rise = voltage drops

$$20V = 8V + 12V$$

Voltage rise \downarrow , voltage drops \downarrow

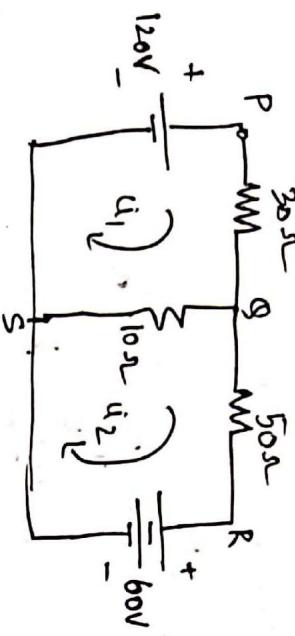1. Solve the mesh and branch currents for the circuit shown.



Solution:-

Apply KVL at loop 1 (PQSRP)

$$30u_1 + 10(u_1 - u_2) = 120$$

$$40u_1 - 10u_2 = 120 \quad \dots \textcircled{1}$$

Apply KVL at loop 2 (QRSG)

$$50u_2 + 10(u_2 - u_1) = -60$$

$$-10u_1 + 60u_2 = -60 \quad \dots \textcircled{2}$$

By using Cramer's rule find Δ

$$\Delta = \begin{bmatrix} 40 & -10 \\ -10 & 60 \end{bmatrix} = (60 \times 40) - (-10 \times -60)$$

$$\boxed{\Delta = 2300}$$

$$\Delta_1 = \begin{bmatrix} 120 & -10 \\ -60 & 60 \end{bmatrix} = (120 \times 60) - (-10 \times -60)$$

$$= 7200 - 600$$

$$\boxed{\Delta_1 = 6600}$$

$$\Delta_2 = \begin{bmatrix} 40 & 120 \\ -10 & -60 \end{bmatrix} = (40 \times -60) - (-10 \times 120)$$


$$= -2400 + 1200$$

$$\boxed{\Delta_2 = -1200}$$

$$u_1 = \frac{\Delta_1}{\Delta} = \frac{6600}{2300} = 2.86 \text{ A}$$

$$u_2 = \frac{\Delta_2}{\Delta} = \frac{-1200}{2300} = -0.521 \text{ A}$$

u_1 & u_2 are loop currents.

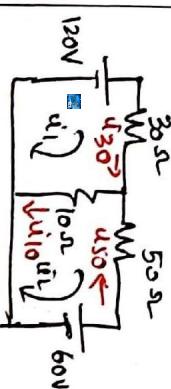

u_{30} , u_{50} & u_{10} are called branch currents.
(Supply the current at the branches).

$$\boxed{\begin{aligned} u_{30} &= u_1 &= 2.86 \text{ A} \\ u_{50} &= u - u_2 &= 0.521 \text{ A} \\ u_{10} &= u_{30} + u_{50} &= 3.381 \text{ A} \end{aligned}}$$

Note:-


u_{50} is opposite to u_2 so $u_{50} = -u_2$.

Current u_{30} & u_{50} combine & flowing

in resistor so $u_{10} = u_{30} + u_{50}$.

u_1 & u_{30} are same so $u_1 = u_{30}$.
(Refer the circuit).

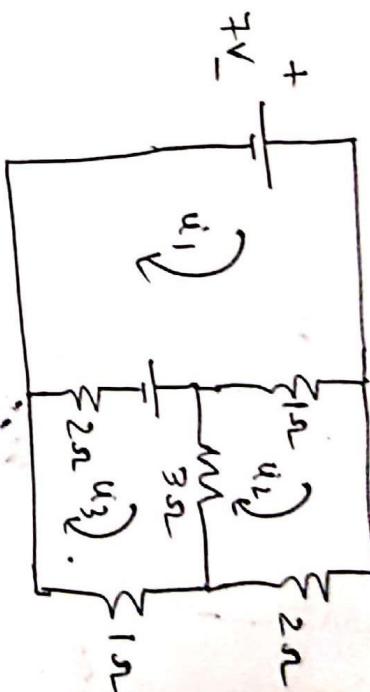2) Use the mesh analysis to determine the three mesh currents in the circuit shown.



Three loops are there in this circuit. Loop 1, 2, 3.

apply KVL in loop 1:

$$1(u_1 - u_2) + 2(u_1 - u_3) = 7 - 6$$

$$3u_1 - u_2 - 2u_3 = 1 \quad \dots \dots \dots (1)$$

loop 2

$$1(u_2 - u_1) + 2(u_2) + 3(u_2 - u_3) = 0$$

$$-u_1 + 6u_2 - 3u_3 = 0 \quad \dots \dots \dots (2)$$

$$\underline{\text{loop 3}}$$

$$3(u_3 - u_2) + 1u_3 + 2(u_3 - u_1) = 6$$

$$-2u_1 - 3u_2 + 6u_3 = 6 \quad \dots \dots \dots (3)$$

Matrix representation:-

$$\Delta = \begin{vmatrix} 3 & -1 & 2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{vmatrix} \begin{bmatrix} \dot{u}_1 \\ \dot{u}_2 \\ \dot{u}_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix}$$

$$\begin{aligned} \Delta &= \begin{vmatrix} 3 & -1 & 2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{vmatrix} \\ &= 3(36-9) + 1(-6-6) - 2(3+12) \\ &= 81 - 12 - 30 \end{aligned}$$

$$\boxed{\Delta = 39}$$

$$\Delta_1 = \begin{vmatrix} 1 & -1 & -2 \\ 0 & 6 & -3 \\ 6 & -3 & 6 \end{vmatrix} \quad \Delta_2 = \begin{vmatrix} 3 & 1 & -2 \\ -1 & 0 & -3 \\ -2 & 6 & 6 \end{vmatrix} \quad \Delta_3 = \begin{vmatrix} 3 & -1 & 1 \\ -1 & 6 & 0 \\ -2 & -3 & 6 \end{vmatrix}$$

$$\boxed{\Delta_2 = 78}$$


$$\boxed{\Delta_3 = 117}$$

$$\boxed{\Delta_1 = 117}$$

$$\dot{u}_1 = \frac{\Delta_1}{\Delta} = \frac{117}{39} = 3A \quad \dot{u}_2 = \frac{\Delta_2}{\Delta} = \frac{78}{39} = 2A \quad \dot{u}_3 = \frac{\Delta_3}{\Delta} = \frac{117}{39} = 3A$$

$$\boxed{\dot{u}_1 = 3A} \quad \boxed{\dot{u}_2 = 2A} \quad \boxed{\dot{u}_3 = 3A}$$

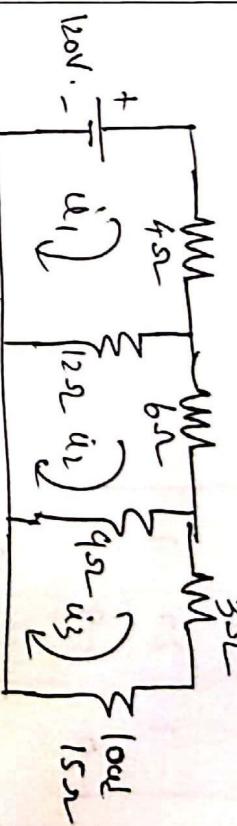3. In the circuit given in figure, obtain the load current and power delivered to the load.



Solution:-
Applying
KVL
[loop]

$$4\dot{u}_1 + 12(\dot{u}_1 - \dot{u}_2) = 120$$

$$16\dot{u}_1 - 12\dot{u}_2 = 120 \quad \dots \textcircled{1}$$

$$12(\dot{u}_2 - \dot{u}_1) + 6\dot{u}_2 + 9(\dot{u}_2 - \dot{u}_3) = 0$$

$$-12\dot{u}_1 + 27\dot{u}_2 - 9\dot{u}_3 = 0 \quad \dots \textcircled{2}$$

$$6\dot{u}_3 \quad 9(\dot{u}_3 - \dot{u}_2) + 3\dot{u}_3 + 15\dot{u}_3 = 0$$

$$-9\dot{u}_2 + 27\dot{u}_3 = 0 \quad \dots \textcircled{3}$$

Matrix representation:-

$$\begin{bmatrix} 16 & -12 & 0 \\ -12 & 27 & -9 \\ 0 & -9 & 27 \end{bmatrix} \begin{bmatrix} \dot{u}_1 \\ \dot{u}_2 \\ \dot{u}_3 \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \\ 0 \end{bmatrix}$$

Mesh Equation by Inspection Method:-

$$\Delta = \begin{vmatrix} 16 & -12 & 0 \\ -12 & 27 & -9 \\ 0 & -9 & 27 \end{vmatrix}$$

$$= 16[729 - 81] + 12[-324 - 0] + 0$$

$$\Delta = 6480$$

$$R_{11} = R_1 + R_{12} \quad (\text{sum of all resistance in the 1st loop})$$

$$R_{22} = R_2 + R_{21} \quad (\text{sum of all the resistances in the 2nd loop})$$

$$R_{21} = R_{12} = -R_L \quad (\text{total resistance shared by loops one and two, negative sign indicates the current } u_1 \text{ & } u_2 \text{ are in opposite direction})$$

$$\Delta_3 = \begin{vmatrix} 16 & -12 & 120 \\ -12 & 27 & 0 \\ 0 & -9 & 0 \end{vmatrix}$$

$$\Delta_3 = 12960$$

$$u_3 = \frac{\Delta_3}{\Delta} = \frac{12960}{6480} = 2A$$

$$u_3 = 2A$$


Current through load resistor R_L is 2A.

So Power delivered to the load is $P = u^2 R$

$$P_L = 6 \text{ W}$$

$$= 2^2 \times 15 = 60 \text{ W}$$

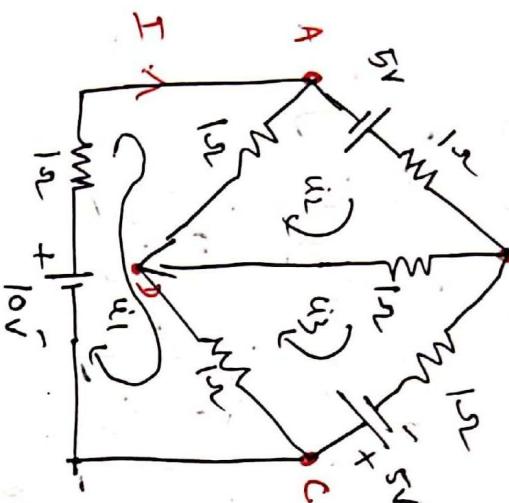2. Determine the currents in bridge circuit by using mesh analysis.



Solution:-

By using Inspection method.

$$\begin{bmatrix} R_{11} & -R_{12} & -R_{13} \\ -R_{21} & R_{22} & -R_{23} \\ -R_{31} & -R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} 1+1+1 & -1 & -1 \\ -1 & 1+1+1 & -1 \\ -1 & -1 & 1+1+1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 5 \\ 5 \end{bmatrix}$$

By applying Cramer's rule.

$$\Delta = \begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix} = 3[9-1] + 1[-3-1] - 1[1+3] = 24 - 4 - 4 = 16$$

$$\Delta_1 = \begin{vmatrix} 10 & -1 & -1 \\ 5 & 3 & -1 \\ 5 & -1 & 3 \end{vmatrix} = 120 \quad u_1 = \frac{\Delta_1}{\Delta} = \frac{120}{16} = 7.5 \text{ A}$$

$$u_1 = 7.5 \text{ A}$$

$$\Delta_2 = \begin{vmatrix} 3 & 10 & -1 \\ -1 & 5 & -1 \\ -1 & 5 & 3 \end{vmatrix} = 100 = u_2 = \frac{\Delta_2}{\Delta} = \frac{100}{16} = 6.25 \text{ A}$$

$$u_2 = 6.25 \text{ A}$$

$$\Delta_3 = \begin{vmatrix} 3 & -1 & 10 \\ -1 & 3 & 5 \\ -1 & -1 & 5 \end{vmatrix} = 100 = u_3 = \frac{\Delta_3}{\Delta} = \frac{100}{16} = 6.25 \text{ A}$$

$$u_3 = 6.25 \text{ A}$$

Current through AD is $i_1 - i_2 = 7.5 - 6.25 = 1.25\text{A}$

Current through AB is $i_2 = 6.25\text{A}$


Current through BD is $i_2 - i_3 = 6.25 - 6.25 = 0\text{A}$

Current through BC is $i_3 = 6.25\text{A}$

Current through CD is $i_1 - i_3 = 7.5 - 6.25 = 1.25\text{A}$

Nodal Method:

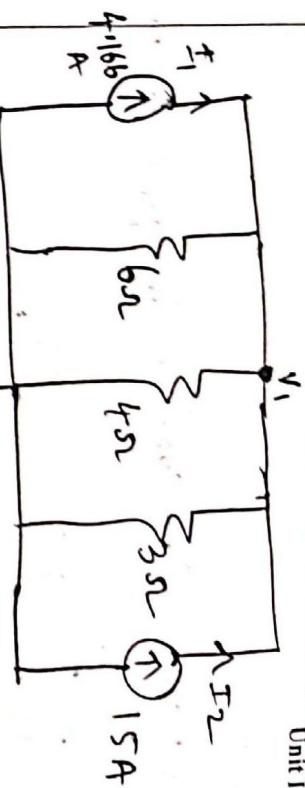- Using Nodal Analysis, obtain the currents flowing in all the resistors of the circuit.



Apply KCL at node V_1

$$4.166 + 5 = \frac{V_1}{6} + \frac{V_1}{4} + \frac{V_1}{3}$$

$$19.166 = V_1 \left[\frac{1}{6} + \frac{1}{4} + \frac{1}{3} \right]$$

$$19.166 = V_1 [0.75]$$

$$V_1 = \frac{19.166}{0.75} = 25.55\text{V}$$

Solution:- Convert all the voltage sources into equivalent sources.

$$I_1 = \frac{25}{6} = 4.166\text{A}$$


$$I_2 = 45/3 = 15\text{A}$$

Current through 6Ω resistor $= \frac{V_1}{6} = \frac{25.55}{6} = 4.25\text{A}$

Current through 4Ω resistor $\frac{V_1}{4} = 25.55 = 6.38\text{A}$

Current through 3Ω resistor $= \frac{V_1}{3} = \frac{25.55}{3} = 8.51\text{A}$

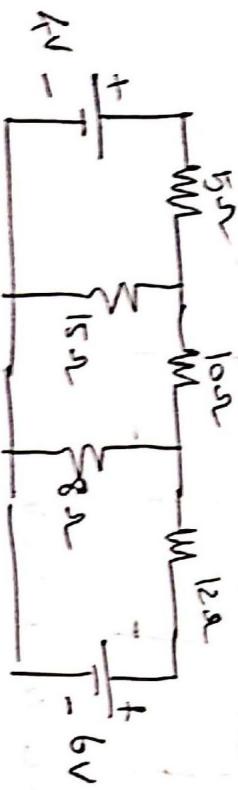2. Using Nodal Method find Current through 8Ω resistor




Convert all the voltage sources in to equivalent current sources.

$$I_1 = 4/5 = 0.8 \text{ A}$$

$$I_2 = 6/12 = 0.5 \text{ A}$$

Circuit becomes

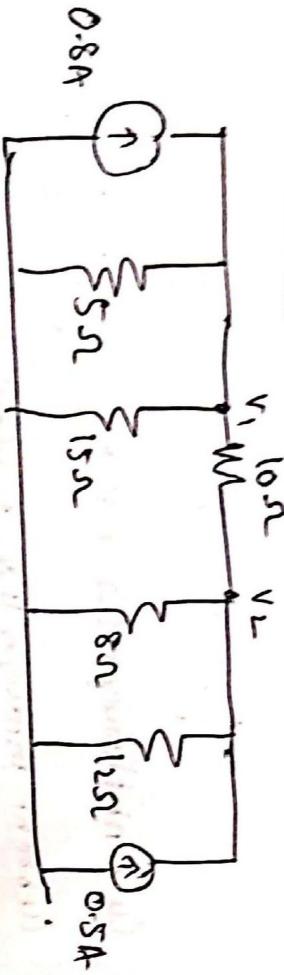

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{15} + \frac{1}{10} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{1}{10} + \frac{1}{8} + \frac{1}{12} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0.8 \\ 0.5 \end{bmatrix}$$

Matrix form by inspection method.

$$\Delta = \begin{vmatrix} 0.366 & -0.1 \\ -0.1 & 0.308 \end{vmatrix} = 0.112 - 0.01$$

$$\Delta_{V_1} = \begin{vmatrix} 0.8 & -0.1 \\ 0.5 & 0.308 \end{vmatrix} = 0.2964$$

$$\Delta_{V_2} = \begin{vmatrix} 0.366 & 0.8 \\ -0.1 & 0.5 \end{vmatrix} = 0.263$$


$$V_1 = \frac{\Delta_{V_1}}{\Delta} = \frac{0.2964}{0.1102} = 2.905 \text{ V}$$

$$V_2 = \frac{\Delta V_2}{\Delta} = \frac{0.263}{0.102} = 2.578 \text{ V}$$

$$\boxed{V_L = 2.578 \text{ V}}$$

Current through 8Ω resistor = $\frac{V_2}{8} = \frac{2.578}{8} = 0.322 \text{ A}$

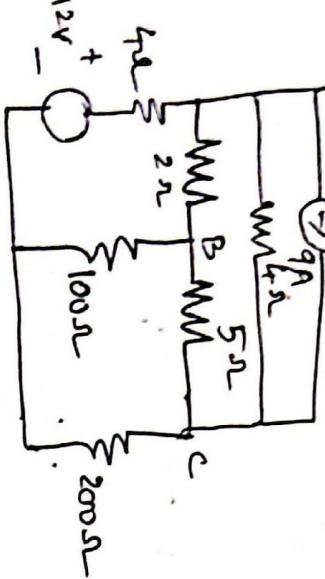
3. Use nodal analysis to determine the voltage across 5Ω resistance and the current in the 12V sources.



Solution:- Convert voltage source into current source.

$$I = \frac{V}{R} = \frac{12}{4} = 3 \text{ A}$$

Circuit becomes:

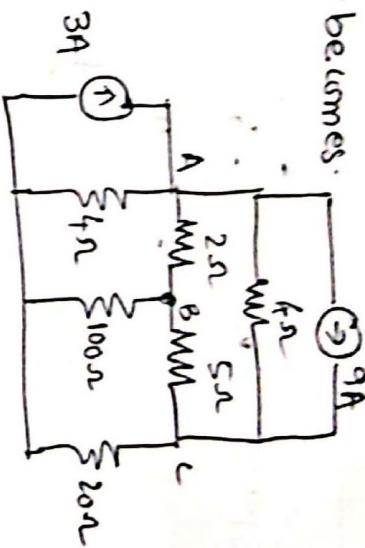

At node A, the current is $3 - 9 = -6 \text{ A}$
At node B, the current is zero.
At node C, the current is 9 A

Node equation in matrix form

$$\begin{bmatrix} \frac{1}{4} + \frac{1}{2} + \frac{1}{4} & -\frac{1}{2} & -\frac{1}{4} \\ -\frac{1}{2} & \frac{1}{2} + \frac{1}{100} + \frac{1}{5} & -\frac{1}{5} \\ -\frac{1}{4} & -\frac{1}{5} & \frac{1}{5} + \frac{1}{20} + \frac{1}{4} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 9 \end{bmatrix}$$

$$\begin{bmatrix} 1 & -0.5 & -0.25 \\ -0.5 & -0.71 & -0.2 \\ -0.25 & -0.2 & 0.5 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 9 \end{bmatrix}$$

Solve V_B & V_C

$$\Delta = \begin{vmatrix} 1 & -0.5 & -0.25 \\ -0.5 & 0.71 & -0.2 \\ -0.25 & -0.2 & 0.5 \end{vmatrix}$$

$$= \boxed{\Delta = 0.0956}$$

$$= ((0.355 - 0.04) + 0.5(-0.254 - 0.05) - 0.25(0.1 + 0.175))$$

$$= 2.475$$

$$\Delta V_C = 2.475$$

$$V_C = \frac{\Delta V_C}{\Delta} = \frac{2.475}{0.0956} =$$

$$\boxed{V_C = 25.88 \text{ V}}$$

Voltage across 5Ω is $V_B - V_C$

$$= 11.76 - 25.88$$

$$\boxed{V_{5\Omega} = -14.12 \text{ V}}$$


$$\Delta V_B = \begin{vmatrix} 1 & -0.5 & -0.25 \\ -0.5 & 0 & -0.2 \\ -0.25 & 0 & 0.5 \end{vmatrix}$$

$$= 1.125$$

$$\Delta V_B = 1.125$$

$$V_B = \frac{\Delta V_B}{\Delta} = \frac{1.125}{0.0956} = \underline{\underline{11.76 \text{ V}}}$$

Voltage Division rule:-

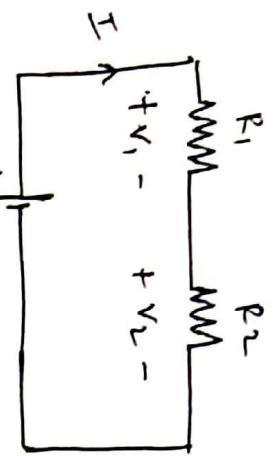

If two resistors are connected in series and if the total voltage applied is V , then the voltage across any one resistance can be found by using the formula


$$\frac{\text{Total Voltage} \times \text{Sum of Resistances}}{\text{Sum of the Resistances}}$$

Sum of the Resistances.

$$V_1 = \frac{V \times R_1}{R_1 + R_2}$$

$$V_2 = \frac{V \times R_2}{R_1 + R_2}$$

Current Division Rule:-

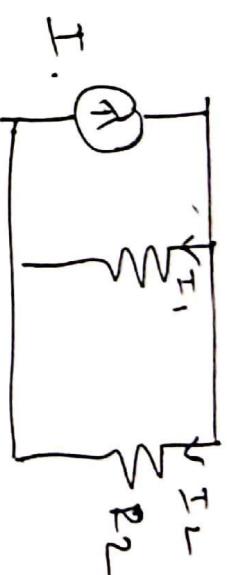

If two resistors are connected in parallel and the total current entering the parallel combination is known, then the current flowing through the resistors can be calculated using

$$\frac{\text{Total Current} \times \text{Opposite Resistance}}{\text{Sum of the Resistances}}$$

Sum of the Resistances.


$$I_1 = \frac{I R_1}{R_1 + R_2}$$

$$I_2 = \frac{I R_2}{R_1 + R_2}$$

Super Position Theorem:-

Super Position Theorem states that the response

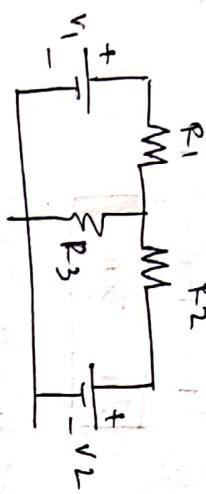In a circuit with multiple sources is given by the algebraic sum of responses due to individual sources acting alone.




Procedure/Steps:

① In a circuit with multiple sources keep only one source active (V_1 - active, V_2 - short)


② Remove all the other sources (voltage sources must be short circuited, current sources must be open circuited)

③ Find the response of the circuit for the individual sources and label the term as I_1' , I_2' & I_3' etc.

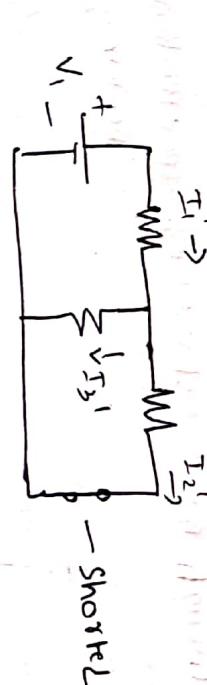④ Now keep the other source active and remove the first source.



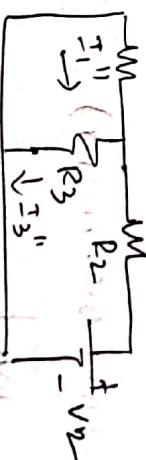⑤ Now take find the response due to the source V_2 and label the current as I_1'' , I_2'' & I_3'' .



Follow the same procedure if more than two sources present.

⑥ Now find the overall response of the circuit by sum up the individual responses.

$I_1 = I_1' + I_1''$ [Note: depending upon the direction assumed sign may vary, once current is calculated other parameters like voltage, current can be calculated]


$$I_2 = I_2' + I_2''$$

$$I_3 = I_3' + I_3''$$

- ① Find the current through 5Ω resistor using superposition Theorem.



Soln: Keep 10A active & remove 20A

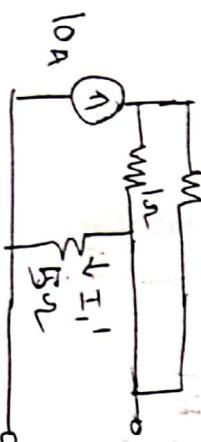

from the fig above current through 5Ω is $10A$

(Even though the current $10A$ divides between two 1Ω

it again join at center 5Ω resistor)

$$[I_L' = 10A]$$

Soln:

Keep 20A active & remove 10A




So total current through 5Ω resistor $I = I_L' + I_L''$

$$I_L = 10A + 20A$$

$$[I_L = 30A]$$

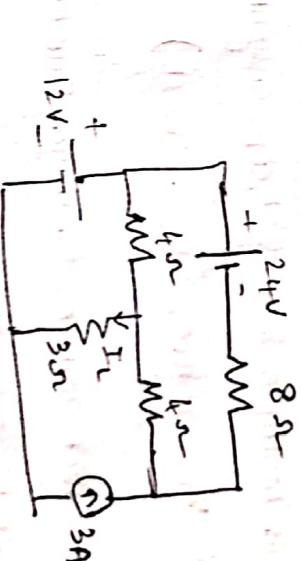
- ② Using Super position theorem find the current through 3Ω resistor.



Soln: - Keep 12V source active 24V short, 3A-open circuit

By inspecting the circuit itself we can observe, the current through 3Ω now is $20A$.

$$[I_L'' = 20A]$$

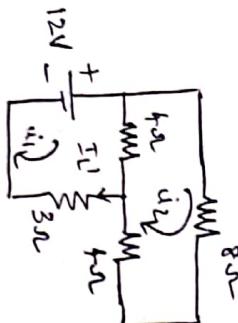

By KVL

$$-7u_1 + 4u_2 = -12 \quad \text{--- (1)}$$

$$4u_1 + 6u_2 = 0 \quad \text{--- (2)}$$


$$\text{So } I_L' = 2A$$

(Since $u_1 = I_L'$ in this circuit)

$$u_1 = 2A$$

$$u_2 = 0.5A$$

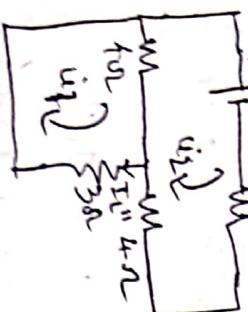Step 2 Keep 24V source active & 12V source short circuited and 3A open circuit.



Let I_L'' be the current through


voltage source 24V

$$16u_1 - 4u_1 = -24 \quad \text{--- (1)}$$

$$7u_1 - 4u_2 = 0 \quad \text{--- (2)}$$

$$u_1 = -1.95A$$


$$I_L'' = u_1 = -1A$$

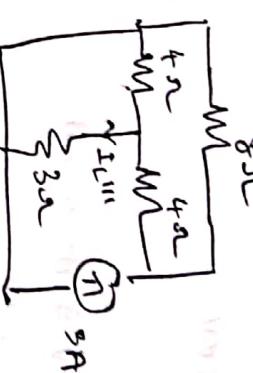

$$4\Omega \parallel 3\Omega = \frac{4 \times 3}{4+3} = 1.714\Omega$$

$$I_{S1} = \frac{3 \times 8}{4+7.14+8} \quad (\text{By current division rule})$$

$$I_{S1} = 1.887A$$

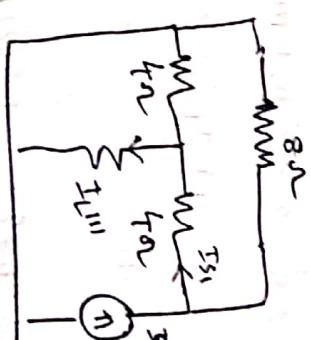

Current Division Rule.

$$I_{L'''} = 1.07A$$

$$\text{So } I_L = I_L' + I_L'' + I_L'''$$


$$= 2 - 1 + 1.07 = 3.07A$$

$$I_L = 3.07A$$


Step 3: Keep 12V & 24V source short circuited and 3A source active.

Let $I_L''' = I_{3\Omega}$ due to 3A source.

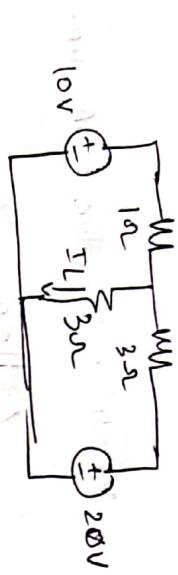- (3) Find the current I_L in the circuit using Super Position Theorem



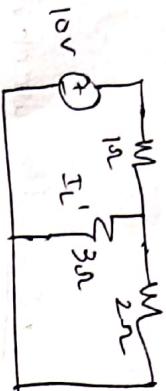Step 1: Keep 10V source active & 20V short circuit.




$$I_{S1}' = \frac{10}{1+3} = \frac{10}{4} = 2.5A$$



$$I_{S2}'' = \frac{20}{2+0.75} = \frac{20}{2.75} = 7.27A$$

$$I_L'' = I_{S2} \times \frac{1}{1+3}$$
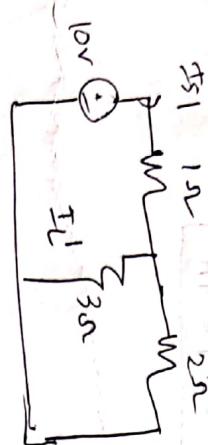
$$I_L'' = 7.27 \times \frac{1}{4} = 1.818A$$



$$I_{S3}''' = \frac{10}{2+3} = \frac{10}{5} = 2A$$

2 & 3 Ω are in parallel
So current I_L''' can be calculated using current division rule.

$$I_L''' = \frac{I_{S1} \times 2}{2+3} = \frac{4.54 \times 2}{5} = 1.8182A$$

$$\boxed{I_L''' = 1.8182A}$$

~~$$I_{S2} = \frac{20}{2+0.75} = 7.27A$$~~

$$I_L''' = \sqrt{I_{S2} \times I_{S3}} = \sqrt{7.27 \times 2} = 3.6364A$$

$$I_L = I_L' + I_L''$$

$$= 2.5 + 1.8182 = 4.3182A$$

Thevenin's Theorem:-

merit's theorem states that a circuit with two terminals can be replaced with an equivalent circuit consisting of a voltage source in series with a resistance or impedance.

519

Shops: - (calcutta) B.H. / E.

skip: Remove the local version

Step 2: Remove all the voltage sources (short circuit)

Measure the resistance across the load terminals, when is the theremin's resistance (R_{load})

Steps to calculate V_{TH} (Thermin's equivalent voltage)

... permit the load resistor and then measure the voltage drop across the load terminal, which gives the open circuit voltage also called (reverse) voltage


Step 3: To calculate the current through load resistance
use the formula.

$$I_L = V_m / R_m + R_L$$



redraw the circuit as shown above & find I_L .

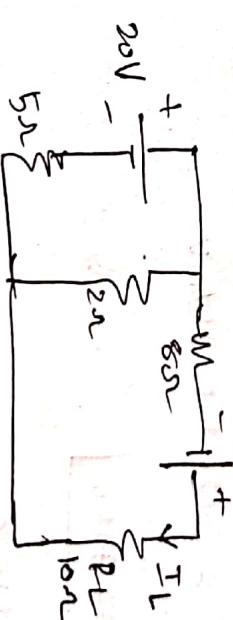PROBLEMS: Determine the current in using Thévenin's theorem.



$$2u_1 + 5u_2 = 20$$


$$M = 20.7 \times 10^{-4}$$

Voltage across 2Ω resistor

$$V_{2\Omega} = I_{2\Omega} \times R \\ = 2.857 \times 2$$

$$V_{2\Omega} = 5.714V$$

12 V voltage source is added

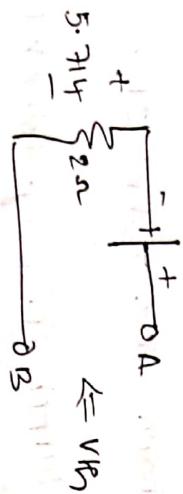


$$V_{th} = 12 + V_{2\Omega} = 12V + 5.714V$$

$$V_{th} = 17.714V$$

SOP To calculate R_{th}

remove load, short circuit - voltage source

open circuit - current source

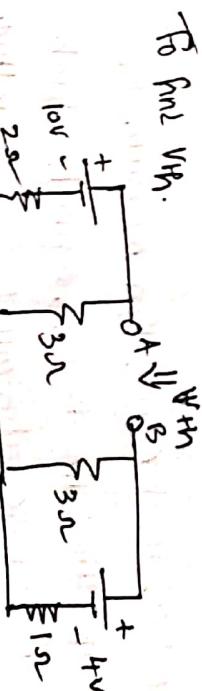

$$R_{th} = 8 + \frac{5 \times 2}{5+2} = 8 + 1.428 = 9.428\Omega$$

$$R_{th} = 9.428\Omega$$


Step 3 To calculate load current I_L

$$I_L = V_{th} / R_{th} + r$$


$$I_L = \frac{17.714}{9.428 + 1} = 0.9118A$$


$$I_L = 0.9118A$$

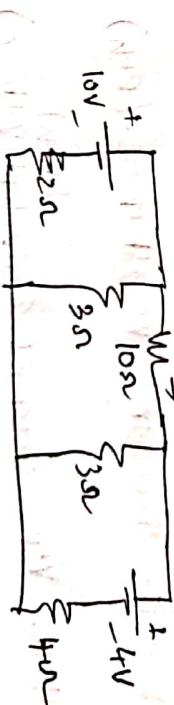② Using Thévenin's theorem find the current I_L in the circuit.



To find V_{th} .

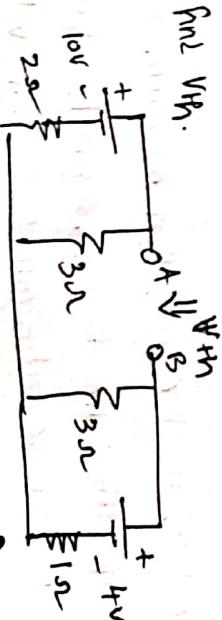

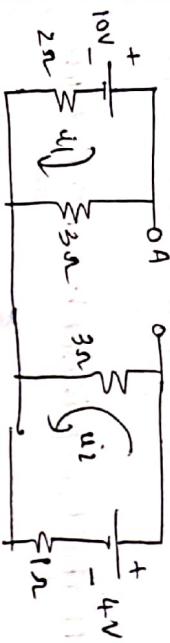

loop

$$3u_1 + 2u_1 = 10$$

$$5u_1 = 10$$

$$\boxed{u_1 = 2A}$$


loop P2

$$3u_2 + 1u_2 = 4$$

$$4u_2 = 4$$

$$\boxed{u_2 = 1A}$$

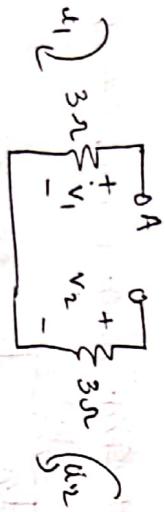
To find voltage drop across A & B, we need to find voltage drop across both the 3Ω resistors.



$$R_{Th} = \left(\frac{3 \times 2}{3+2} \right) + \left(\frac{3 \times 1}{3+1} \right)$$

$$\boxed{R_{Th} = 1.95\Omega}$$

Thevenin's circuit:

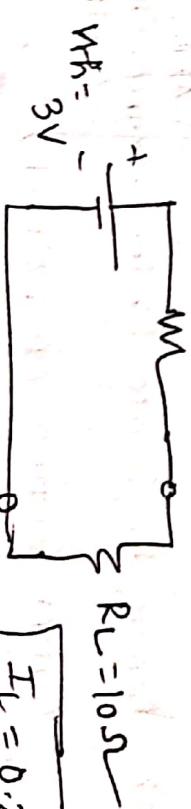

$$v_{th} = 3V - \boxed{R_L = 10\Omega}$$

$$A \rightarrow M \rightarrow M \rightarrow B$$

$$+ V_1 -$$

$$- V_2 +$$

$$6V$$

$$3V$$


$$So \quad V_{AB} = V_{th} = 6V - 3V = 3V$$

$$\boxed{V_{th} = 3V}$$

To find Thevenin's Resistance R_{th}



Redraw the circuit.

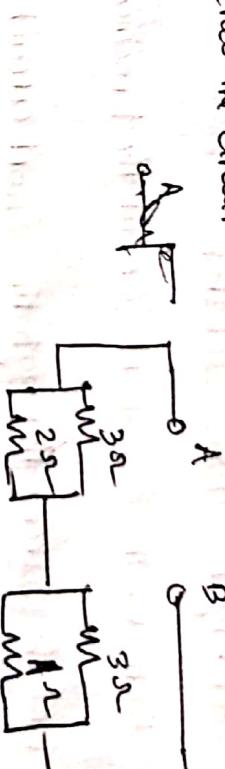

$$I_L = V_{th}$$

$$= \frac{3}{R_{th} + R_L}$$

$$= 0.251A$$

Norton's Theorem:

States that it is possible to simplify any linear circuit

to an equivalent circuit with just a single current source and parallel resistance connected to a load.

Steps: To calculate Norton's current:

Step 1: Identify the load resistor.

Step 2: Remove it & short circuit the terminal.

Step 3: Find the current through the short circuit terminal which is Norton's current (I_N).

Steps: To calculate R_N or P_N (Norton's Resistance)

Step 1: Remove the load resistor (R_L) & label the terminal as A & B


Step 2: Remove the source (voltage source - short circuit current source - open circuit)

Step 3: Measure the resistance across the terminals A & B, which gives the Norton's resistance (R_N)

Step 3: Draw the Norton's equivalent circuit & its formula

$$I_{th} = I_N \cdot R_N$$

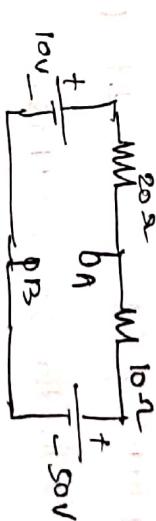Solution:- ① Find the Thvenin's & Norton's equivalents of the circuit with respect to terminal A & B.




Solution:- To find R_{th} short circuit voltage sources.



$$R_{th} = \frac{20 \times 10}{20 + 10} = 6.667\Omega$$

Step 2 To find V_{th}

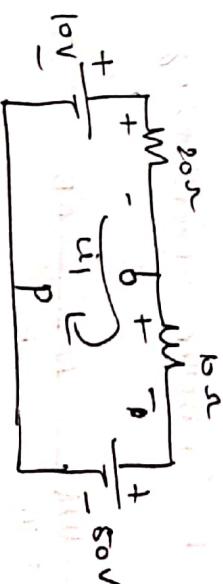

$$R_{th} = \frac{20 \times 10}{20 + 10} = 6.667\Omega$$


$$20\dot{u}_1 + 10\ddot{u}_1 + 50 - 10 = 0$$

$$30x_1 = -40$$

$$d_1 = -40/30 = -1.33A.$$

$$u_1 = -1.33A$$

Voltage across A & B is either

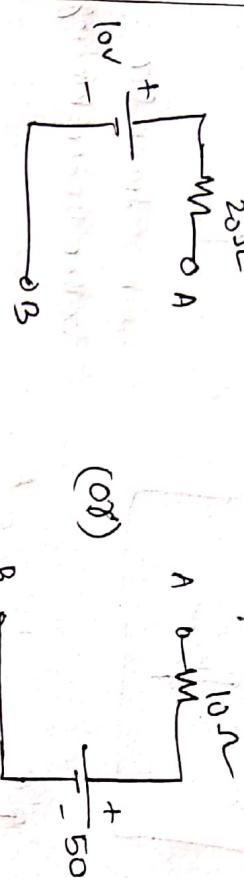


$V_{AB} = 10V$ - Voltage across 2Ω

$$V_{20\Omega} = U_1 \times 20 = -26.66V$$

$$V_{TH} = V_{AB} = 10 - (-26.66 \text{ V})$$

$$V_{TH} = 36.66V$$

for Noether's Theorem.

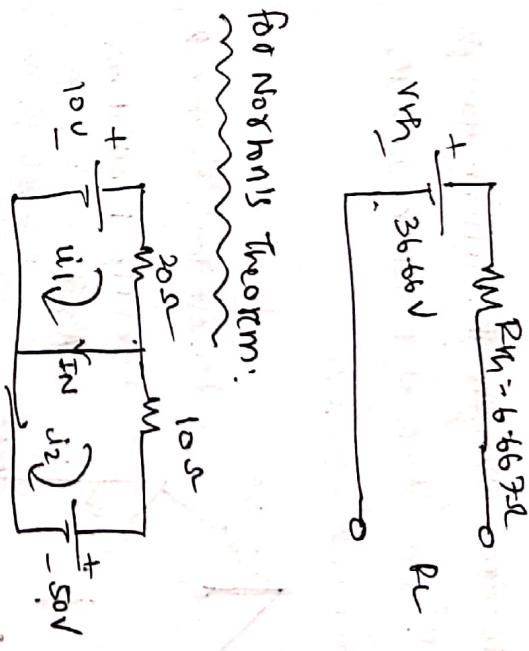

$$20 \mu = 10$$

$$u_2 = -5A$$

$$T_N = u_1 - u_2$$


$$= 0.5 - \left(\frac{1}{2}\right)$$

Nox'n's Equivalent Cct:

$$I_N = 5.5A$$

A circuit diagram consisting of a vertical line representing a battery labeled 'B'. A horizontal line extends from the right side of the battery. A resistor is represented by a zigzag line labeled 'R = 5.5 Ω' in red ink. A voltmeter, represented by a circle with two leads, is connected across the resistor. The circuit then continues as a single horizontal line to the right, ending with an open terminal pair labeled 'A'.

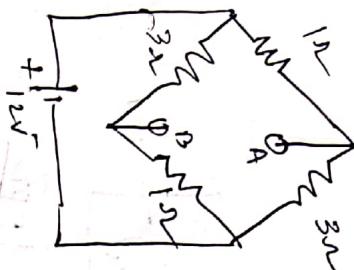- (2) Using Norton's theorem, determine the current through an ammeter connected across A & B of the circuit, take the resistance of the ammeter as 0.5Ω



1. Remove load resistor R_B & short circuit the terminals A & B.

2. Short circuit the terminal A & B and find the current through it

$$u_1 + 3u_1 - 3u_3 = 0 \text{ --- (1)}$$

$$4u_1 - 3u_3 = 0 \text{ --- (2)}$$

$$4u_2 - 1u_3 = 0 \text{ --- (3)}$$

$$u_1 = 6A$$

$$u_2 = 2A$$


$$u_3 = 8A$$

$$I_N = u_1 - u_2$$

$$= 6 - 2 = 4A$$

$$\boxed{I_N = 4A}$$


To find R_N or P_N

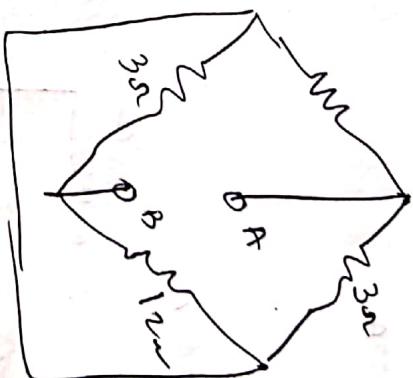

Circuit drawn for better understanding

$$\boxed{R_N = 1.5\Omega}$$

Norton's Equivalent Circuit:

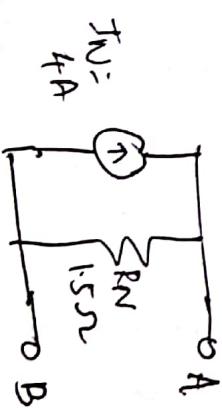

Maximum Power Transfer Theorem (MPT)

MPT states that maximum power will be delivered to the load when the load impedance and source impedance are equal.

Steps:

(1) Find R_h (Remove voltage source; current source & load resistance & label the


terminal as A & B) find V_{th} (Thevenin's equivalent voltage) i.e. the voltage across the terminals A & B.

(2) Find maximum power using the formula.

$$P_{max} = \frac{V_{th}^2}{4R_h}$$

Soln

Step:- Find R_h (Remove R)

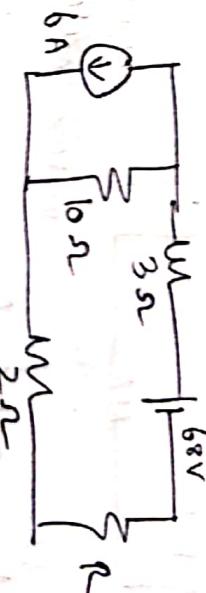

① find the value of 'R' for maximum power transfer

and calculate the maximum power.

so


$$V_{th} = 12.8V$$

be v_A 60V and v_B 0V

$$V = IR \quad (\text{By source transformation formula})$$

$$60V + \frac{-}{+} \frac{10\Omega}{10\Omega + 3\Omega + 6.8\Omega} \times 6.8\Omega = A \quad \Leftarrow V_{th}.$$

Step 2 To find R_{th}

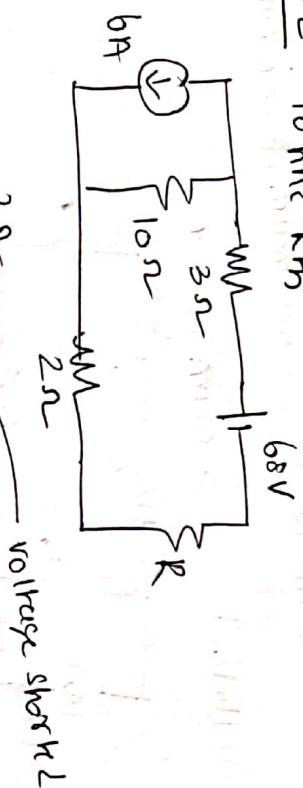

EnggTree.com
Current source open

$$R_{th} = 3 + 10 + 12 = 15\Omega$$

Steps:-

1. Interchange the position of source & response.

[Voltage - Short
current - open]

2. find the response at the particular branch.

Beto
3. compare it with the response before
Interchanging.


maximum power P_{max}

$$P_{max} = V_{th}^2 / 4R_{th}$$


$$= \frac{(128)^2}{4 \times 15} = 273.06W$$

$$P_{max} = 273.06W$$

1. Calculate I_X prove the reciprocity theorem by interchanging the position of $10V$ source & I_X .

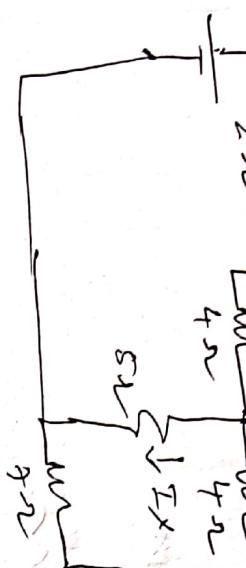Soln:

Interchanging source & response.

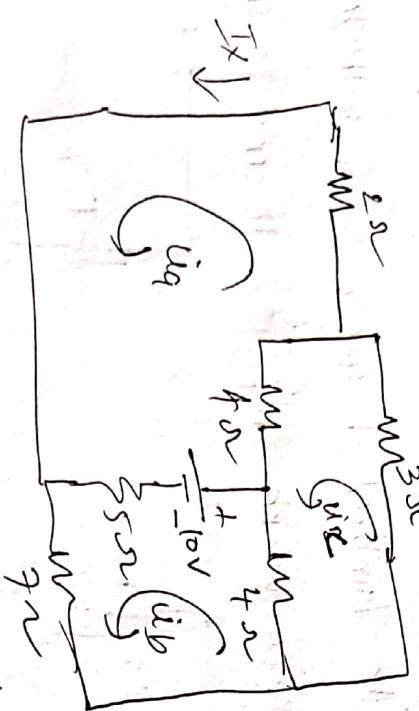

$$\begin{bmatrix} 2+4+5 & -5 & -4 \\ -5 & 5+4+3 & -4 \\ -4 & -4 & 3+4+4 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_x \end{bmatrix} = \begin{bmatrix} 10 \\ -11 \\ 0 \end{bmatrix}$$


$$\Delta = 1069$$

$$\Delta_a = \begin{bmatrix} 10 & -5 & -4 \\ -10 & 16 & -4 \\ 0 & -4 & 11 \end{bmatrix} = 890$$

$$I_X = I_a = \frac{\Delta_a}{\Delta} = \frac{890}{1069}$$

$$I_X = I_a = \frac{\Delta_a}{\Delta} = \frac{890}{1069} = 0.8326A$$

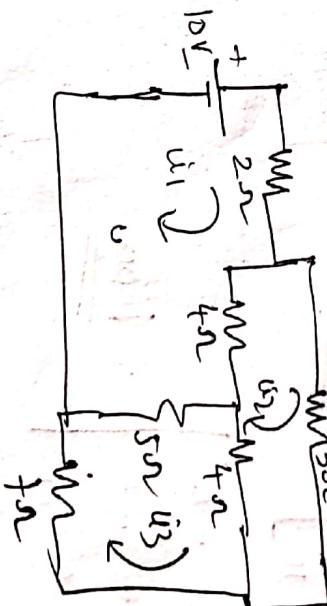for original circuit (original position of the voltage source)




$$I_X = I_1 - I_2$$

$$Z_{eq} = \frac{1}{\frac{1}{z_1} + \frac{1}{z_2} + \dots + \frac{1}{z_n}}$$

$$E_{eq} = \left[\frac{E_1}{z_1} + \frac{E_2}{z_2} + \frac{E_3}{z_3} + \dots + \frac{E_n}{z_n} \right] Z_{eq}$$


$$E_{eq} = \left[\frac{20}{8} + \frac{10}{2} + \frac{5}{10} \right] \times 1.3793$$

$$E_{eq} = 11.0344 \text{ V}$$

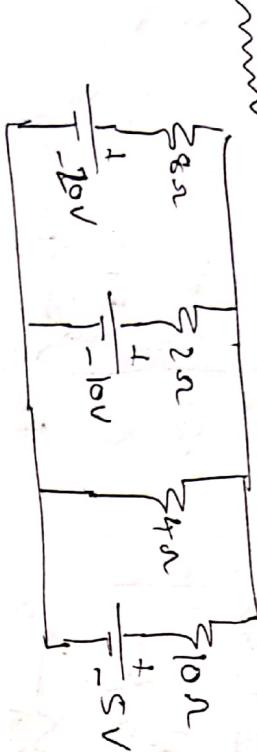


Problem:-

Soln Re-arranging the circuit.

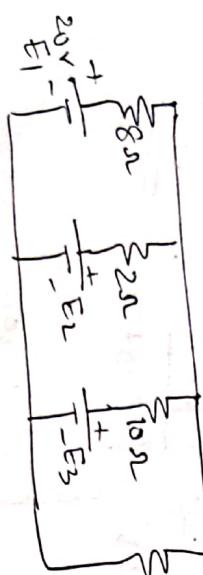

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{8} + \frac{1}{2} + \frac{1}{10}}$$

$$R_{eq} = 1.3793 \Omega$$

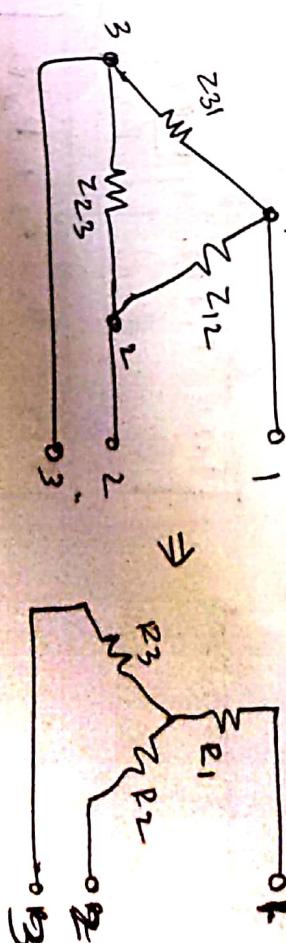

Impedance in Star to delta ($\lambda \rightarrow \Delta$) & Delta to Star



$$\begin{aligned} R_{eq} &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \\ &= 1.3793 \Omega \\ E_{eq} &= \frac{1}{I} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \\ &= 11.0344 \text{ V} \\ V &= IR \\ I &= V/R \\ &= 11.0344 / (1.3793 + 4) \end{aligned}$$

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$


Star to Delta:

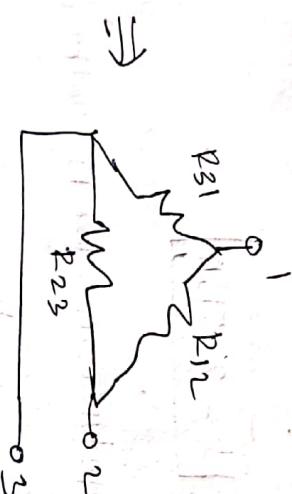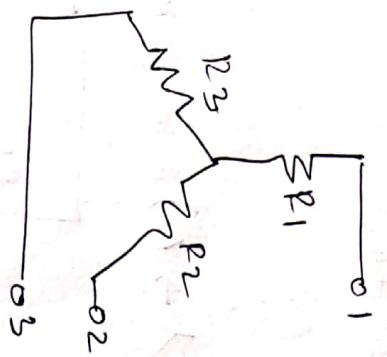

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$
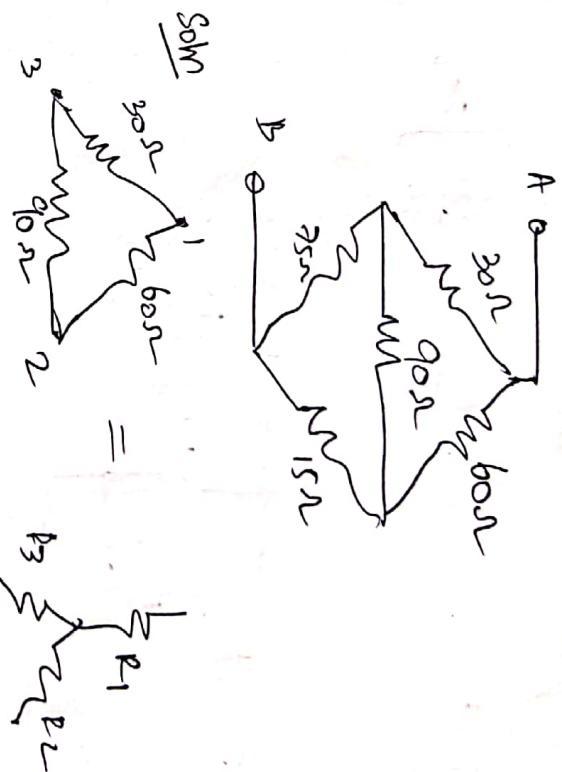
$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$



$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$


$$= \frac{60 \times 30}{30 + 90 + 60} = \underline{\underline{10\Omega}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$= \frac{60 \times 90}{30 + 90 + 60} = \underline{\underline{30\Omega}}$$

$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$
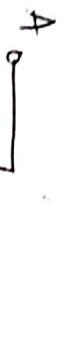
$$= \frac{30 \times 90}{30 + 90 + 60} = \underline{\underline{15\Omega}}$$



15Ω & 30Ω are in series




30Ω & 15Ω are in series

so

15Ω

10Ω


30Ω

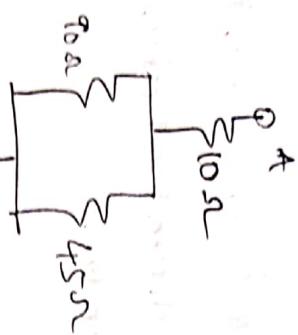

10Ω & 15Ω are in


parallel.
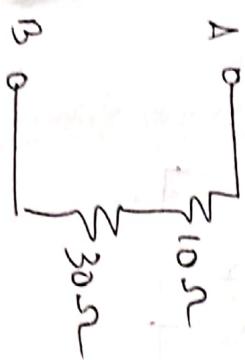
$$10\Omega \parallel 15\Omega = \underline{\underline{30\Omega}}$$



$$R_{AB} = 40\Omega$$

Duality:

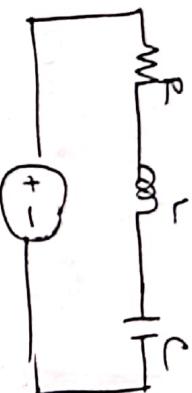

Original network

Dual network

- * In an electrical network, electrical terms are associated in pairs called as duals.
- * A dual of a expression is formed by interchanging voltage & current in the expressions

Dual elements

Original	Dual
Resistance	Conductance
Capacitance	Inductance
Inductance	Capacitance
Voltage source	Current source

original

Dual

Current Source

Source Branch

Mesh equation

KCL

Switch closed at
 $t=0$

Open circuit

Short circuit

Impedance

Reactance

Susceptance

Voltage source

Parallel Branch

Node equation

KVL



Switch opened at
 $t=0$

Short circuit

Open circuit

Admittance

Conductance

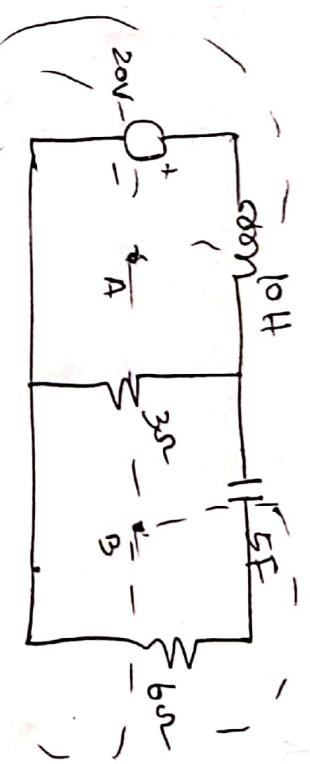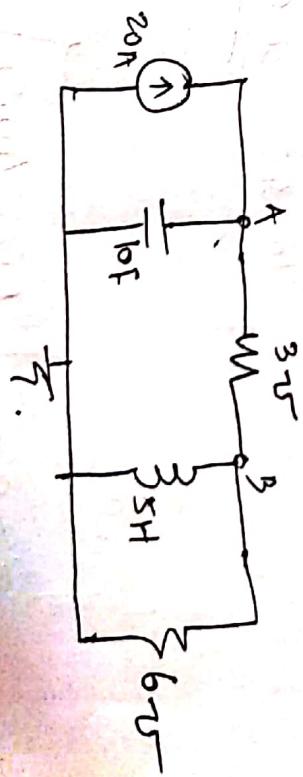

① Label A & B inside loops & place reference node outside

② Draw a dotted line from each node to reference node through all the available branches.

③ Draw its dual.

Draw the dual of the network shown.


Sinusoid \rightarrow is a signal that has the form of the cosine or sine function.

$$v(t) = V_m \sin \omega t$$

V_m = amplitude of the sinusoid.

ω = angular frequency in radians

ωt = the argument of the sinusoid.

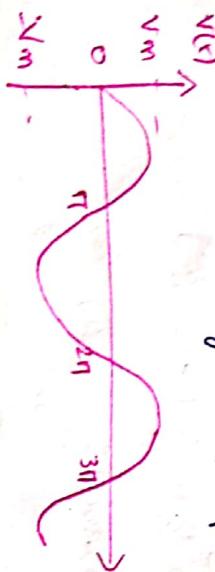

$$\omega T = 2\pi$$

$T = \text{Period of sinusoid}.$

$$T = \frac{2\pi}{\omega}$$


$$\omega = 2\pi f$$

If $f = \text{frequency in hertz} \Rightarrow \omega = \text{angular frequency}.$

'f' is also called cycle frequency.

ϕ = phase.

$$v_2 = V_m \sin(\omega t + \phi)$$

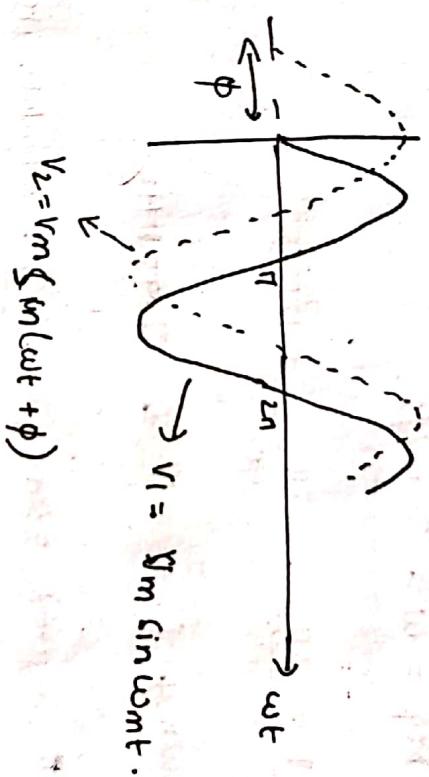

$$v_2 = V_m \sin(\omega t + \phi)$$

The starting point of v_2 occurs first in time, therefore we say that v_2 leads v_1 by ϕ (or) v_1 lags v_2 by ϕ .

If $\phi = 0 \Rightarrow v_1$ & v_2 are in-phase.
 $\phi \neq 0 \Rightarrow v_1$ & v_2 are out-of phase.

$f = \text{frequency in hertz} \Rightarrow \omega = \text{angular frequency}.$

More general expression for the sinusoid.

$$v(t) = V_m \sin(\omega t + \phi)$$

① Find the amplitude, phase & frequency of the sinusoid.

$$V(t) = 12 \cos(50t + 10^\circ)$$

$$\text{Amplitude} = V_m = 12 \text{ V}$$

$$\text{Phase} = \phi = 10^\circ$$

$$\text{Angular freq} = \omega = 50 \text{ rad/s}$$

$$\text{Period } T = \frac{2\pi}{\omega} = \frac{2\pi}{50} = 0.1257 \text{ s}$$

$$\text{Frequency } f = \frac{1}{T} = 7.958 \text{ Hz}$$

Given the sinusoid $v = 5 \sin(4\pi t - 60^\circ)$, calculate its amplitude, phase, angular frequency, period and frequency.

$$\text{Amplitude} = 5 \text{ V}$$

$$\text{Phase} = -60^\circ$$

$$\text{Angular frequency } \omega = 4\pi = 4 \times 3.14 = 12.56 \text{ rad/sec}$$

$$\text{frequency } f = \frac{\omega}{2\pi} = \frac{12.56}{2 \times \pi} = \underline{\underline{2 \text{ Hz}}}$$

② Calculate the phase angle between $V_1 = -10 \cos(\omega t + 50^\circ)$ and $V_2 = 12 \sin(\omega t - 10^\circ)$. State which sinusoid is leading.

$$V_1 = -10 \cos(\omega t + 50^\circ)$$

$$= 10 \cos(\omega t + 180^\circ - 180^\circ)$$

$$= 10 \cos(\omega t - 130^\circ) \quad \text{(Explain how to get this)}$$

$$V_2 = 12 \sin(\omega t - 10^\circ) = 12 \cos(\omega t - 10^\circ - 90^\circ)$$

$$V_2 = 12 \cos(\omega t - 100^\circ) \quad \text{--- --- ②. ex}$$

From ① & ② Phase difference between V_1 & V_2 is 30° .

V_2 leads V_1 by 30° .

Phasor:

A phasor is a complex number that represents the amplitude and phase of a sinusoid.

Rectangular form:

$$Z = x + jy$$

Complex no in rectangular form.

$$j = \sqrt{-1}$$

$x \Rightarrow$ real part

$y \Rightarrow$ imaginary part

Polar form:

$$Z = r \angle \phi = r e^{j\phi}$$

Complex no can also be written in polar form:-

Exponential form .

$\delta =$ magnitude of 'Z'
 $\phi =$ phase of Z

$Z = r e^{j\phi} \Rightarrow$ Rectangular form

$Z = r \angle \phi \Rightarrow$ Polar form

$Z = \delta e^{j\phi} \Rightarrow$ Exponential form.

Addition & Subtraction are better performed in rectangular form.

Multiplication & Division are better performed in Polar form

Addition:

$$Z_1 + Z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

Subtraction:

$$Z_1 - Z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

multiplication:

$$Z_1 Z_2 = r_1 r_2 \angle (\phi_1 + \phi_2)$$

Division:

$$\frac{Z_1}{Z_2} = \frac{r_1}{r_2} \angle (\phi_1 - \phi_2)$$

Reciprocal:

$$\frac{1}{Z} = \frac{1}{Y} L - \phi$$

Square root

$$\sqrt{Z} = \sqrt{Y} L - \phi/2$$

Complex Conjugate:

$$Z^* = x - jy = r L - \phi = r e^{-j\phi}$$

$$V(t) = V_m \cos(\omega t + \phi) = \text{Time Domain representation}$$

Polar Diagram:

Phasor Diagram showing:

$$V = V_m L - \phi \quad \& \quad I = I_m L - \theta$$

Problems:

Transform the sinusoids to phasors.

$$\textcircled{1} \quad u = 6 \cos(50t - 40^\circ) A$$

$$\boxed{I = 6 L - 40^\circ A}$$

$$\textcircled{2} \quad V = -4 \sin(30t + 50^\circ) V$$

$$\approx 4 \cos(30t + 150^\circ + 90^\circ) \quad (\text{Since } -\sin A = \cos(A + 90^\circ))$$

$$\boxed{V = 4 L 140^\circ V}$$

$$\textcircled{3} \quad V = -7 \cos(2t + 40^\circ) V \\ = 7 \cos(2t + 40 + 180^\circ) \\ = 7 \cos(2t + 220^\circ) V$$

$$\boxed{V = 7 L 220^\circ V}$$

(4) $\dot{u} = 4 \sin(10t + 10^\circ) V$

$$= 4 \cos(10t + 10^\circ - 90^\circ) V$$

$$= 4 \cos(10t - 80^\circ) V$$


$$\dot{u} = 4 \angle -80^\circ V$$

Phasor Relation ship for circuit elements:-

$$\dot{u} = I_m \cos(\omega t + \phi) = Current$$

$$V = u_R$$

$$V = R I_m \cos(\omega t + \phi)$$

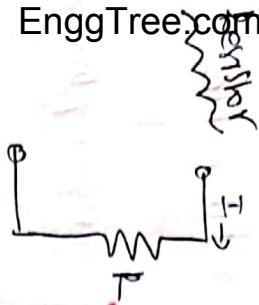

Phasor form:-


$$V = R I_m \angle \phi$$

Phasor diagram for resistor

$$I = I_m \angle \phi$$

$$V = IR.$$

Voltage and current are in-phase.

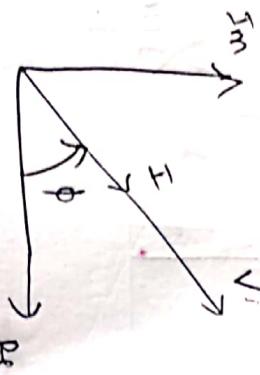

For Inductor:-

$$+ \frac{d\dot{u}}{dt}$$

$$V$$

Time Domain

$$V = L \frac{di}{dt}$$

$$V = j\omega L I$$

freq-domain

Assume current through inductor is $\dot{u} = I_m \cos(\omega t + \phi)$

$$V = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \phi)$$

-phasor

$$V = \omega L I_m \cos(\omega t + \phi + 90^\circ)$$


$$[- - \sin A = (\cos(A + 90^\circ))$$

$$V = \omega L I_m \angle \phi + 90^\circ$$

$$I_m \angle \phi = I$$



Phasor diagram for Inductor:-

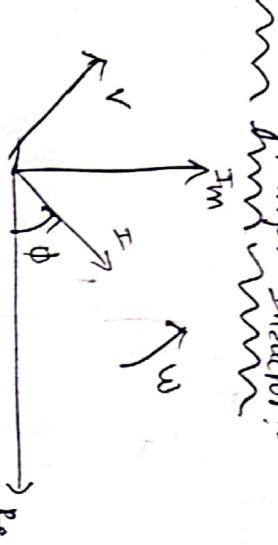

Voltage & current are 90° out of phase.

Current lags Voltage by 90° .

For capacitor:-


$$\text{Time Domain: } i = C \frac{dv}{dt} \quad \text{Frequency Domain: } I = j\omega C V$$

assume the voltage across it is $v = V_m \cos(\omega t + \phi)$

current through the capacitor is

$$i = C \frac{dv}{dt}$$
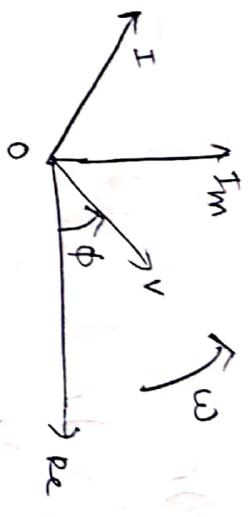
$$I = j\omega C V \Rightarrow V = \frac{I}{j\omega C}$$



Current & voltage are 90° out of phase.

Current leads the voltage by 90° .

Summary of voltage current relationships.

Element	Time Domain	Frequency Domain
R	$v = R i$	$V = R I$

$$v = R i$$

$$V = R I$$

$$v = L \frac{di}{dt}$$

$$V = j\omega L I$$

$$C$$

$$i = C \frac{dv}{dt}$$

$$V = \frac{I}{j\omega C}$$

Problem:-

The voltage $V = 12 \cos(60t + 45^\circ)$ is applied to a $0.1H$

Inductor. Find the steady state current through the
inductor.

Soln

$$V = j\omega L I$$

$$\omega = 60 \text{ rad/s}$$

$$V = 12 \angle 45^\circ \text{ V}$$

$$I = \frac{V}{j\omega L} = \frac{12 \angle 45^\circ}{j60 \times 0.1} = \frac{12 \angle 45^\circ}{6 \angle 90^\circ}$$

$$I = 30 \cos(100t + 60^\circ) \text{ mA}$$

$$I = V / j\omega C$$

$$= 6 \angle -30^\circ \times j100 \times 50 \times 10^{-6}$$

Impedance & Admittance of Passive Elements:-

Element

Impedance

Admittance

R

$$Z = R$$

$$Y = 1/R$$

L

$$Z = j\omega L$$

$$Y = 1/j\omega L$$


C

$$Z = 1/j\omega C$$

$$Y = j\omega C$$

If voltage $V = 6 \cos(100t - 30^\circ)$ is applied to a $50\mu F$ capacitor, calculate the current through it.

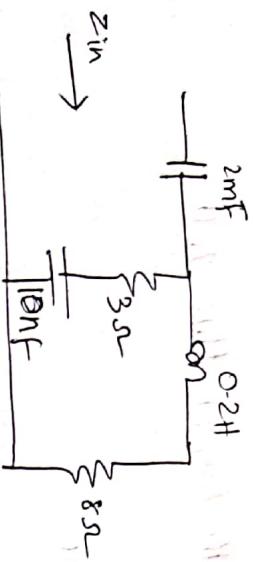Find the input impedance of the circuit operates at $\omega = 50\text{rad/s}$



$$Z_1 = \frac{1}{j\omega C} = \frac{1}{j50 \times 2 \times 10^{-3}} = -j10\Omega$$

$$Z_2 = 3 + \frac{1}{j\omega C} = 3 + \frac{1}{j50 \times 2 \times 10^{-3}} = (3-j10)\Omega$$

$$Z_3 = 8 + j\omega L = 8 + j50 \times 0.2 = (8+j10)\Omega$$

$$Z_1 + (Z_2 || Z_3)$$


$$Z_1 = 20 + \frac{1}{j\omega C} = 20 + \frac{1}{j10 \times 2 \times 10^{-3}} = 20 - 50j$$

$$Z_2 = 50 + j\omega L = 50 + j \times 10 \times 2 = 50 + 20j$$

$$\begin{aligned} Z &= Z_1 + Z_2 \parallel Z_3 \\ &= -j10 + \frac{(3-j10)(8+j10)}{11+j8} \end{aligned}$$

$$Z_{in} = 3.22 - j11.07 \Omega$$

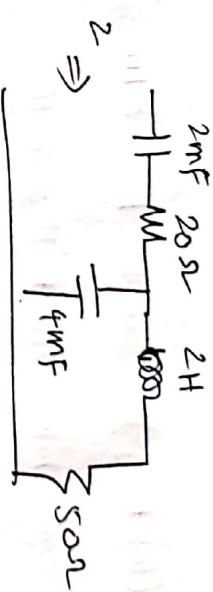Determine the input impedance of the circuit at $\omega = 10\text{rad/s}$



$$Z = 32.38 - j73.76\Omega$$

$$Z_1 = \frac{1}{j\omega C} = \frac{1}{j10 \times 2 \times 10^{-3}} = -j10\Omega$$

$$Z_2 = 20 + \frac{1}{j\omega C} = 20 + \frac{1}{j10 \times 2 \times 10^{-3}} = 20 - 50j$$


$$Z_3 = 50 + j\omega L = 50 + j \times 10 \times 2 = 50 + 20j$$

$$Z_1 + (Z_2 || Z_3)$$

$$\begin{aligned} Z &= Z_1 + Z_2 \parallel Z_3 \\ &= \frac{(20-50j) + (-25j)(50+20j)}{(-25j) + 50 + 20j} = \frac{1346.29 - 68.19j}{50.24 - 5.71j} \end{aligned}$$

$$Z = 32.23 - j73.83 \Omega$$

Determine $v_o(t)$ in the circuit.


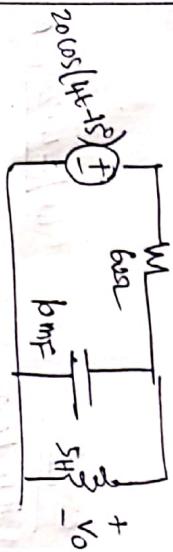


$$v_s = 20 \cos(4t - 15^\circ) = 20 \angle -15^\circ V$$

$$\omega = 4$$

$$j\omega f = \frac{1}{j\omega c} = \frac{1}{j4 \times 10 \times 10^{-3}} = -j25 \Omega$$
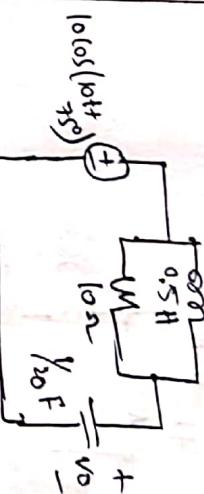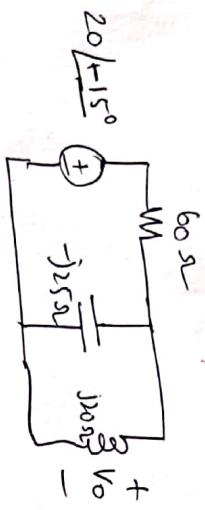
$$5H = j\omega L = j4 \times 5 = j20 \Omega$$



$$v_s = 10 \angle -15^\circ V$$

$$\omega = 10 \text{ rad/sec}$$

$$z_1 = (0.5H \parallel 10\Omega) \quad z_2 = (1/20 \Omega)$$

$$0.5H \Rightarrow j\omega L = j10 \times 0.5 =$$

$$z_1 = j\omega L = j10 \times 0.5 = 5j$$

$$z_2 = 10\Omega$$

$$z_3 = 1/j\omega c = 1/j10 \times 1/20 = 1/6.5j = -2j$$

$$Z = (z_1 \parallel z_2) + z_3$$

$$(5j \parallel 10) + (-2j)$$

$$z_{in} = 2 + j2 \Omega$$


$$2 + j4 - 2j$$

$$V_o = \frac{Z_2}{Z_1 + Z_2} \quad v_s = \frac{j100}{6.0 + 100j} (20 \angle -15^\circ)$$

$$= (0.8575 \angle 30.96^\circ)(20 \angle -15^\circ) = 17.15 \angle 15.96^\circ V$$

$$\boxed{\text{Time domain} \Rightarrow v_o(t) = 17.15 \cos(4t + 15.96^\circ) V}$$

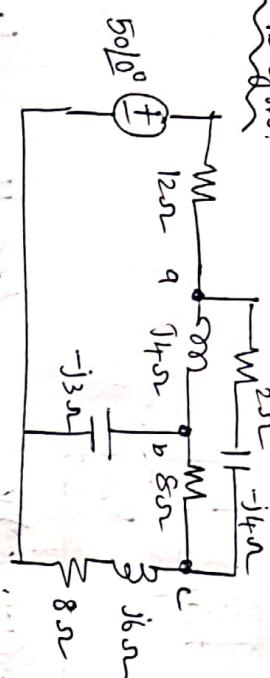Find the current 'I' in the circuit
using mesh analysis.



Delta network, connected to nodes a,b,c can be converted to the Y network

$$Z_{an} = \frac{j_4(2-j_4)}{j_4+2-j_4+j_8} = \frac{4(4+j_2)}{10} = (1.6 + j0.8) \Omega$$

$$Z_{bn} = \frac{j_4(j_8)}{10} = j3.2 \Omega$$


$$Z_{cn} = \frac{8(2-j_4)}{10} = (1.6 - j3.2) \Omega$$

The total impedance at the source terminals is


$$\begin{aligned} Z &= 1.6 + Z_{an} + (Z_{bn} - j1.6) \parallel (Z_{cn} + j6 + j8) \\ &= 1.6 + 1.6 + j0.8 + (j0.2) \parallel (9.6 + j2.8) \\ &= 1.6 + j0.8 + j0.2 \parallel (9.6 + j2.8) \end{aligned}$$

The desired current I is
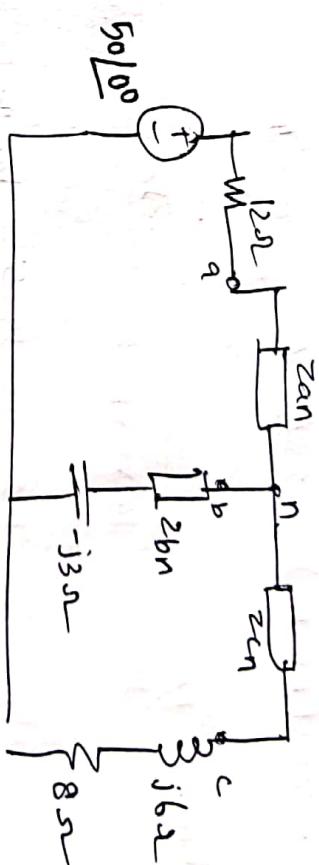
$$I = \frac{V_s}{Z} = \frac{50\angle 0^\circ}{13.64 \angle 42.04^\circ} = 3.666 \angle -42.04^\circ A$$



Mesh Analysis:

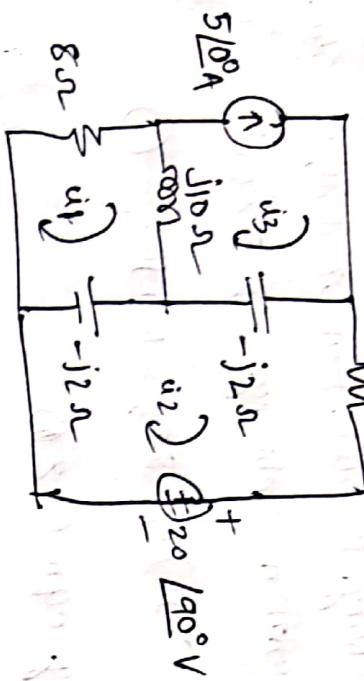

$$\text{KVL @ loop 1: } (8 + j10 - j2)I_1 - (-j2)I_2 - j10I_3 = 0 \quad \text{--- (1)}$$

$$\text{KVL @ loop 2: } (4 - j2 - j2)I_2 - (-j2)I_1 - (-j2)I_3 + 20\angle 90^\circ = 0 \quad \text{--- (2)}$$

form loop 3

$$I_3 = 5\angle 0^\circ - \text{①} \text{ sub this in ② & ③}$$

$$(8 + j8)I_1 + j2I_2 = j50 - \text{--- (4)}$$

$$j2I_1 + (4 - j4)I_2 = -j20 - j10 \text{ --- (5)}$$


$$= 32(1+j)(1-j) + 4 = 68$$

$$\Delta_2 = \begin{bmatrix} 8 + j8 & j50 \\ j2 & -j30 \end{bmatrix} = 340 - j240 = 416.17 \angle -35.22^\circ$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{416.17 \angle -35.22^\circ}{68} = 6.12 \angle -35.22^\circ$$

$$I_0 = -I_2 = 6.12 \angle 144.78^\circ \text{ A}$$

Q) Solve for V_o in the fig.

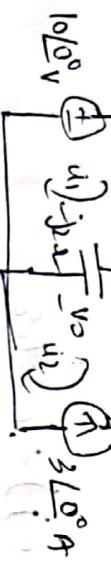

for loop 1

$$-10 + (8 - j2)I_1 - (-j2)I_2 - 8I_3 = 0$$

$$(8 - j2)I_1 + j2I_2 - 8I_3 = 10 \quad \text{--- (1)}$$

$$I_2 = -3 \quad \text{--- (2)}$$

for loop 2

$$(8 - j2)I_1 + j2I_2 - 8I_3 = 10 \quad \text{--- (1)}$$

$$I_2 = -3 \quad \text{--- (2)}$$

from loop 3 & 4

$$I_4 = I_3 + I_2 \quad \text{--- (4)}$$

$$\begin{aligned} \text{Voltage } V_o &= -j2(I_1 - I_2) = -j2(3.618 \angle 274.5^\circ + 3) \\ &= -7.213 \angle 4 - j6.56 \angle 56^\circ = 9.756 \angle 222.32^\circ \end{aligned}$$

Instead of solving the above four equations, we reduce them to two by elimination combining eqn ① & ②

$$(8 - j2)I_1 - 8I_3 = 10 + j6 \quad \text{--- (5)}$$

by combining eqn ③ & ④

$$-8I_1 + (14 + j)I_3 = -24 + j35 \quad \text{--- (6)}$$


$$\Delta = \begin{vmatrix} 8 - j2 & 8 & 8 \\ -8 & 14 + j & 8 \\ -8 & 14 + j & 8 \end{vmatrix} = \begin{bmatrix} 10 + j6 \\ -24 - j35 \end{bmatrix}$$

$$\Delta_1 = \begin{vmatrix} 10 + j6 & 8 & 8 \\ -24 - j35 & 14 + j & 8 \\ -8 & 14 + j & 8 \end{vmatrix} = 140 + j10 + j84 - 6 - 192 - j280$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{-58 - j166}{50 - j20} = 3.618 \angle 274.5^\circ \text{ A}$$

Applying KCL at node 1
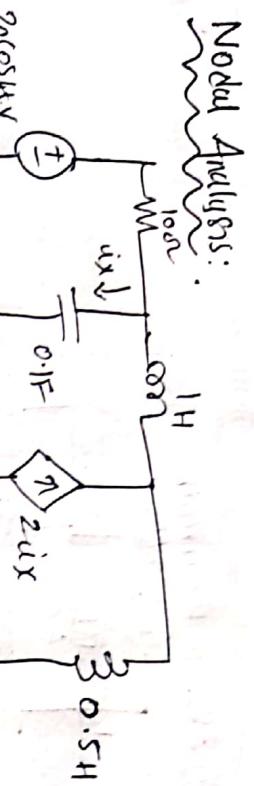
$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$



First convert to freq. domain.


$$20\cos 4t = 20\angle 0^\circ, \omega = 4\pi rad/s.$$

$$1H \Rightarrow j\omega L = j4$$

$$0.5H \Rightarrow j\omega L = j2$$

$$0.1F = 1/j\omega C = -j2.5$$

freq. Domain Equivalent circuit.

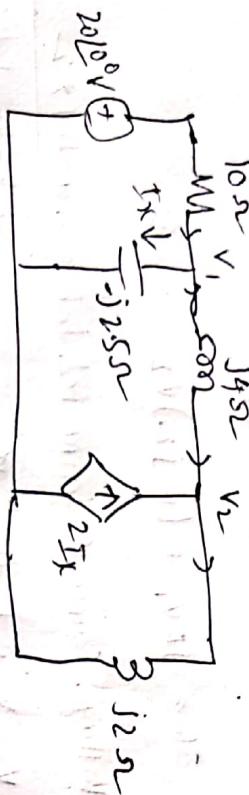

At node 2

$$2ix + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

$$\text{But } ix = V_1 / -j2.5$$

$$\frac{2V_1}{-j2.5} + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

Simplifying we get

$$11V_1 + 15V_2 = 0 \dots \textcircled{1}$$

$$\begin{bmatrix} 1+j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

$$A = \begin{bmatrix} 1+j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} = 15-j5$$

$$\Delta_1 = \begin{vmatrix} 20 & j2.5 \\ 0 & 15 \end{vmatrix} = 300, \quad \Delta_2 = \begin{vmatrix} 1+j1.5 & 0 \\ 11 & 0 \end{vmatrix} = -220$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{300}{15-j5} = 18.97 \angle 18.43^\circ V$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-220}{15-j5} = 13.91 \angle 198.3^\circ V$$


The current I_x is given by

$$I_x = \frac{V_1}{j2.5} = \frac{18.97 \angle 18.43^\circ}{2.5 \angle -90^\circ} =$$

$$= 7.59 \angle 108.4^\circ A$$

$$i_x = 7.59 \cos(4t + 108.4^\circ) A$$

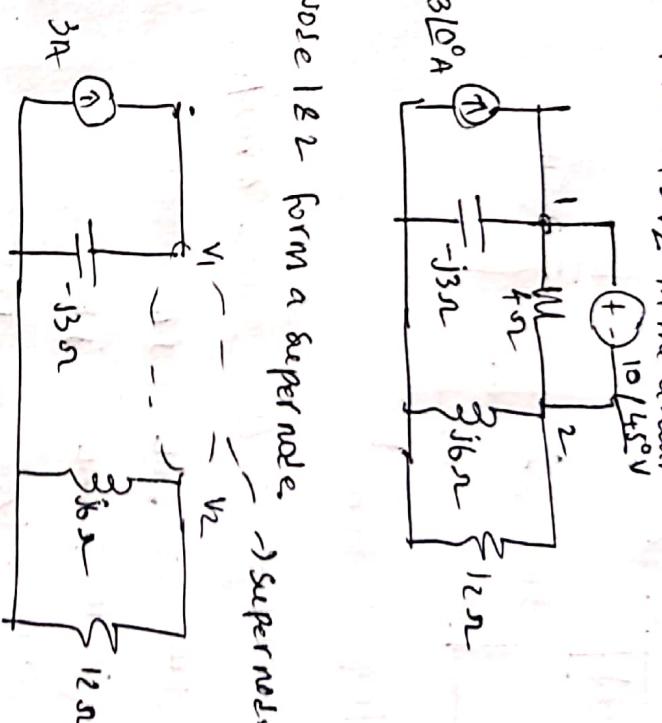Note 1 & 2 form a supernode \rightarrow supernode



Applying KCL

$$3A = \frac{V_1}{-j3} + \frac{V_2}{j6} + \frac{V_2}{12}$$

$$3A = j4V_1 + (1-j2)V_2 \quad \text{--- (1)}$$

But a voltage source is connected between nodes 1 & 2

$$\text{So } V_1 = V_2 + 10 \angle 45^\circ \quad \text{--- (2)}$$

Solve (2) in (1)

$$3A = j4(V_2 + 10 \angle 45^\circ) + (1-j2)V_2 \quad | \quad V_2 = 31.41 \angle 87.18^\circ V$$

From (1)

$$V_1 = V_2 + 10 \angle 45^\circ = 25.98 \angle 70.45^\circ$$

CHENNAI INSTITUTE OF TECHNOLOGY

Instantaneous power & Average power:-

Instantaneous power = Instantaneous voltage \times instantaneous current

$$P(t) = v(t)i(t)$$

The instantaneous power (watts) is the power at any instant of time.

Let

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$V_m \& I_m \Rightarrow \text{are the amplitudes}$$

θ_v & $\theta_i \Rightarrow$ phase angle of voltage & current respectively.

$$P(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$\cos A \cos B = \frac{1}{2} [\cos(A-B) + \cos(A+B)]$$

$$P(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m (\cos(2\omega t + \theta_v + \theta_i))$$

constant or time dependent

Sinusoidal fn

$P(t)$ can be positive or negative

If $P(t) = \text{positive} \Rightarrow$ Power is absorbed by the circuit

If $P(t) = \text{negative} \Rightarrow$ Power is delivered by the source.

Average power

Average power in watts, is the average of the instantaneous power over one period.

$$P = \frac{1}{T} \int_0^T P(t) dt \quad \dots \dots \textcircled{2}$$

Sys (2) in (1)

$$P = \frac{1}{T} \int_{\frac{T}{2}}^{\frac{1}{2}} V_m I_m \cos(\theta_v - \theta_i) dt$$

$$+ \frac{1}{T} \int_{\frac{1}{2}}^T V_m I_m \cos(2wt + \theta_v + \theta_i) dt$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \frac{1}{T} \int_0^T dt$$

$$+ \frac{1}{2} V_m I_m \frac{1}{T} \int_0^T \cos(2wt + \theta_v + \theta_i) dt$$

constant

Sinusoid

first integrand is constant, second is sine form.

Average of a sinusoid over a period is zero.

So Average power is

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Since $\cos(\theta_v - \theta_i) = \cos(\theta_i - \theta_v) \Rightarrow$ difference in
the phases of the voltage & current.

$P(t) = \text{time varying}$

$P = \text{does not depend on time}$

for instantaneous power we must know $v(t) & i(t)$
(time varying)

But average power can be calculated in when the voltage & current are expressed in steady state domain or frequency domain

Eg. $v(t) = V_m \underline{\cos \theta_v}$

$i(t) = I_m \underline{\cos \theta_i}$

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} V_m I_m \underline{\cos(\theta_v - \theta_i)}$$

$$= \frac{1}{2} V_m I_m [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

Read part of this equation in average power.

$$P = \frac{1}{2} \operatorname{Re}[V I^*]$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

when $\theta_v = \theta_i = 0^\circ$

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R = \frac{1}{2} |I|^2 R$$

(Shows the circuit is purely resistive)

when $\theta_v - \theta_i = 90^\circ$

$$P = \frac{1}{2} V_m I_m \cos 90^\circ = 0$$

Shows that the circuit is purely reactive.

Circuit absorbs no average power

A resistive load (R) absorbs power at all times,
while a reactive load (L or C) absorbs zero average power

~~A reactive load (L) absorbs power at all times,
while a reactive load (C) absorbs zero average power~~

① Problem

Given that $v(t) = 120 \cos(377t + 45^\circ)V$
 $i(t) = 10 \cos(377t - 10^\circ)A$

Find the instantaneous power & average power absorbed by the passive linear ntk.

Instantaneous power

$$P = Vi = 1200 \cos(377t + 45^\circ) \cos(377t - 10^\circ)$$

$$P(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

~~phasor B = phasor A + phasor C~~

$$= 600 [\cos(754t + 35^\circ) + \cos(754t - 55^\circ)]$$

$$P(t) = 344.2 + 600 \cos(754t + 135^\circ)W$$

Average power P_{avg}

$$\begin{aligned} P &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} (120) 10 \cos(45^\circ - (-10^\circ)) \\ &= 600 \cos 55^\circ = 344.2 W \end{aligned}$$

(2) Calculate the instantaneous power & average power absorbed by the passive component.

$$V(t) = 80 \cos(10t + 20^\circ) V$$

$$i(t) = 15 \sin(10t + 60^\circ) A$$

$i(t)$ can be written as

$$i(t) = 15 \cos(10t + 60^\circ - 90^\circ) A$$

$$i(t) = 15 \cos(10t - 30^\circ) A$$

$$\begin{aligned} v(t) &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v - \theta_i) \\ &= \frac{1}{2} \cdot 80 \cdot 15 \cos(20 - (-30)) \\ &= 600 \cos(50^\circ) \end{aligned}$$

$$\boxed{P_{avg} = 385.7 W}$$

(3) Calculate the average power absorbed by an impedance $Z = 30 + j70 \Omega$ when a voltage $V = 120 \angle 0^\circ$ is applied across it.

$$= \frac{1}{2} 80 \times 15 \cos(20 - (-30)) + \frac{1}{2} 80 \times 15 \cos(2 \times 10t + 20 - 30)$$

$$= 600 \cos(50^\circ) + 600 \cos(20t + 10^\circ)$$

$$\boxed{P(t) = 385.7 + 600 \cos(20t + 10^\circ) W}$$

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \cdot 80 \cdot 15 \cos(20 - (-30))$$

$$= 600 \cos(50^\circ)$$

$$I = \frac{V}{Z} = \frac{120 \angle 0^\circ}{30 - j70} = \frac{120 \angle 0^\circ}{76.16 \angle -66.8^\circ} = 1.596 \angle 66.8^\circ A$$

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} (120)(1.596) \cos(0 - 66.8^\circ)$$

$$\boxed{P_{avg} = 37.24 W}$$

(4) A current $I = 10L^{30^\circ}$ flows through an impedance

$Z = 20L^{-22^\circ}\Omega$, find the average power delivered to the impedance.

$$V = I \cdot Z = 10L^{30^\circ} \times 20L^{-22^\circ}$$

$$V = 100\sqrt{2} 200L^{8^\circ} V$$


$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_r - \theta_i)$$

$$= \frac{1}{2} \times 200 \times 10 \cos(8 - 30^\circ)$$

$$= 1000 \cos(-22^\circ)$$

$$\boxed{P_{avg} = 927.2 W}$$

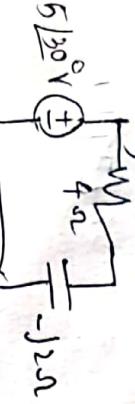- (5) Find the avg. power supplied by the source & the avg power absorbed by the resistor



$$I = \frac{5L^{30^\circ}}{4 - j2} = \frac{5L^{30^\circ}}{4.472L^{-26.57^\circ}}$$

$$P_{avg} = \frac{1}{2}(5)(1.118) \cos(30^\circ - 56.57^\circ) = 2.5W$$

Current through resistor is

$$I_R = I = 1.118L^{56.57^\circ} A$$

$$V_R = 4I_R = 4.472L^{56.57^\circ} V$$

Power absorbed by resistor is

$$P = \frac{1}{2}(4.472)(1.118) = 2.5W$$


(since phase diff b/w voltage & current is zero)

$$(\theta_r - \theta_i = 0)$$

Which is the same as the average power delivered by

The zero average power is absorbed by the capacitor.

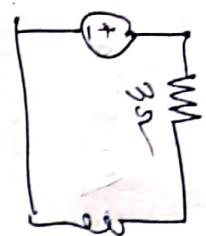Calculate the power (avg) absorbed by the resistor & inductor. Find the avg power supplied by voltage source.



$$I = \frac{8\angle 45^\circ V}{3 + j1} = \frac{8\angle 45^\circ}{3.16 \angle 18.43^\circ} = 2.56 \angle 26.57^\circ A$$

Power by Supply

$$P_{avg} = \frac{1}{2} \times 8 \times 2.53 \cos(45^\circ - 26.57^\circ)$$

$$P_{avg(\text{avg})} = 9.6W$$

Current through Resistor

$$I = \frac{8\angle 45^\circ}{3 + j1} = 2.56 \angle 45^\circ A$$

$$V = (2.56 \angle 45^\circ) \times 3 = 7.68 \angle 45^\circ V$$

$$P_{avg(\text{res})} = \frac{1}{2} \times 8 \times 2.53 \cos(45^\circ - 45^\circ)$$

Current through resistor. $I = 2.53 \angle 26.57^\circ A$


$$\text{Voltage across resistor } (2.53 \angle 26.57^\circ \times 3) = 7.59 \angle 26.57^\circ$$

$$\text{Power in Resistor} = \frac{1}{2} \times 8 \times 9.59 \times 2.53 \cos(26.57 - 26.57) = \frac{1}{2} \times 9.59 \times 2.53$$

$$P_{avg \text{ res.}} = 9.6W$$

Power in Inductor is zero.

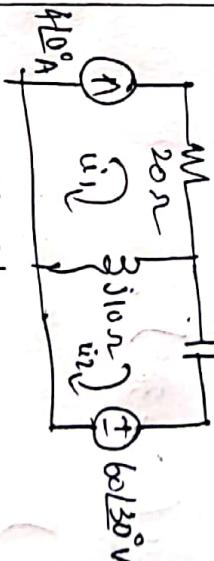③ Determine the average power generated by each source and the power absorbed by each passive elements of the circuit.



$$\text{apply mesh 1: } 10\angle 30^\circ - 20I_1 - 3\angle 10^\circ = 4A$$

from mesh loop 2

$$(j10 - j5)I_2 - j10I_1 + 60\angle 30^\circ = 0, \\ j5I_2 = -60\angle 30^\circ + j40 \Rightarrow I_2 = -12\angle -60^\circ + 8 = 10.58 \angle 79.1^\circ A$$

for the voltage source, the current flowing from it is I_2

$$I_2 = 10.58 \angle 29.1^\circ A$$

& voltage is $60 \angle 30^\circ V$ so avg power is

$$P_S = \frac{1}{2} (60) (10.58) \cos(30^\circ - 29.1^\circ) =$$

$$= \underline{207.8W}$$

thus avg power is absorbed by the source, in view

of the direction of I_2 & polarity of the voltage source

the CR is delivering average power to the voltage source.

for the current source: $I_1 = 4 \angle 0^\circ$.

$$V_1 = 20 I_1 + j10(I_1 - I_2) = 80 + j10(4 - 2 - j10.39)$$

$$= 183.9 + j20.$$

$$= 184.984 \angle 6.21^\circ V$$

The avg power supplied by the current source is
 $P = -\frac{1}{2} (184.984) (4) \cos(6.21^\circ - 0) = \underline{-367.8W}$

Negative sign indicates the current source is supplying power to the circuit.

For the resistor the current through it is $I_1 = 4 \angle 0^\circ$

Voltage across it is $20 I_1 = 80 \angle 0^\circ$;

$$P_R = \frac{1}{2} (80)(4) = \underline{160W}$$

For the capacitor, the current through it is $I_2 = 10.58 \angle 29.1^\circ$

& the voltage across it is $-j5 I_2 = (5 \angle -90^\circ) (10.58 \angle 29.1^\circ)$

$$= 52.9 \angle 29.1^\circ - 90^\circ.$$

Avg power absorbed by capacitor is

$$P_C = \frac{1}{2} (52.9) (10.58) \cos(-90^\circ) = 0$$

$$\text{Inductor current is } (I_1 - I_2) = 2 - j10.39 = 10.58 \angle -29.1^\circ$$

$$\text{Voltage across inductor } V_{L} = 10.58 \angle -91.1^\circ + 90^\circ$$

Hence the average power absorbed by the inductor is

$$P_3 = \frac{1}{2} (10.58)(10.58) \cos 40^\circ = 0$$

We see that the inductor & the capacitor absorb zero average power and that the total power supplied by the current source equals the power absorbed by the resistor & the voltage source or

$$P_1 + P_2 + P_3 + P_4 + P_5 = -36.85 + 160 + 0 + 0 + 20.5 = 0$$

indicating that power is conserved.

Effective or RMS value:

The effective value of a periodic current is the dc current that delivers the same average power to a resistor as the periodic current.

$$I_{\text{eff}} = I_{\text{rms}}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

Power factor is the cosine of the phase difference between voltage & current. It is also the ratio of the range of load

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

average power can be written in terms of rms values

$$P = I^2 R = \frac{V_{\text{rms}}^2}{R}$$

Apparent power & Power factor:-

Apparent power (in VA) is the product of the rms values of voltage and current.

$$\text{units (volt-Amp)}$$

Power factor:- Ratio of average apparent power to apparent power

$$\text{pf} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

$\theta_v - \theta_i$ = Power factor angle.

Q1

A Series-connected load draws a current $i(t) = 4\cos(\theta_v t + 10^\circ)$ when the applied voltage is $v(t) = 120 \cos(100\pi t - 20^\circ) V$, find the apparent power & the power factor of the load, determine the element values that form the series-connected load.

$$\text{Apparent power } S = V_{\text{rms}} I_{\text{rms}} \frac{120}{\sqrt{2}} \frac{4}{\sqrt{2}} = \underline{\underline{240 \text{ VA}}}$$

$$\text{Power factor } P_f = \cos(\theta_v - \theta_i) =$$

$$= \cos(-20 - 10) = 0.866 \text{ (leading)}$$

(Because current leads voltage)

$$Z = \frac{V}{I} = \frac{120 - 20^\circ}{4 \angle 10^\circ} = 25.98 - j15 \Omega$$

$$P_f = \cos(-30^\circ) = 0.866 \text{ (leading)}$$

Load impedance 'Z' can be modeled by a

25.98 Ω resistor in series with a capacitor

$$X_C = -15 = -1/\omega C$$

$$C = \frac{1}{15\omega} = \frac{1}{15 \times 100\pi} = 2.122 \mu F$$

Q2 Obtain power factor & the apparent power of a load whose impedance is $Z = 60 + j40 \Omega$ $V(t) = 150 \cos(337t + 10^\circ)$

Apparent power in terms:

$$I(t) = \frac{v(t)}{Z} = \frac{150 \angle 10^\circ}{60 + j40} = \frac{150 \angle 10^\circ}{72.11 \angle 33.69}$$

$$S = V_{\text{rms}} I_{\text{rms}} = \frac{150}{\sqrt{2}} \times \frac{2.08}{\sqrt{2}} = \underline{\underline{156 \text{ VA}}}$$

$$P_f = \cos(\theta_v - \theta_i) =$$

$$= \cos(10 + 23.69) = 0.832 \text{ (lagging)}$$

(Because current lags voltage)

Complex power: $\text{Im}(\text{VA})$

is the product of the rms voltage phasor and the complex conjugate of the rms current phasor. As a complex quantity its real part is real power ' P ' & its imaginary part is reactive power ' Q '.

$$\text{Complex power } S = S = P + jQ = \frac{1}{2} V I^*$$

$$= V_{\text{rms}} I_{\text{rms}} / \theta_V - \theta_I$$

$$\text{Apparent power } S = |S| = V_{\text{rms}} I_{\text{rms}} = \sqrt{P^2 + Q^2}$$

$$\text{Real power } P = \text{Re}(S) = S \cos(\theta_V - \theta_I)$$

$$\text{Reactive power } Q = \text{Im}(S) = S \sin(\theta_V - \theta_I)$$

$$\text{Power factor} = \frac{P}{S} = \cos(\theta_V - \theta_I)$$

Problem

- ① The voltage across a load $(V(t)) = 60 \cos(\omega t - 10^\circ) V$ and the current through the element in the direction of the voltage drop is $i(t) = 1.5 \cos(\omega t + 50^\circ) A$

Find (a) complex & apparent powers

- (b) Real & reactive power
(c) Power factor & the load impedance

$$V_{\text{rms}} = \frac{60}{\sqrt{2}} L^{-10^\circ} \quad I_{\text{rms}} = \frac{1.5}{\sqrt{2}} L^{50^\circ}$$

$$\text{Complex power} = V_{\text{rms}} I_{\text{rms}}^* \left(\frac{60}{\sqrt{2}} L^{-10^\circ} \right) \left(\frac{1.5}{\sqrt{2}} L^{50^\circ} \right)$$

$$\text{Complex power} = 45 L^{-60^\circ} \text{ VA}$$

$$\text{Apparent power } S = |S| = 45 \text{ VA}$$

(13)

(b) we can express the complex power in rectangular form

$$S = 45 \angle -60^\circ = 45 [\cos(-60) + j \sin(-60^\circ)]$$

$$= 22.5 - j38.97$$

Since $S = P+jQ$, the real power is

$$\boxed{\text{Real power } P = 22.5 \text{ W}}$$

while reactive power is

$$\boxed{Q = -38.97 \text{ VAR}}$$

Determine complex power, apparent power, real power, reactive power, power factor & load impedance.

Complex power

$$S = V_{\text{rms}} I_{\text{rms}}^*$$

$$S = \frac{110}{\sqrt{2}} \angle 85^\circ \times \frac{0.4}{\sqrt{2}} \angle -15^\circ$$

$$\boxed{S = 44 \angle 70^\circ \text{ VA}}$$

Apparent power:

$$\boxed{|S| = 44 \text{ VA}}$$

The power factor

$$P_f = \cos(-60^\circ) = 0.5 \text{ (leading)}$$

Real power

$$Z = \frac{V}{I} = \frac{60 \angle -10^\circ}{1.5 \angle 50^\circ} = 40 \angle -60^\circ \Omega$$

Complex power in rectangular form

$$15.04 + j41.3 \text{ W}$$

$$S = P+jQ$$

Real power $P = 15.04 \text{ W}$

Reactive power $Q = 41.3 \text{ VAR}$

Power factor

$$\text{Pf} = \cos(\theta_r - \theta_i) \quad \text{or} \quad \text{Pf} = \cos(\theta)$$

$$= \cos(85^\circ - 15^\circ)$$

$$= \cos(70^\circ)$$

$$\boxed{\text{Pf} = 0.342 \text{ lagging}}$$

Impedance.

$$Z = \frac{V}{I} = \frac{\sqrt{240 \times \sqrt{2}}}{12 \text{ kVA}} = \frac{110 \angle 45^\circ}{0.4 \angle 15^\circ}$$

$$= 275 \angle 70^\circ \Omega$$

$$\boxed{Z = 94.05 + j258.4 \Omega}$$

- ⑤ For constant $\text{losses} = 110 \text{ kVA}, \text{ time} = 0.4$
- ③ A load Z draws 12 kVA at a P.F. of 0.856 lagging from a 120V rms sinusoidal source. Calculate the average & reactive power delivered to the load,

- (b) Peak current and the load impedance.

Given that $\text{Pf} = \cos\theta = 0.856$, we obtain the power angle as $\theta = \cos^{-1} 0.856 = 31.13^\circ$

If apparent power is $S = 12,000 \text{ VA}$ the average or real power is

$$\boxed{P = S \cos\theta = 12000 \times 0.856 = 10.272 \text{ kW}}$$

where the Reactive power is

$$\boxed{Q = S \sin\theta = 12000 \times 0.517 = 6.204 \text{ kVA}}$$

- (b) Since the pf is lagging, the complex power is

$$\boxed{S = P + jQ = 10.272 + j6.204 \text{ kVA}}$$

$$V_{rms} = V_{rms} I_{rms}^*$$

$$\begin{aligned} I_{rms}^* &= \frac{S}{V_{rms}} = \frac{100}{\sqrt{10,272 + j6204}} \\ &= 85.6 + j51.7 A \\ &= \underline{\underline{100 \angle 31.13^\circ A}} \end{aligned}$$

Thus $I_{rms} = 100 \angle -31.13^\circ$ & its peak current is

$$I_m = \sqrt{2} I_{rms} = \sqrt{2} \times 100 = \underline{\underline{141.4 A}}$$

The load Impedance

$$Z = \frac{V_{rms}}{I_{rms}} = \frac{120 \angle 0^\circ}{\underline{\underline{100 \angle -31.13^\circ}}} = 1.2 \angle 31.13^\circ \Omega$$

which is an inductive Impedance.

UNIT-4

TRANSIENTS AND RESONANCE IN RLC CIRCUIT

Here We Will examine Two types of Simple Circuits:


- A Circuit Comprising a resistor and Capacitor
- and a Circuit Comprising a resistor and an Inductor.

These are called RC and RL.

The Source-free RC Circuit:

* A Source-free RC Circuit Occurs When its DC source is suddenly disconnected. The energy already stored in the capacitor is released to the resistors.

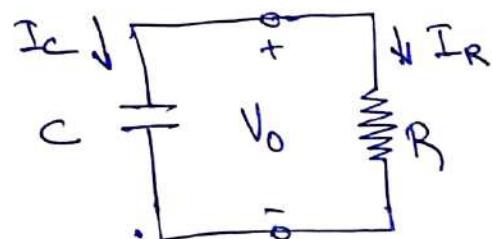- Consider a Series Combination of a resistor and an Initially Charged Capacitor.



→ Objective is to determine the Circuit response, assume to be the Voltage $V(t)$ across the capacitor.

Since capacitor initially charged, We can assume that at time $t=0$, the initial Voltage is,

$$V(0) = V_0, \quad \text{EnggTree.com}$$

then the corresponding value of energy stored

$$U(0) = \frac{1}{2} CV^2$$

Applying KCL at the node of the Circuit,

$$I_C + I_R = 0$$

We know that $I_C = C \frac{dV}{dt}$ and $I_R = \frac{V}{R}$

$$C \frac{dV}{dt} + \frac{V}{R} = 0$$

by rearranging

$$\frac{dV}{V} = -\frac{1}{RC} dt$$

Integrating both sides,

$$\ln V = -\frac{t}{RC} + \ln A$$

$$\boxed{\frac{dV}{V} = \ln A}$$

A \Rightarrow integration constant, thus,

$$\frac{\ln V}{\ln A} = -\frac{t}{RC}$$

Taking Powers of e produce

$$\boxed{e^{\frac{\ln V}{\ln A}} = e^{-t/RC}}$$


$$\frac{V}{A} = e^{-t/RC}$$

$$\therefore V(t) = A e^{-t/RC}$$

at initial condition $V(0) = A = V_0$

$$\boxed{V(t) = V_0 e^{-t/RC}}$$

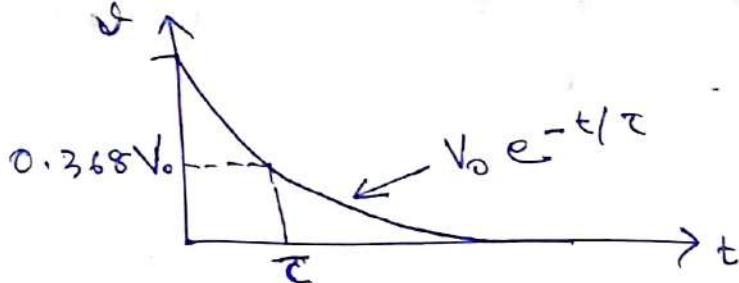This shows the voltage response of the RC circuit is an exponential decay of the initial voltage.



The Response is due to the initial energy stored due to physical characteristics of the circuit and not due to some external voltage or current source, it is called the natural response of the circuit.

From the graph, As t-increases the voltage decreases toward zero.

The rapidity with which the voltage decreases is expressed in terms of the time constant (τ).

that, $t = \tau$

then


$$V(t) = V_0 e^{-t/RC}$$

where $\tau = RC$

$$V(t) = V_0 e^{-t/\tau} = V_0 e^{-t/RC} = V_0 e^{-t/\tau} = 0.368V_0$$

In terms of time constant


$$V(t) = V_0 e^{-t/\tau}$$

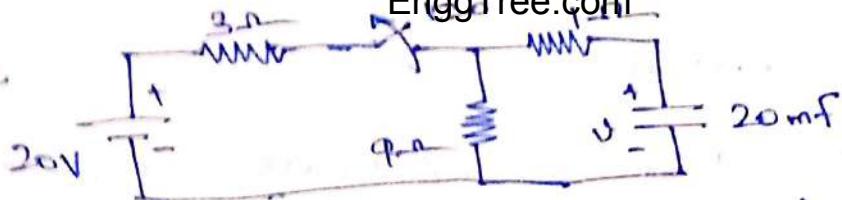

The switch in the circuit has been closed for a long time, and it's opened at $t=0$. Find $V_c(t)$ for $t \geq 0$. Calculate the initial energy stored in the capacitor.

Solution:

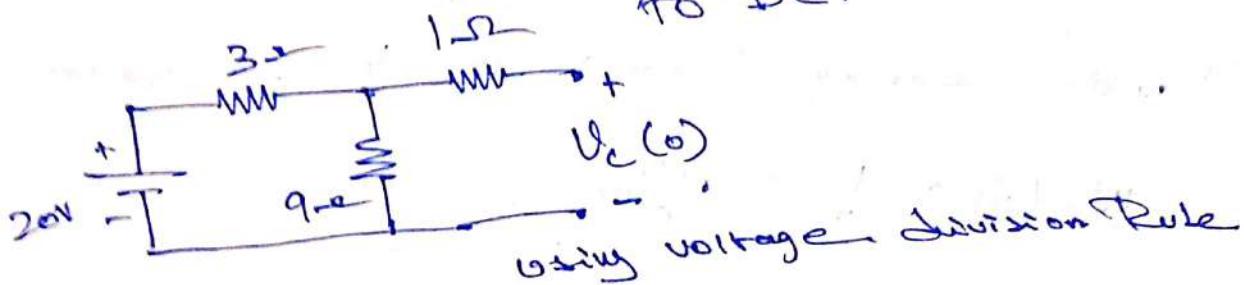for $t < 0 \rightarrow$ Switch Closed, the capacitor is on Open Circuit, AD DC.




$$V_c(0) = 20 \times \frac{9}{9+3} = 15 \text{ V} \quad t < 0$$

Voltage across a capacitor cannot change instantaneously, the voltage across the capacitor at $t=0^-$ is same at $t=0^+$.

$$V_c(0) = V_0 = 15 \text{ V}$$

for $t > 0$, the switch is opened;

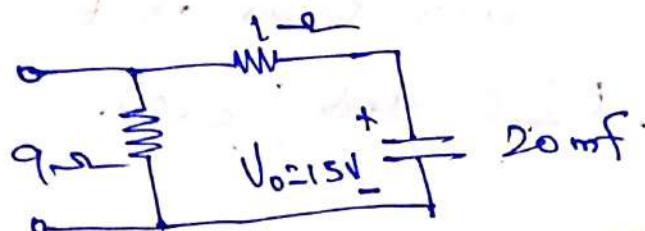

source free RC circuit.

$$Req = 1 + \frac{1}{9} = 10 \Omega$$

time constant,

$$\tau = R_0 C = 60 \times 20 \times 10^{-3} = 0.2 \text{ s}$$

The Voltage across the Capacitor

for $t \geq 0 \rightarrow$

$$V(t) = V_c(0) e^{-t/\tau}$$

$$= 15 e^{-t/0.2} \text{ V}$$


$V(t) = 15 e^{-5t} \text{ V}$

Initial energy stored in the Capacitor

$$W_c(0) = \frac{1}{2} C V_c^2(0)$$

$$= \frac{1}{2} \times 20 \times 10^{-3} \times 15^2$$


$W_c(0) = 2.25 \text{ J}$

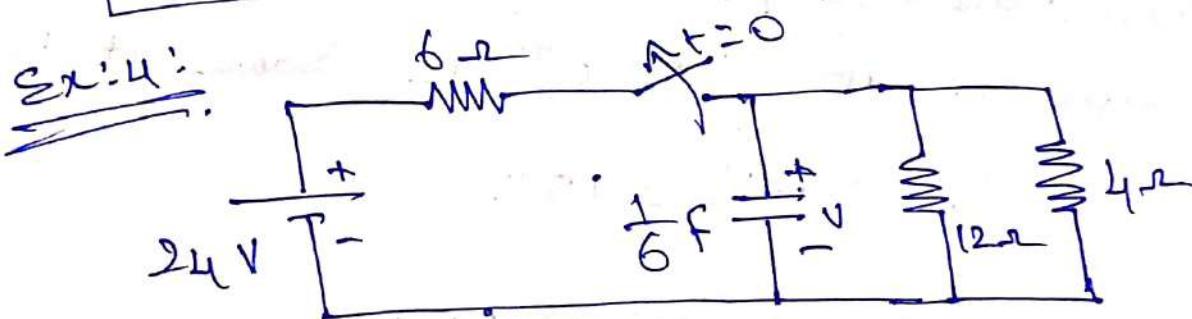

If the Switch Opens at $t=0$, find
 $V(t)$ for $t \geq 0$ and $W_c(0)$.

~~Solution:~~

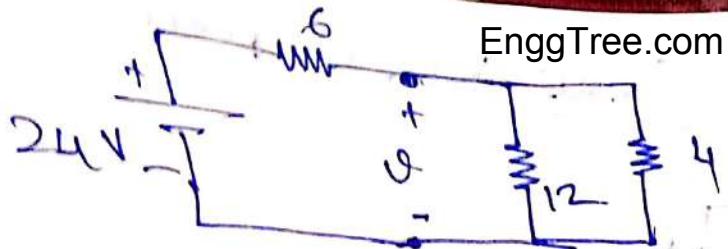for $t < 0 \rightarrow$ Switch Closed
Capacitor at Open Circuited.




$$\text{Circuit diagram: } 24V \xrightarrow{6\Omega} \parallel \xrightarrow{12\Omega} C \quad \Rightarrow \quad 24 \times \frac{3}{6+3} = 8V$$

$$U_C(t) = 8V \quad t < 0$$

for $t \geq 0$ Switch Opened

$$U_C(0) = V_0 = 8V$$

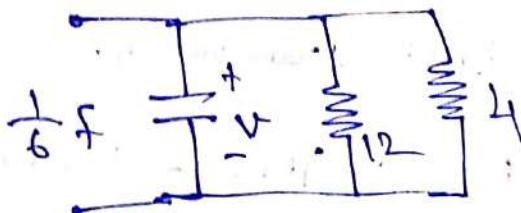

$$\frac{1}{6}f \quad \frac{1}{I} - v \quad \parallel \quad 3 \quad R_{eq} = 3$$

$$T = RC = 3 \times \frac{1}{6} = 0.5s$$


Voltage across capacitor, $t \geq 0$

$$V(t) = U_C(0) e^{-t/0.5}$$

$$V(t) = 8 e^{-2t}$$

$$W_C(0) = \frac{1}{2} C V_C^2(0) = \frac{1}{2} \times \frac{1}{6} \times 8^2 = 5.33 J$$

THE SOURCE IN R.L. CIRCUIT

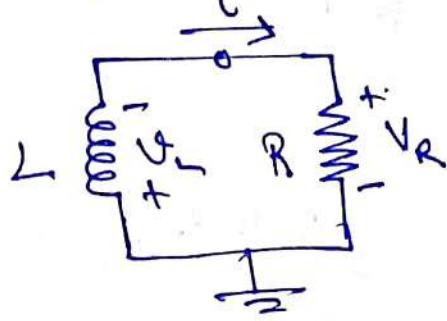

Our goal to determine the Circuit Response.

We select the Inductor Current as the response in order to take advantage of the idea that the Inductor Current cannot change instantaneously.

Assume at $t=0$ the Inductor has initial Current I_0 ,

$$i(0) = I_0$$

The Corresponding energy stored in the inductor,

$$W(0) = \frac{1}{2} L I_0^2$$

Apply KVL around the loop,

$$V_L + V_R = 0$$

but, $V_L = L \frac{di}{dt}$ if $V_R = iR$, then

$$L \frac{di}{dt} + Ri = 0$$

for simplification, divide by 'L'

$$\frac{di}{dt} + \frac{R}{L} i = 0$$

Rearranging terms and integrating gives

$$\int \frac{di}{i} = - \left(\frac{R}{L} dt \right)$$

$$\ln i \Big|_{I_0}^{i(t)} = - \left[\frac{Rt}{L} \right]_0^t$$


$$\ln i(t) - \ln I_0 = - \frac{Rt}{E} + C$$

$$\ln \frac{i(t)}{I_0} = - \frac{Rt}{L}$$

Taking e powers

$$i(t) = I_0 e^{-\frac{Rt}{L}}$$

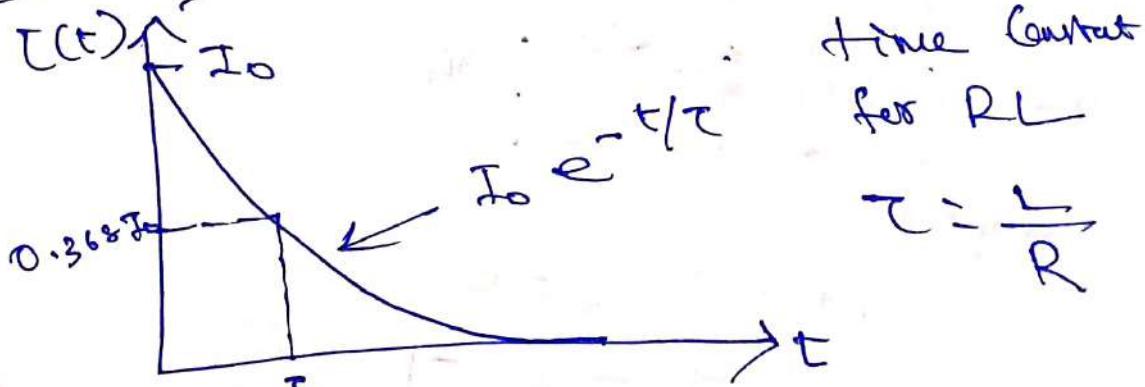This shows that the natural response of the RL circuit is an exponential decay of the initial current.



$$i(t) = I_0 e^{-t/\tau}$$

then we can find Voltage across
the resistor as

$$V_R(t) = iR = I_0 R e^{-t/\tau}$$


Power dissipate in the Resistor

$$P = V_R i = I_0^2 R e^{-2t/\tau}$$

$$\begin{aligned} &= I_0 R e^{-t/\tau} \times I_0 e^{-t/\tau} \\ &= I_0^2 R e^{-2t/\tau} \end{aligned}$$

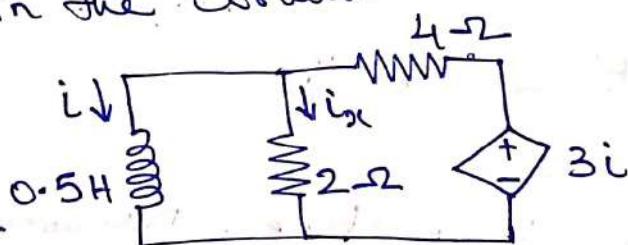
Problem:

Assuming that $i(0)=10A$, calculate $i(t)$ and $i_R(t)$ in the circuit.



Solution:

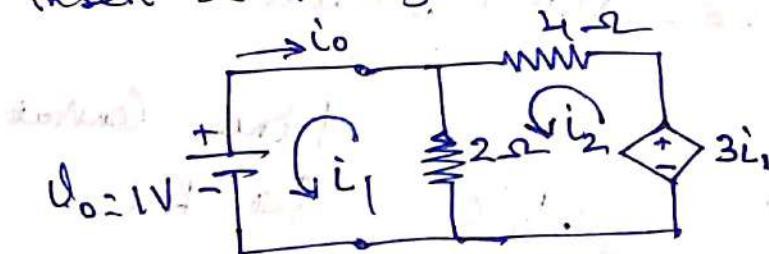Because of the dependent source, we insert a voltage source with $V_0=1V$,



Apply KVL

$$1 + 2(i_1 - i_2) = 0$$

$4i_2 + 2i_2 - 2i_1 - 3i_1 = 0$

$6i_2 - 5i_1 = 0 \quad \text{Eqn ①}$

$i_2 = \frac{5}{6}i_1$

Sub i_2 from eqn ①

~~$2i_1 - 2\left(\frac{5}{6}i_1\right) = -1$~~

~~$i_1 \left[2 - \frac{10}{6} \right] + 1 = 0$~~

~~$i_1 \left[\frac{2}{6} \right] + 1 = 0$~~

$2i_1 - 2i_2 = -1$

$-5i_1 + 6i_2 = 0$

$\Delta = \begin{vmatrix} 2 & -2 \\ -5 & 6 \end{vmatrix} = 12 - 10 = 2$

$\Delta_{i_1} = \begin{vmatrix} -1 & -2 \\ 0 & 6 \end{vmatrix} = -6$

$i_1 = \frac{\Delta_{i_1}}{\Delta} = \frac{-6}{2} = -3 \text{ A}$

$\therefore i_0 = -i_1 = -(-3) = \underline{\underline{3 \text{ A}}}$

$\therefore R_{eq} = R_{in} = \frac{V_0}{i_0} = \frac{1}{3} \Omega$

then the time constant is

$\tau = \frac{L}{R_{eq}} = \frac{0.5}{\frac{1}{3}} = 1.5 \text{ s}$

the current through the inductor is,

$i(t) = i(0) e^{-t/\tau} = 10 e^{-t/1.5} \text{ A} \quad t > 0$

Voltage across the inductor is

$v = L \frac{di}{dt} = 0.5 \frac{d}{dt} 10 e^{-t/1.5}$

$= (0.5)(10)\left(-\frac{1}{1.5}\right) e^{-t/1.5}$

$v = -3.33 e^{-t/1.5} \text{ V}$


Since inductor and resistor are in parallel,

Parallel,

$$i_{rc}(t) = \frac{v}{2} = -\frac{3.33 e^{-t/1.5}}{2} = -1.666 e^{-t/1.5} \text{ A}$$

Ex 2: find i and V_x in the circuit in


figure, Let $i(0) = 5 \text{ A}$

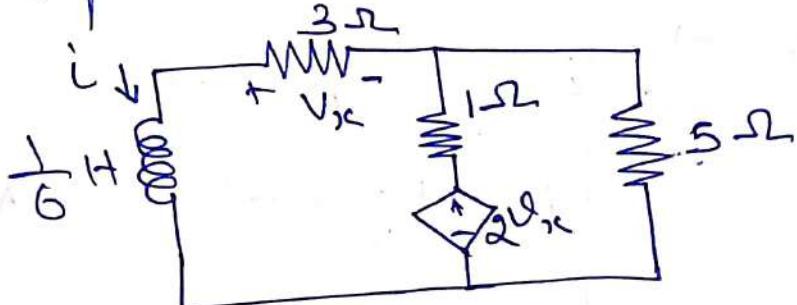

Solution: Given: $i(0) = 5$

Find: i and V_x

first find R_{eq} ,

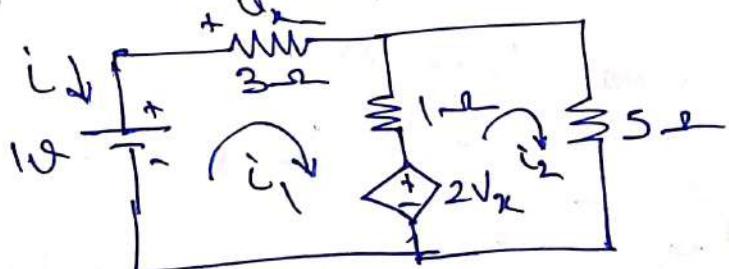

Apply KVL

$$-i + 3i_1 + 1(i_1 - i_2) + 2V_x = 0$$

$$4i_1 - i_2 + 2(3i_1) = -1$$

$$10i_1 - i_2 = +1 \quad \textcircled{1}$$

Loop 2

$$1[i_2 - i_1] + 5i_2 - 2V_x = 0$$

$$i_2 - i_1 + 5i_2 - 2(3i_1) = 0$$

$$6i_2 - 7i_1 = 0$$

$$-7i_1 + 6i_2 = 0$$

$$\Delta = \begin{vmatrix} 10 & -1 \\ -7 & 6 \end{vmatrix} = 60 - 7 = 53$$

$$\Delta_1 = \begin{vmatrix} +1 & -1 \\ 0 & 6 \end{vmatrix} = +6$$

$$i_1 = \frac{+6}{53} = +0.113$$

$$R_{eq} = R_m = \frac{V_o}{I_o} = \frac{1}{+0.113} = 8.8 \Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{1/6}{8.8} = 0.0189 \text{ s}$$

$$i(t) = i(0) e^{-t/\tau}$$


$$i(t) = 5 e^{-t/0.0189} = 5 e^{-53t} \text{ A}$$

$$V_x = 3 \times i(t)$$


$$= 3 \times [-5 e^{-53t}]$$

$$V_x = -15 e^{-53t} V$$

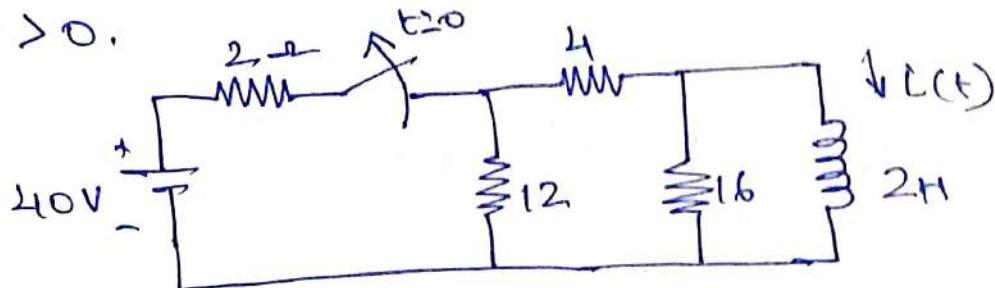Ex 3: The switch in the circuit has been closed for a long time. At $t=0$ the switch is opened. Calculate $i(t)$ for $t > 0$.



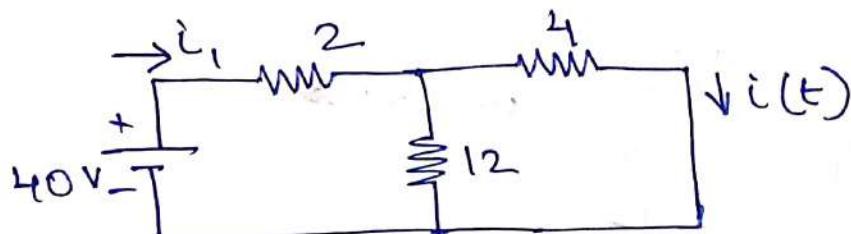Solution: at $t < 0 \rightarrow$ Switch closed,
Inductor acts as short circuit.
 $\rightarrow 16\Omega$ Resistor is short circuited.



$$i_1 = \frac{40}{5} = 8 \text{ A}$$

and $i(t)$ obtain by current division rule


$$i(t) = 8 \times \frac{12}{12+4} = 6 \text{ A} \quad t < 0$$

Since current through an inductor cannot change instantaneously.

$$i(0) = i(0^-) = 6 \text{ A} \quad \text{at } t=0$$

When $t > 0 \rightarrow$ Switch Opened,
Voltage source disconnected.

Source free RL circuit

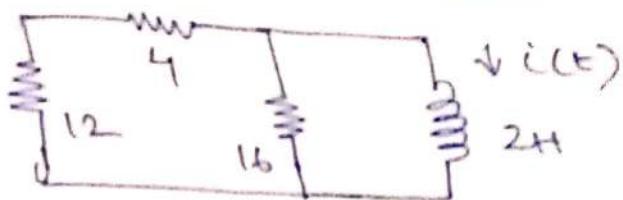

$$\text{Req} \Rightarrow \boxed{\begin{array}{c} 4 \\ \parallel \\ 16 \end{array}} \parallel 2H$$

$$= \frac{16 \times 16}{16 + 16} = 8 \Omega$$

∴ time Constant


$$\tau = \frac{L}{\text{Req}} = \frac{2}{8} = \frac{1}{4} \text{ s}$$

Thees

$$i(t) = i(0) e^{-t/\tau}$$


$$i(t) = 6 e^{-4t} \text{ A} \quad t \geq 0$$

Ex-4.

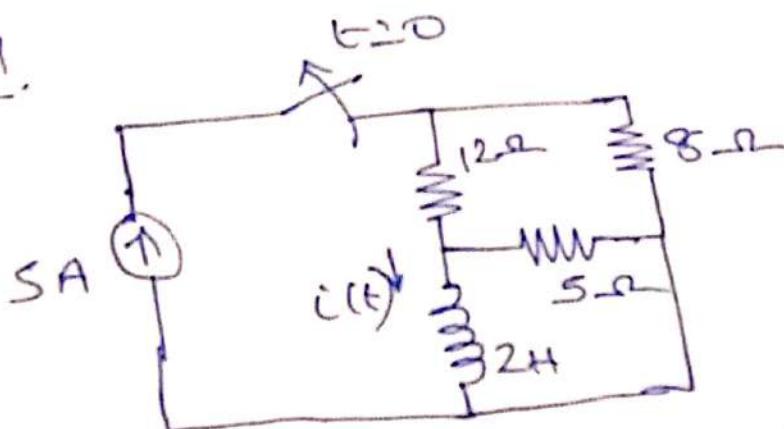


Ans: $i(t) = 2 e^{-2t} \text{ A}$

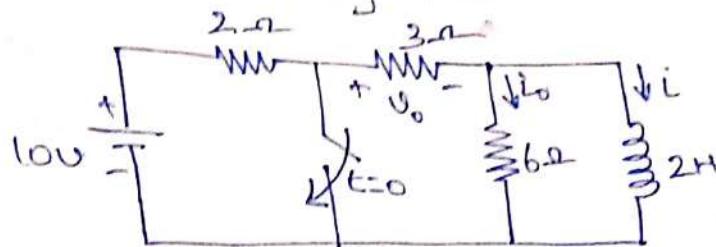Ex 7.5 In the circuit given, find i_0 , v_o + i for all time, assuming that the switch was open for a long time.



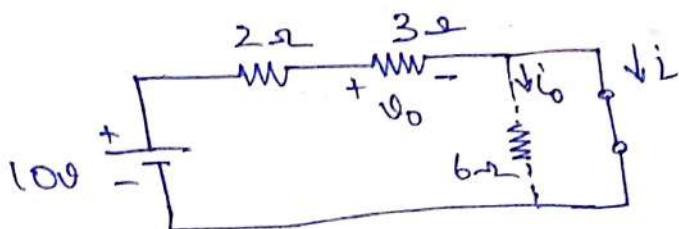Solution: \Rightarrow for $t < 0 \rightarrow$ Switch is open, then DC source connected to Inductor, so it behaves like short circuit.




$$i_0 = 0; t < 0$$

$$i = \frac{10}{3+2} = 2 \text{ A}; t < 0$$

$$v_o = i \times 3 = 2 \times 3 = 6 \text{ V}; t < 0$$

then $\underline{i(0)} = 2 \text{ A}$.

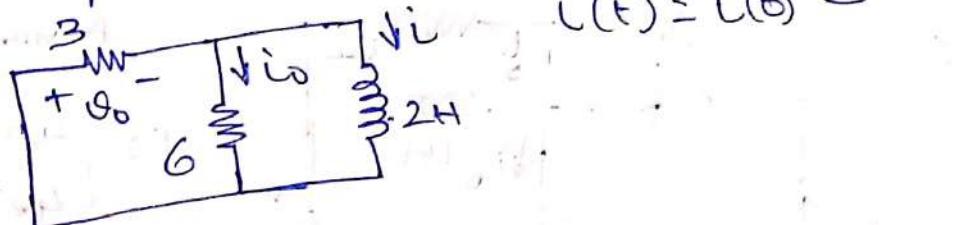\Rightarrow for $t > 0 \rightarrow$ Switch is closed, so that voltage source is short circuited



$$R_{eq} = \frac{3 \times 6}{3+6} = \frac{18}{9} = 2 \Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{2}{2} = 1 \text{ Sec}$$

$$i(t) = 2e^{-t} A$$

$$\therefore i(t) = \underline{2e^{-t} A} \text{ at } t \geq 0$$

Need to find i_0 i.e. current through 6Ω
resistor

by Current division Rule,

$$i_0 \text{ or } i_6 = (-2e^{-t}) \times \frac{3}{9} \quad \left[\begin{array}{l} \text{note:} \\ i(t) \text{ is reverse} \\ \text{direction when} \\ \text{current through is} \\ 6\Omega \end{array} \right]$$

$$i_0(t) = \underline{-\frac{2}{3} e^{-t} A} \quad \text{at } t \geq 0$$

$$V_o(t) = V_L = L \frac{di}{dt}$$


$$= 2 \times \frac{d(-2e^{-t})}{dt}$$

$$= 2 \times [-2(-1)e^{-t}]$$

$$= 2 \times 2e^{-t}$$

$$V_o(t) = \underline{4 e^{-t} V}$$

Ex:

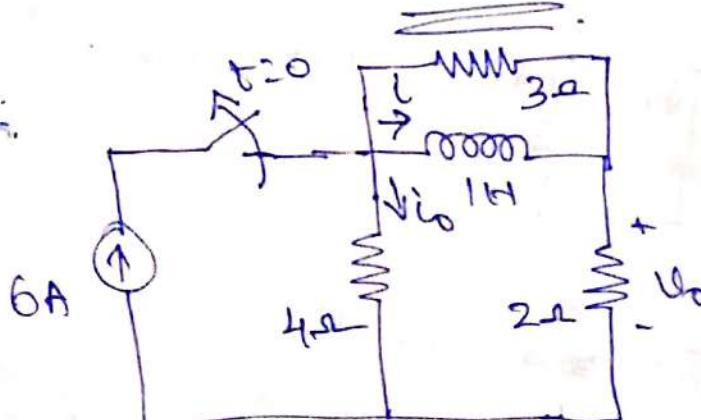

Answer

$$i = \begin{cases} 4A & t < 0 \\ 4e^{-2t} A & t \geq 0 \end{cases}$$


$$V_o = \begin{cases} 4V & t < 0 \\ -\frac{8}{3}e^{-2t} V & t \geq 0 \end{cases}$$

$$(62) \begin{cases} 2A & t < 0 \\ -4/3e^{-2t} A & t \geq 0 \end{cases}$$

UNIT STEP function:

The Unit Step function $u(t)$ is '0' for Negative values of 't' and '1' for positive value of 't'.

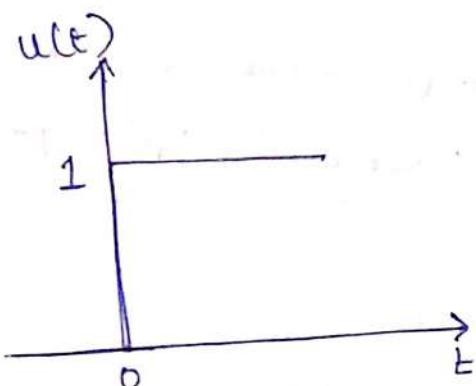
i.e., $u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$



The Unit Step function is undefined at $t=0$, where it changes abruptly from 0 to 1.

→ If the abrupt changes occurs at $t=t_0$, then the Unit Step function becomes,
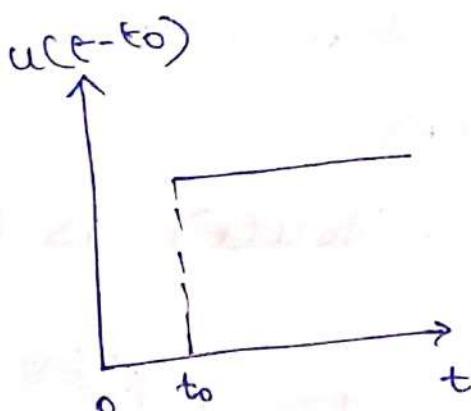
$$u(t-t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$




that $u(t)$ delayed by t_0 seconds.

→ If the change is at $t=-t_0$, the Unit Step function becomes,

EnggTree.com

$$u(t+t_0) = \begin{cases} 0, & t < -t_0 \\ 1, & t > -t_0 \end{cases}$$

i.e $u(t)$ is advanced by t_0 seconds.

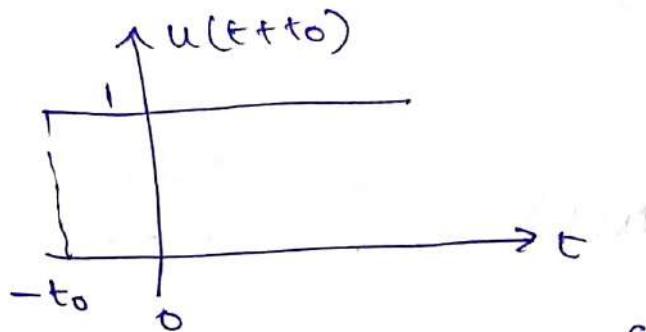

We use the Step function to represent an abrupt change in Voltage or Current.

Examp, Step Voltage,

$$V(t) = \begin{cases} 0 ; & t < t_0 \\ 1 , & t > t_0 \end{cases}$$



it expressed in terms of Unit Step function as,

$$V(t) = V_0 u(t-t_0)$$

If $t_0 = 0$, then, Step Voltage,


$$V(t) = V_0 u(t).$$

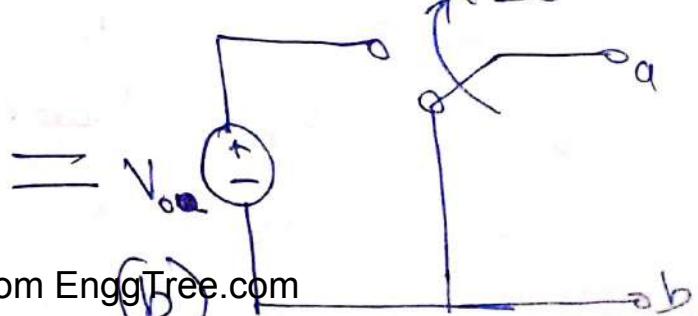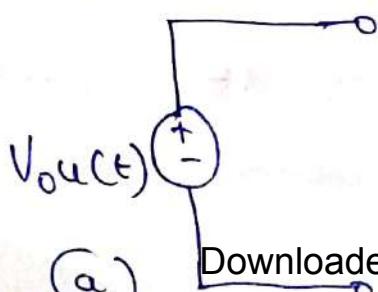A voltage source $V_0 u(t)$ is shown in figure.



from the figure (b) it is evident that terminals a-b are short circuited $V=0$ for $t < 0$, and $V = V_0$ at terminals for $t > 0$.

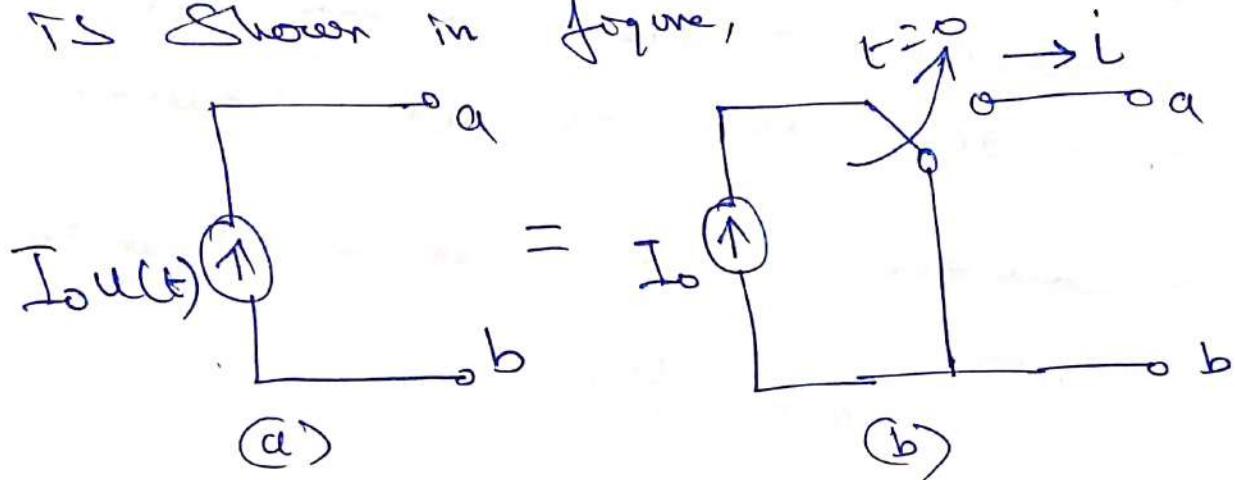Similarly, a Current Source of $I_{out}(t)$ is shown in figure,




from figure (b), Noticed that terminals a & b Open Circuited $i=0$ for $t < 0$, and $i = I_o$ flow for $t > 0$.

STEP RESPONSE OF AN RC CIRCUIT


When the dc source of an RC circuit is suddenly applied, the voltage or current source can be modeled as a step function and the response is known as a step response.

→ The step response is the response of the circuit due to sudden application of a dc voltage or current source.

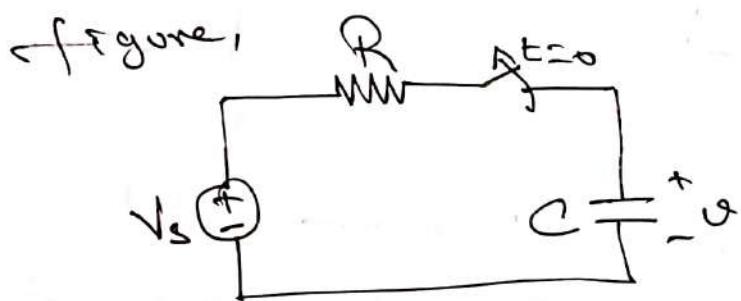→ Consider the RC circuit shown in figure,



which can be replaced by the circuit,

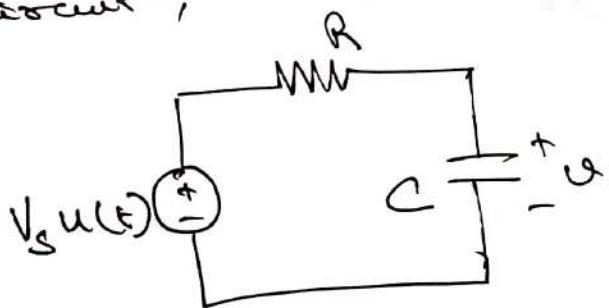

$V_s \rightarrow$ is a constant dc voltage source
Assume an initial voltage V_0 on the capacitor, the voltage on the capacitor cannot change instantaneously.

$$V(0^-) = V(0^+) = V_0$$

Apply KCL,

$$i_R + i_C = i_o$$

$$\frac{V}{R} + C \frac{dv}{dt} = \frac{V_s u(t)}{R}$$

$$\frac{V}{R} - \frac{V_s u(t)}{R} + C \frac{dv}{dt} = 0$$

$$\frac{V - V_s u(t)}{R} + C \frac{dv}{dt} = 0$$

divide by 'C'

$$\frac{V - V_s u(t)}{RC} + \frac{dv}{dt} = 0$$

$$\frac{dv}{dt} + \frac{V}{RC} = \frac{V_s u(t)}{RC}$$

where V is voltage across capacitor at $t > 0$. So $u(t) = 1$ at $t > 0$.

$$\frac{dv}{dt} + \frac{V}{RC} = \frac{V_s}{RC}$$

Rearranging terms,

$$\frac{dv}{dt} = - \frac{(V - V_s)}{RC}$$

$$\frac{dv}{V - V_s} = - \frac{dt}{RC}$$

Integrating both sides

$$\int \frac{dv}{V - V_s} = \int - \frac{dt}{RC}$$

$$\ln(V - V_s) \Big|_{V_0}^{V(t)} = -\frac{t}{RC} \Big|_0^t$$

$$\ln[V(t) - V_s] - \ln[V_0 - V_s] = -\frac{t}{RC} + 0$$

$$\ln \frac{V - V_s}{V_0 - V_s} = -\frac{t}{RC}$$

Taking exponential of both sides,

$$\frac{V - V_s}{V_0 - V_s} = e^{-t/RC}$$

$$\text{where } \tau = RC$$

$$\frac{V - V_s}{V_0 - V_s} = e^{-t/\tau}$$

$$V - V_s = (V_0 - V_s) e^{-t/\tau}$$

$$V(t) = V_s + (V_0 - V_s) e^{-t/\tau}, \quad t > 0.$$

Thus,

$$V(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s) e^{-t/\tau}, & t \geq 0 \end{cases}$$

This is known as Complete Response
of the RC circuit to a Sudden
application of DC Voltage Source.
Capacitor is Initially Charged.

If we assume capacitor is uncharged initially $V_0 = 0$, so the equation becomes,

$$V(t) = \begin{cases} 0, & t < 0 \\ V_s(1 - e^{-t/\tau}), & t > 0 \end{cases}$$

Can be written alternatively as,

$$\boxed{V(t) = V_s(1 - e^{-t/\tau}) u(t)}$$

This is the complete step response of the RC circuit when the capacitor is initially uncharged.

→ The current through the capacitor is obtained from above equation, by using

$$I(t) = C \frac{dV}{dt}$$

$$I(t) = C \frac{d}{dt} V_s(1 - e^{-t/\tau}) u(t)$$

$$\tau = RC \quad t > 0, \quad u(t) = 1$$

$$I(t) = (C)(V_s) \left[-\left(-\frac{1}{\tau}\right) e^{-t/\tau} \right]$$

$$I(t) = \frac{C}{\tau} V_s e^{-t/\tau}$$

$$\boxed{I(t) = \frac{V_s}{R} e^{-t/\tau} u(t)}$$

Complete Response = Natural response + forced
 (Stored energy) Response
 (Independent Source)

Complete Response = Transient Response + Steady State
 (Temporary part) Response
 (Permanent part)

Natural Response = Transient Response

forced Response = Steady State Response

→ Complete Response may be written as,

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}$$


$V(0)$ → initial voltage

$V(\infty)$ → final or steady state value.

To find Step Response of an RC Circuit
 Requires three things,

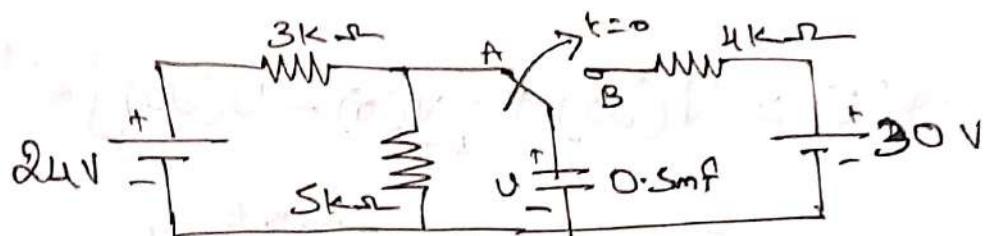
1. The initial Capacitor Voltage $V(0)$, $t < 0$
2. The final Capacitor Voltage $V(\infty)$, $t > 0$
3. The time constant τ .

Ex: 1 The switch in figure has been in position A for a long time. At $t=0$, the switch moves to B. Determine $v(t)$ for $t>0$ and calculate its value at $t=1\text{s}$ and 4s .



~~Solution:~~

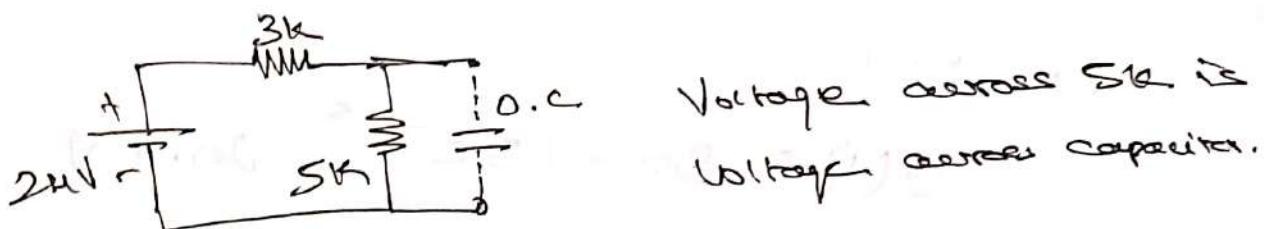* For $t<0 \rightarrow$ Switch is at position 'A'.
Capacitor acts like open circuit.




Using voltage division Rule

$$v(0^-) = 24 \times \frac{5}{3+5} = 15\text{V}$$

* The capacitor voltage cannot change
instantaneously, so,

$$v(0) = v(0^-) = v(0^+) = 15\text{V}$$

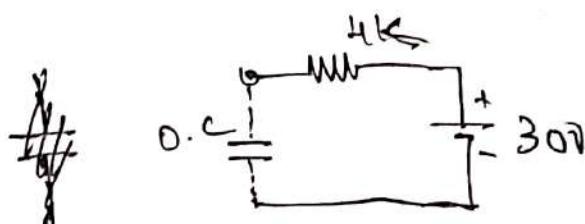* For $t>0 \rightarrow$ Switch is in position 'B'.



$$R_{th} = 4\text{k}\Omega$$

time Constant,

$$\tau = R_m C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2 \text{ s}$$

\rightarrow the capacitor acts like Open Circuit,
to DC at Steady State,

$$V(\infty) = 30V. \quad t > 0$$

Thus,

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}$$

$$= 30 + [15 - 30] e^{-0.5t} \text{ V}$$

$$V(t) = 30 - 15e^{-0.5t} \text{ V}$$

At $t = 1$



$$V(1) = 30 - 15e^{-0.5} = 20.9 \text{ V}$$

At $t = 4$,

$$V(4) = 30 - 15e^{-2} = 27.97 \text{ V}$$

=.

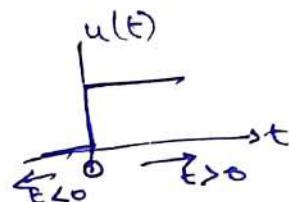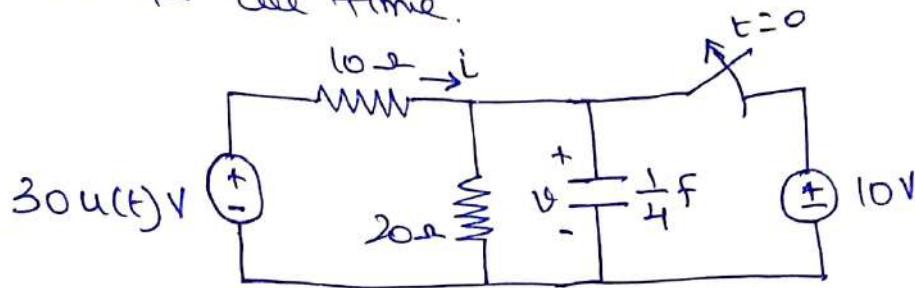Ex:2: In figure the switch has been closed for a long time and is opened at $t=0$. Find i and v for all time.




Solution:

for $t < 0 \rightarrow$ Switch closed

at $t < 0$ the $30u(t) = 0$

So $10V$ source connected with capacitor

It behaves Open Circuited.

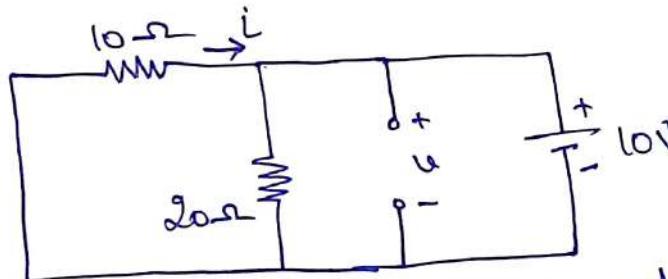

$$30u(t) = \begin{cases} 0 & t < 0 \\ 30 & t > 0 \end{cases}$$


No current flows through 20Ω resistor,

$$I = -\frac{V}{10} = -\frac{10}{10} = -1 \text{ A}, \quad V = 10 \text{ V}$$

Capacitor voltage cannot change instantaneously

$$\text{so, } V(0) = V(0^-) = 10 \text{ V}$$

for $t > 0 \rightarrow$ Switch opened.

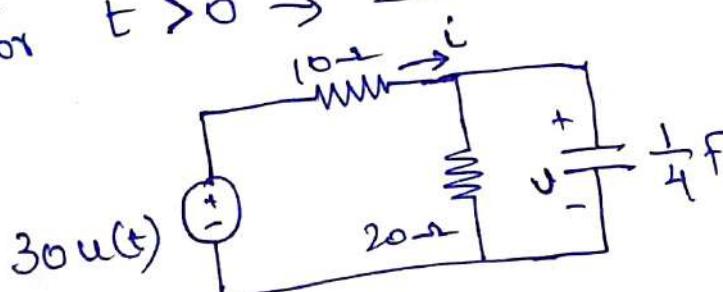

After a long time, the circuit reaches Steady State & Capacitor acts like an open circuit again.

Steady State Voltage, $V(\infty)$ Obtain Using Voltage Division,

$$V(\infty) = 30 \times \frac{20}{20+10} = 20 \text{ V}$$

Find R_{th} by,

$$R_{th} = \frac{10 \times 20}{10 + 20} = \frac{200}{30} = \frac{20}{3} \Omega$$

time constant,

$$\tau = R_{th} C = \frac{20}{3} \times \frac{1}{4} = \frac{20}{12} = \frac{5}{3} \text{ s}$$

Thus,

$$v(t) = V(\infty) + [v(0) - V(\infty)] e^{-t/\tau}$$

$$= 20 + [10 - 20] e^{-(3/5)t}$$

$$v(t) = (20 - 10 e^{-0.6t}) \text{ V}$$

To obtain i ,

$i \rightarrow$ Sum of current through 20Ω and Capacitor.


$$i = \frac{v}{20} + C \frac{dv}{dt}$$

$$= \frac{20 - 10 e^{-0.6t}}{20} + \frac{1}{4} \times \frac{d[20 - 10 e^{-0.6t}]}{dt}$$

$$= (1 + e^{-0.6t}) \text{ A}$$

STEP RESPONSE OF AN RL CIRCUIT

Consider the RL circuit.

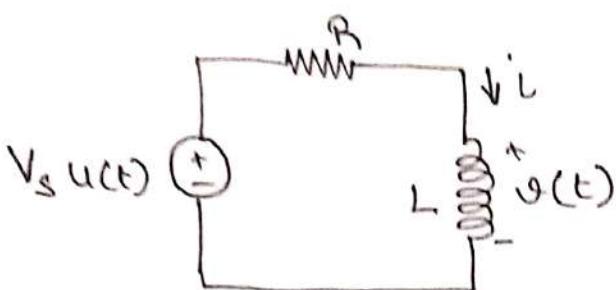

Our goal is to find the inductor current i as the circuit response.

Let the response be the sum of the Natural Current and the forced Current.

$$i = i_n + i_f \quad \text{--- (1)}$$

$\downarrow \quad \downarrow$
Natural response forced response

We know that Natural response is the decaying exponential.

$$i_n = A e^{-t/\tau} \quad \text{--- (2)}$$

$A \rightarrow$ is a constant

forced response is the value of the current long time after switch is closed. At the same time the inductor becomes short circuit and the voltage across it is zero.

The entire source voltage V_s appears across R , thus,

$$i_f = \frac{V_s}{R} \quad \text{--- (3)}$$

Sub equation (2) & (3) in (1)

$$i = A e^{-t/\tau} + \frac{V_s}{R} \quad \text{--- (4)}$$

We now determine the constant A from the value of i_i . Let I_0 be initial current, the current through the inductor cannot change instantaneously,

$$i(0^+) = i(0^-) = I_0 \quad \text{--- (5)}$$

Thus at $t=0$, then equation (4)

Becomes,

$$I_0 = A + \frac{V_s}{R}$$

$$\text{Then, } A = I_0 - \frac{V_s}{R}$$

Substituting 'A' in equation (4)

$$i(t) = \frac{V_s}{R} + \left[I_0 - \frac{V_s}{R} \right] e^{-t/\tau} \quad \text{--- (5)}$$

This is the complete response of the RL circuit.

The Response in equation (5) may be

written as,

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau} \quad \text{--- (6)}$$

$i(0) \rightarrow$ initial value

$i(\infty) \rightarrow$ final value

To find the step response of an RL
circuit requires three things,

1. The initial inductor current $i(0)$ at $t=0^+$
2. final inductor current $i(\infty)$. } $t > 0$
3. The time constant τ .

If switching takes place at time $t=t_0$
instead of $t=0$, equation becomes,

$$i(t) = i(\infty) + [i(t_0) - i(\infty)] e^{-(t-t_0)/\tau}$$

If $i_0 = 0$, then

$$i(t) = \begin{cases} 0, & t < 0 \\ \frac{V_s}{R} (1 - e^{-t/\tau}), & t > 0 \end{cases}$$

$$\therefore i(t) = \frac{V_s}{R} (1 - e^{-t/\tau}) u(t)$$

This is the Step Response of the RL
circuit with no initial inductor current.

The voltage across the inductor is obtained

by,

$$v(t) = L \frac{di}{dt} = V_s \frac{L}{\tau R} e^{-t/\tau}$$


$$\text{where } \tau = \frac{L}{R}$$

$$\therefore v(t) = V_s e^{-t/\tau} u(t)$$

Ex:

find $i(t)$ in the circuit for $t > 0$.

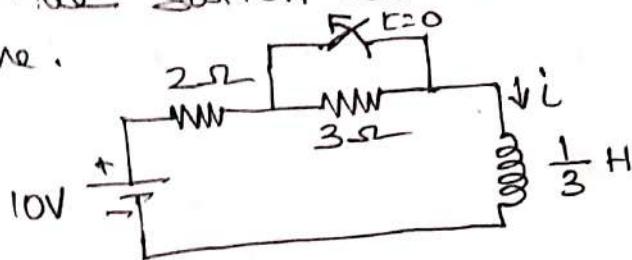Assume that the switch has been closed for a long time.



Solution:

→ for $t < 0$, → the switch is closed position.
So, the 3-Ω Resistor is short-circuited, +
Inductor acts like a short circuit.

The Current through the inductor at $t = 0^-$

$$i(0^-) = \frac{10}{2} = 5 \text{ A}$$

Since the inductor current cannot change
instantaneously,

$$i(0) = i(0^-) = i(0^+) = 5 \text{ A.}$$

→ for $t > 0$, the switch is Open,
2Ω + 3Ω are in Series,

$$i(\infty) = \frac{10}{3+2} = 2 \text{ A at } t > 0.$$

Therein Resistance across inductor,

$$R_{in} = 2 + 3 = 5 \Omega.$$

for time constant,


$$\tau = \frac{L}{R_{in}} = \frac{\frac{1}{3}}{5} = \frac{1}{15} \text{ s.}$$

Thus,

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$= 2 + (5-2) e^{-15t}$$

$$i(t) = 2 + 3 e^{-15t} \text{ A } t > 0.$$

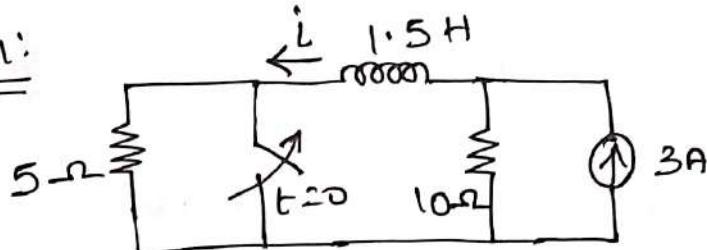PRC Prob 1:

The switch in fig has been closed for a long time. It opens at $t=0$ find $i(t)$ for $t>0$.

Solution: for $t < 0$ - Switch closed, so inductor short circuited and $5\Omega + 10\Omega$ are short circuited (no current flows through $5\Omega + 10\Omega$).

$$i = 3 \text{ A } t < 0.$$

So initial current through inductor cannot change instantaneously,

$$i(0) = I(0) = 3 \text{ A } t = 0$$

for $t > 0$ Switch opened, inductor like short circuit, the current i_1 by CDR

$$i(\infty) = 3 \times \frac{10}{10+5} = 2 \text{ A } t > 0$$

Thevenin Resistance, R_{th} ,

$$\begin{aligned} R_{th} &= \frac{5 \times 10}{15} = \frac{50}{15} = \frac{3.33}{3.33} \\ &= 5 + 10 = 15 \Omega \end{aligned}$$

time constant,


$$\tau = \frac{L}{R_{th}} = \frac{1.5}{\frac{3.33}{15}} = 0.45 \rightarrow 0.1$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$= 2 + [3 - 2] e^{-t/0.1} \rightarrow$$

$$i(t) = (2 + e^{-t}) A, t > 0.$$

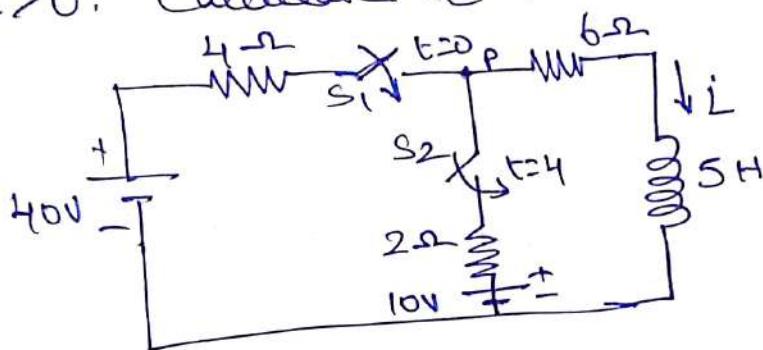Ex2: At $t=0$, Switch 1 in fig is closed, and Switch 2 is closed 4 s later. Find $i(t)$ for $t > 0$. Calculate i for $t=2\text{s}$ and $t=5\text{s}$



Solution: Need to consider three time intervals, $t < 0$, $0 < t < 4$, $t > 4$ separately.

\rightarrow for $t < 0$ \rightarrow switches S_1 & S_2 are open, so

$$i=0. \quad i(0^+) = i(0) = 0$$

\rightarrow for $0 < t < 4 \Rightarrow S_1$ is closed so 4Ω

6Ω are in series.

$$i(\infty) = \frac{40}{4+6} = 4 \text{ A}$$

$$R_{eq} = 4+6 = 10\Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{5}{10} = \frac{1}{2} = 0.5 \rightarrow$$

Then,

$$i(t) = i(\infty) + \{i(0) - i(\infty)\} e^{-t/\tau}$$

$$i(t) = 4 + (0-4) e^{-2t} = 4(1 - e^{-2t}) A$$

$0 < t < 4$

→ for $t > 4$, S_2 is closed, $10V$ DC source is connected. The ~~Inductor~~ charge does not affect the Inductor Current because the Current Cannot Change abruptly. The initial Current is,

$$i(4) = i(4^-) = 4(1 - e^{-8}) \underset{\approx}{=} 4A$$

To find $i(\infty)$, let V be the voltage at node P in fig, Using KCL,

$$\frac{40-V}{4} + \frac{10-V}{2} = \frac{V}{6}$$

$$\frac{40}{4} - \frac{V}{4} + \frac{10}{2} - \frac{V}{2} = \frac{V}{6}$$

$$10 + 5 - \frac{V}{4} - \frac{V}{2} - \frac{V}{6} = 0$$

$$-V \left[\frac{1}{4} + \frac{1}{2} + \frac{1}{6} \right] = -15 \Rightarrow V = 16.3636$$

$$L = \frac{V}{I} = \frac{16.3636}{\frac{4}{6}} = 2.727A$$

$$\therefore i(\infty) = 2.727A$$

Thevenin resistance at Inductors terminal,

$$R_{th} = [4 \parallel 2] + 6 = \frac{4 \times 2}{6} + 6 = \frac{22}{3} \Omega$$

$$Z = \frac{L}{R+4} = \frac{5}{22/3} = \frac{15}{22} \rightarrow$$

$$\therefore i(t) = i(\infty) + [i(4) - i(\infty)] e^{-(t-4)/\tau}$$

Note: $(t-4)$ is time delay

$$i(t) = 2.727 + (4 - 2.727) e^{-(t-4)/\tau}$$

$$= 2.727 + 1.273 e^{-(t-4)/0.6818}$$

$$i(t) = 2.727 + 1.273 e^{-1.4667(t-4)}, t \geq 4$$

$$\therefore i(t) = \begin{cases} 0, & t < 0 \\ 4(1 - e^{-2t}) & 0 < t < 4 \\ 2.727 + 1.273 e^{-1.4667(t-4)}, & t > 4 \end{cases}$$

At: $t = 2$


$$i(2) = 4(1 - e^{-4}) = 3.93 A$$

$t = 4$

$$i(5) = 2.727 + 1.273 e^{-1.4667}$$

$$= \underline{\underline{3.02 A}}$$

THE SOURCE-FREE SERIES RLC CIRCUIT

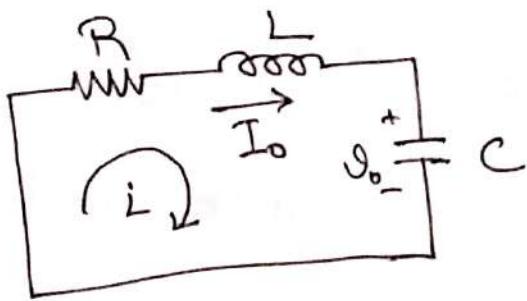

Consider Series RLC Circuit,

initial Capacitor Voltage $\rightarrow V_0$
initial Inductor Current $\rightarrow I_0$ } at $t=0$

\rightarrow the initial value of the derivative of i ,

$$\frac{di(0)}{dt} = -\frac{1}{L} [RI_0 + V_0]$$

[This equation used to find A₂ constant].

\rightarrow Characteristic equation of i ,
[roots of equation]

$$S_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$S_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

where $\alpha = \frac{R}{2L}$ & $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\therefore S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Thus, Natural response of the Series RLC circuit is,

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

A_1 find by initial value $i(0)$

A_2 find by $\frac{di(0)}{dt}$

Based on s_1 & s_2 there are three types of solutions

① If $\underline{\alpha > \omega_0} \rightarrow \underline{\text{Overdamped Case}}$

Response is,

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

② Critically Damped Response

$$\underline{\alpha = \omega_0}$$

$$s_1 = s_2 = -\alpha = -\frac{R}{2L}$$

Response is,

$$i(t) = (A_2 + A_1 t) e^{-\alpha t}$$

③ $\alpha < \omega_0$ Underdamped Case

$$s_1 = -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha + j\omega_d$$

$$s_2 = -\alpha - \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha - j\omega_d$$

$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \rightarrow$ damping frequency.

$\omega_0 \rightarrow$ Undamped Frequency
EnggTree.com

Response is,


$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

time constant $\rightarrow 1/\alpha$


Period $\rightarrow T = 2\pi/\omega_d$

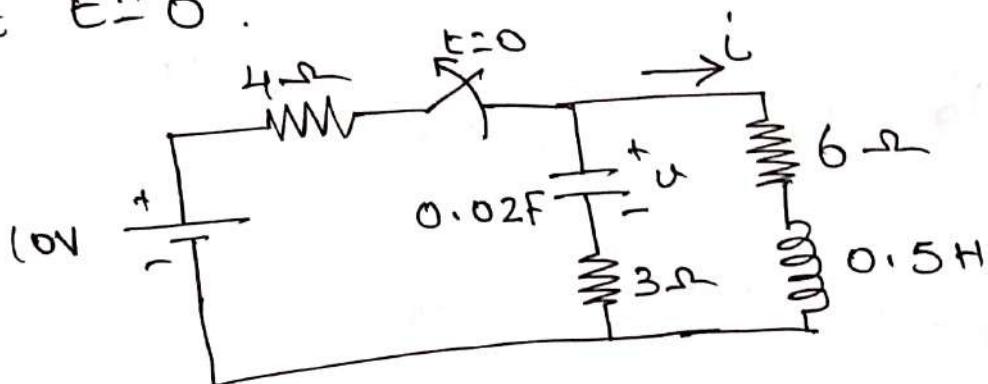Example Problem 1:

Find $i(t)$ in the circuit. Assume that the circuit has reached steady state at $t=0^+$.



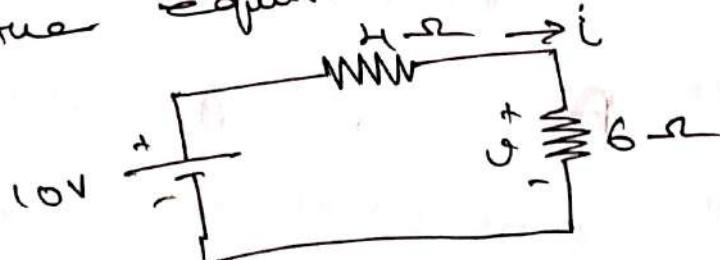Solution: for $t < 0 \rightarrow$ Switch is closed.
The capacitor behaves like open circuit,
 \rightarrow Inductor acts like short circuit, then
the equivalent circuit is,



Initial Current through Inductor $i(0) = \frac{10}{4+6} = 1 \text{ A}$ and


Voltage across $i(0) = 6 \times 1 = 6 \text{ V}$ [Voltage across 6 ohm]

Downloaded from EnggTree.com

$i(t) \rightarrow$ Current through inductor

$v(t) \rightarrow$ Voltage across capacitor.

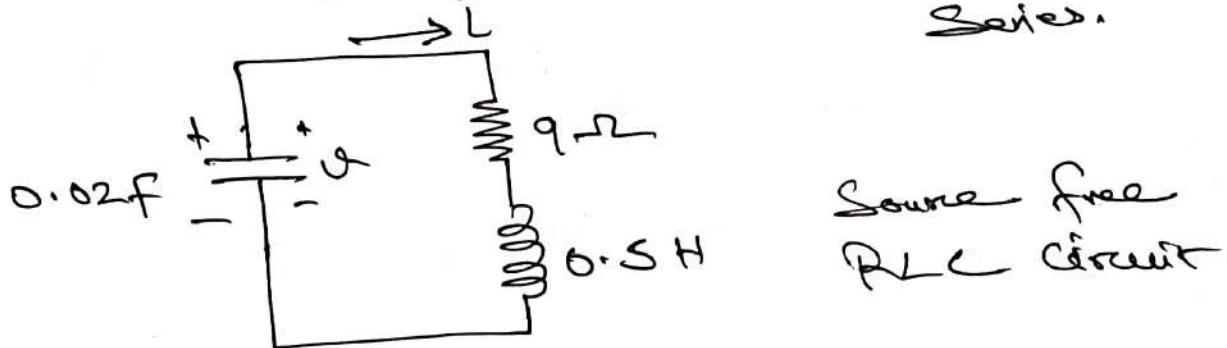- * for $t > 0$, \rightarrow Switch Opened, equivalent circuit is, $6\Omega + 3\Omega$ are in series.



Roots are calculated as,

$$\alpha = \frac{R}{2L} = \frac{9}{2 \times 0.5} = 9$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.5 \times 0.02}} = 10$$

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -9 \pm \sqrt{9^2 - 10^2} = -9 \pm \sqrt{81 - 100}$$

$$S_{1,2} = -9 \pm j4.359 \quad [S_{1,2} = -\alpha \pm j\omega_d]$$

$\alpha < \omega_0 \rightarrow$ Under damped

$$i(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$

$$i(t) = e^{-9t} (A_1 \cos 4.359t + A_2 \sin 4.359t)$$

$A_1 \vee A_2$ find initial conditions.

At $t = 0$,

$$i(0) = 1 = A_1$$

then A_2 find by,

$$\textcircled{1} \rightarrow \left. \frac{di}{dt} \right|_{t=0} = -\frac{1}{L} [Ri(0) + V(0)] \\ = -2[9 - 6] = -6 \text{ A/s}$$

$V(0) = V_0 = -6 \rightarrow$ because of
[Opposite direction of capacitor voltage \rightarrow
 $6 \text{ in resistor voltage.}$]

Now, derive $i(t)$

$$\textcircled{2} \rightarrow \frac{di}{dt} = -9e^{-9t} (A_1 \cos 4.359t + A_2 \sin 4.359t) \\ + e^{-9t} (4.359) \{-A_1 \sin 4.359t + A_2 \cos 4.359t\}$$

Impose the two equations, $\textcircled{1} \vee \textcircled{2}$
at $t = 0$

$$-6 = -9[A_1 + 0] + 4.359[0 + A_2]$$

$$\boxed{A_1 = 1}$$

$$-6 = -9[1] + 4.359[A_2]$$

$$A_2 = \frac{-6 + 9}{4.359} = \frac{3}{4.359} = 0.6882$$

Sub values $A_1 \vee A_2$ in $i(t)$

Complete response,

$$i(t) = e^{-at} (\cos 4.35at + 0.6882 \sin 4.35at)$$

A

Source Free Parallel RLC Circuit

$(\alpha > \omega_0)$ Overdamped

$$V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$(\alpha = \omega_0)$ Critically Damped Case

$$v(t) = (A_1 + A_2 t) e^{-\alpha t}$$

$(\alpha < \omega_0)$ Underdamped Case

$$s_{1,2} = -\alpha \pm j\omega_L$$

$$\omega_L = \sqrt{\omega_0^2 - \alpha^2}$$

$$v(t) = e^{-\alpha t} (A_1 \cos(\omega_L t) + A_2 \sin(\omega_L t))$$

$$\frac{V_0}{R} + I_0 + C \frac{dV(t)}{dt} = 0$$

$$\frac{dV(t)}{dt} = -\frac{(V_0 + RI_0)}{RC}$$

In the parallel circuit find $V(t)$ & for $t=0$,
 assuming $V(0)=5V$, $i(0)=0$, $L=1H$ & $C=10mF$
 consider these values:

$$R = 1.923 \Omega, R = 5 \Omega, R = 6.25 \Omega$$

(well)

$$\text{if } R = 1.923 \Omega$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 1.923 \times 10 \times 10^{-3}} = \underline{\underline{26}}$$

$$\omega_0 = \frac{1}{RC} = \frac{1}{1 \times 10 \times 10^{-3}} = \underline{\underline{10}}$$

Since $\alpha > \omega_0$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -2, -50$$

∴ The corresponding response is

$$V(t) = A_1 e^{-2t} + A_2 e^{-50t}$$

Initial condition to get A_1 & A_2

$$V(0) = 5 = A_1 + A_2$$

$$\frac{dV(t)}{dt} = -\frac{V(t) + R_i(0)}{RC} = -\frac{5+0}{1.923 \times 10 \times 10^{-3}} = \underline{\underline{-260}}$$

By differentiating

$$\frac{dV}{dt} = -2A_1 e^{-2t} - 50A_2 e^{-50t}$$

At $t=0$

$$-260 = -2A_1 - 50A_2$$

$$A_1 = -0.2083$$

$$A_2 = 5.208$$

Subs A_1 , A_2 .

$$v(t) = -0.2083 e^{-2t} + 5.208 e^{-50t}$$

~~case 2~~ $R = 5 \times 10^3$

$$\omega = \frac{1}{2RC} = \frac{1}{2 \times 5 \times 10^3} = 10$$

While $\omega_0 = \omega$ remains the same.

$\omega = \omega_0 = 10$, the response is critically damped,

$$S_1 = S_2 = -10$$

$$v(t) = (A_1 + A_2 t) e^{-10t}$$

To get A_1 & A_2

$$v(0) = 5 = A_1$$

$$\frac{dv(0)}{dt} = -\frac{v(0) + R_0 i(0)}{RC} = -\frac{5 + 0}{5 \times 10^3 \times 10^{-3}} = -100$$

By diff.

$$\frac{dv}{dt} = (-10A_1 - 10A_2 t + A_2) e^{-10t}$$

$$At t=0$$

$$-100 = -10A_1 + A_2$$

$$A_1 = 5$$

$$A_2 = -50$$

$$v(t) = (5 - 50t) e^{-10t}$$

When $R=6.25\Omega$

$$\frac{V}{R_C} = \frac{1}{2 \times 6.25 \times 10 \times 10^{-3}} = \underline{\underline{8}}$$

(While $\omega_0 = 10$ remains the same, As $\omega < \omega_0$ in this case)

RC response is underdamped. The roots of the characteristic eqn

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -8 \pm j6$$

hence

$$v(t) = (A_1 \cos 6t + A_2 \sin 6t) e^{-8t}$$

We obtain A_1 & A_2

$$V(0) = 5 = A_1$$

$$\frac{dV(0)}{dt} = \frac{-V(0) + Rv(0)}{R_C} = \frac{-5 + 0}{6.25 \times 10 \times 10^{-3}} = \underline{\underline{-80}}$$

But differentiating

$$\frac{dv}{dt} = (-8A_1 \cos 6t - 8A_2 \sin 6t - 6A_1 \sin 6t + 6A_2 \cos 6t)e^{-8t}$$


At $t=0$,

$$-80 = -8A_1 + 6A_2$$

$$A_1 = 5, A_2 = -6.67 \text{ Thus}$$

$$v(t) = (5 \cos 6t - 6.67 \sin 6t) e^{-8t}$$

Find $V(t)$ for $t > 0$ in the circuit.

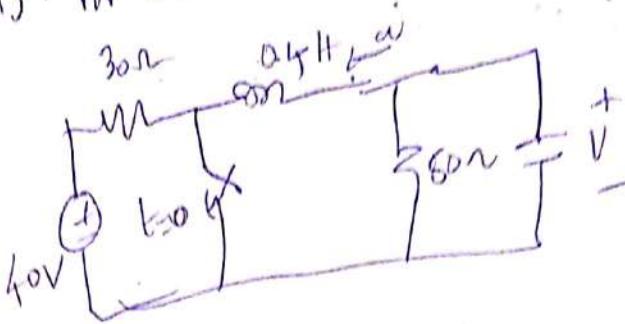

At $t < 0$

$$V(0) = \frac{50 \times 40}{50 + 30} = \underline{\underline{25V}}$$

initial current through the inductor

$$i(0) = -\frac{40}{30+50} = -\underline{\underline{0.5A}}$$

$$\frac{dV(0)}{dt} = -V(0) + R i(0) = 25 - \frac{50 \times 0.5}{50 \times 20 \times 10^{-6}} = \underline{\underline{0}}$$

$t > 0$: Switch is closed, 30Ω & $1Vdc$ are bypassed.

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 50 \times 20 \times 10^{-6}} = \underline{\underline{500}}$$

$$\omega_0 = \frac{1}{RC} = \frac{1}{0.4 \times 20 \times 10^{-6}} = \underline{\underline{354}}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -500 \pm \sqrt{250000 - 124992.6} = -500 \pm 354$$

$$s_1 = -\underline{\underline{854}} \quad s_2 = -\underline{\underline{146}}$$

Since $\omega > \omega_0$, we have overdamped / reflex.

$$V(t) = A_1 e^{-854t} + A_2 e^{-146t}$$

At $t=0$

$$V(0) = 25 = A_1 + A_2$$

$$A_2 = 25 - A_1$$

Taking the derivative of $V(t)$

$$\frac{dV}{dt} = -854A_1 e^{-854t} - 146A_2 e^{-146t}$$


$$\frac{dV(0)}{dt} = 0 \Rightarrow -854A_1 - 146A_2$$


$$0 = 854A_1 + 146A_2$$

$$A_1 = \underline{\underline{-5.156}}$$

$$A_2 = \underline{\underline{30.16}}$$

$$V(t) = -5.156e^{-854t} + 30.16e^{-146t}$$

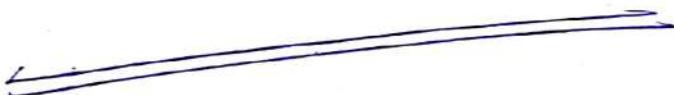

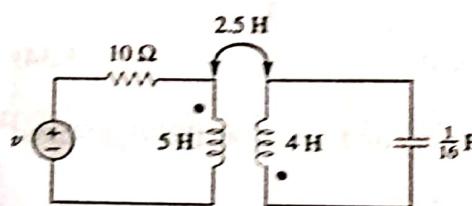Example 13.3**Figure 13.16**

For Example 13.3.

Consider the circuit in Fig. 13.16. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time $t = 1 \text{ s}$ if $v = 60 \cos(4t + 30^\circ) \text{ V}$.

Solution:

The coupling coefficient is

$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2.5}{\sqrt{20}} = 0.56$$

indicating that the inductors are tightly coupled. To find the energy stored, we need to calculate the current. To find the current, we need to obtain the frequency-domain equivalent of the circuit.

$$\begin{aligned} 60 \cos(4t + 30^\circ) &\Rightarrow 60/30^\circ, \quad \omega = 4 \text{ rad/s} \\ 5 \text{ H} &\Rightarrow j\omega L_1 = j20 \Omega \\ 2.5 \text{ H} &\Rightarrow j\omega M = j10 \Omega \\ 4 \text{ H} &\Rightarrow j\omega L_2 = j16 \Omega \\ \frac{1}{16} \text{ F} &\Rightarrow \frac{1}{j\omega C} = -j4 \Omega \end{aligned}$$

The frequency-domain equivalent is shown in Fig. 13.17. We now apply mesh analysis. For mesh 1,

$$(10 + j20)I_1 + j10I_2 = 60/30^\circ \quad (13.3.1)$$

For mesh 2,

$$j10I_1 + (j16 - j4)I_2 = 0$$

$$I_1 = -1.2I_2 \quad (13.3.2)$$

Substituting this into Eq. (13.3.1) yields

$$I_2(-12 - j14) = 60 \angle 30^\circ \Rightarrow I_2 = 3.254 \angle 160.6^\circ \text{ A}$$

$$I_1 = -1.2I_2 = 3.905 \angle -19.4^\circ \text{ A}$$

In the time-domain,

$$i_1 = 3.905 \cos(4t - 19.4^\circ), \quad i_2 = 3.254 \cos(4t + 160.6^\circ)$$

At time $t = 1 \text{ s}$, $4t = 4 \text{ rad} = 229.2^\circ$, and

$$i_1 = 3.905 \cos(229.2^\circ - 19.4^\circ) = -3.389 \text{ A}$$

$$i_2 = 3.254 \cos(229.2^\circ + 160.6^\circ) = 2.824 \text{ A}$$

The total energy stored in the coupled inductors is

$$\begin{aligned} w &= \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 + M_i_1i_2 \\ &= \frac{1}{2}(5)(-3.389)^2 + \frac{1}{2}(4)(2.824)^2 + 2.5(-3.389)(2.824) = 20.73 \text{ J} \end{aligned}$$

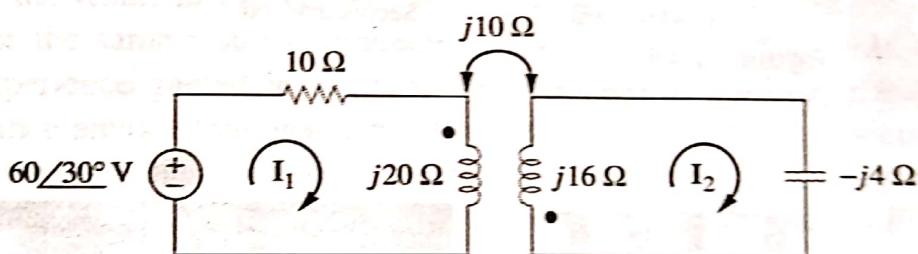


Figure 13.17

Frequency-domain equivalent of the circuit in Fig. 13.16.

Practice Problem 13.3

For the circuit in Fig. 13.18, determine the coupling coefficient and the energy stored in the coupled inductors at $t = 1.5 \text{ s}$.

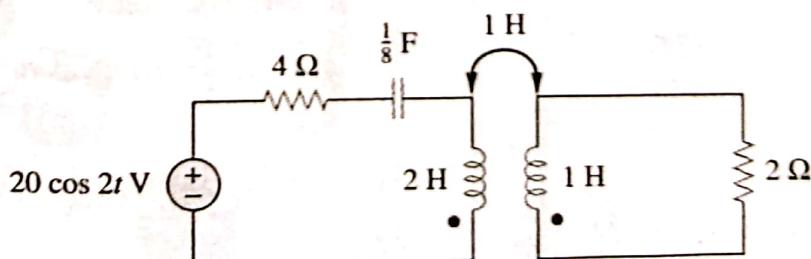


Figure 13.18

For Practice Prob. 13.3.

Answer: 0.7071, 9.85 J.

Example 13.7

An ideal transformer is rated at 2400/120 V, 9.6 kVA, and has 50 turns on the secondary side. Calculate (a) the turns ratio, (b) the number of turns on the primary side, and (c) the current ratings for the primary and secondary windings.

Solution:

(a) This is a step-down transformer, since $V_1 = 2,400 \text{ V} > V_2 = 120 \text{ V}$.

$$n = \frac{V_2}{V_1} = \frac{120}{2,400} = 0.05$$

(b)

$$n = \frac{N_2}{N_1} \Rightarrow 0.05 = \frac{50}{N_1}$$

or

$$N_1 = \frac{50}{0.05} = 1,000 \text{ turns}$$

(c) $S = V_1 I_1 = V_2 I_2 = 9.6 \text{ kVA}$. Hence,

$$I_1 = \frac{9,600}{V_1} = \frac{9,600}{2,400} = 4 \text{ A}$$

$$I_2 = \frac{9,600}{V_2} = \frac{9,600}{120} = 80 \text{ A} \quad \text{or} \quad I_2 = \frac{I_1}{n} = \frac{4}{0.05} = 80 \text{ A}$$

Practice Problem 13.7

The primary current to an ideal transformer rated at 3300/110 V is 3 A. Calculate: (a) the turns ratio, (b) the kVA rating, (c) the secondary current.

Answer: (a) 1/30, (b) 9.9 kVA, (c) 90 A.

Example 13.8

For the ideal transformer circuit of Fig. 13.37, find: (a) the source current I_1 , (b) the output voltage V_o , and (c) the complex power supplied by the source.

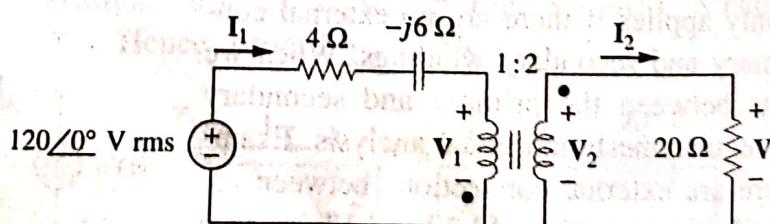


Figure 13.37

For Example 13.8.

Solution:

(a) The 20-Ω impedance can be reflected to the primary side and we get

$$Z_R = \frac{20}{n^2} = \frac{20}{4} = 5 \Omega$$

Thus,

$$\begin{aligned} Z_{in} &= 4 - j6 + Z_R = 9 - j6 = 10.82 \angle -33.69^\circ \Omega \\ I_1 &= \frac{120 \angle 0^\circ}{Z_{in}} = \frac{120 \angle 0^\circ}{10.82 \angle -33.69^\circ} = 11.09 \angle 33.69^\circ A \end{aligned}$$

(b) Since both I_1 and I_2 leave the dotted terminals,

$$I_2 = -\frac{1}{n} I_1 = -5.545 \angle 33.69^\circ A$$

$$V_o = 20I_2 = 110.9 \angle 213.69^\circ V$$

(c) The complex power supplied is

$$S = V_s I_1^* = (120 \angle 0^\circ)(11.09 \angle -33.69^\circ) = 1,330.8 \angle -33.69^\circ VA$$

In the ideal transformer circuit of Fig. 13.38, find V_o and the complex power supplied by the source.

Practice Problem 13.8

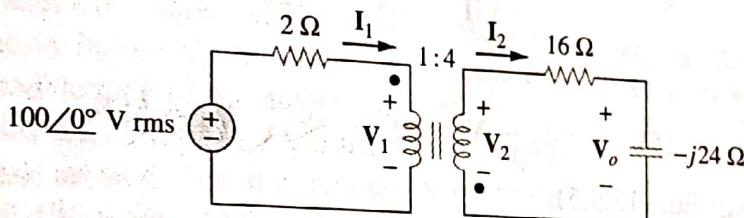


Figure 13.38
For Practice Prob. 13.8.

Answer: $178.9 \angle 116.56^\circ V$, $2,981.5 \angle -26.56^\circ VA$

Example 13.9

Calculate the power supplied to the 10Ω resistor in the ideal transformer circuit of Fig. 13.39.

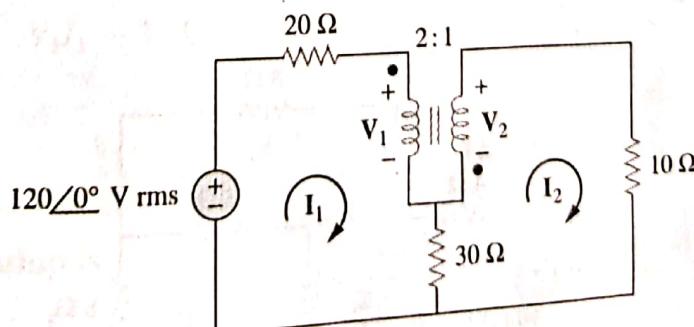


Figure 13.39
For Example 13.9.

Solution:
Reflection to the secondary or primary side cannot be done with this circuit: there is direct connection between the primary and secondary sides due to the 30Ω resistor. We apply mesh analysis. For mesh 1,

$$-120 + (20 + 30)\mathbf{I}_1 - 30\mathbf{I}_2 + \mathbf{V}_1 = 0$$

or

$$50\mathbf{I}_1 - 30\mathbf{I}_2 + \mathbf{V}_1 = 120 \quad (13.9.1)$$

For mesh 2,

$$-\mathbf{V}_2 + (10 + 30)\mathbf{I}_2 - 30\mathbf{I}_1 = 0 \quad (13.9.1)$$

or

$$-30\mathbf{I}_1 + 40\mathbf{I}_2 - \mathbf{V}_2 = 0 \quad (13.9.2)$$

At the transformer terminals,

$$\mathbf{V}_2 = -\frac{1}{2}\mathbf{V}_1 \quad (13.9.3)$$

$$\mathbf{I}_2 = -2\mathbf{I}_1 \quad (13.9.4)$$

(Note that $n = 1/2$.) We now have four equations and four unknowns, but our goal is to get \mathbf{I}_2 . So we substitute for \mathbf{V}_1 and \mathbf{I}_1 in terms of \mathbf{V}_2 and \mathbf{I}_2 in Eqs. (13.9.1) and (13.9.2). Equation (13.9.1) becomes

$$-55\mathbf{I}_2 - 2\mathbf{V}_2 = 120 \quad (13.9.5)$$

and Eq. (13.9.2) becomes

$$15\mathbf{I}_2 + 40\mathbf{I}_2 - \mathbf{V}_2 = 0 \Rightarrow \mathbf{V}_2 = 55\mathbf{I}_2 \quad (13.9.6)$$

Substituting Eq. (13.9.6) in Eq. (13.9.5),

$$-165\mathbf{I}_2 = 120 \Rightarrow \mathbf{I}_2 = -\frac{120}{165} = -0.7272 \text{ A}$$

The power absorbed by the 10Ω resistor is

$$P = (-0.7272)^2(10) = 5.3 \text{ W}$$

Practice Problem 13.9

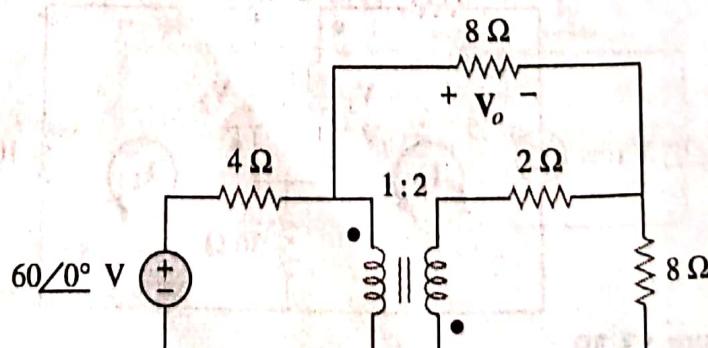
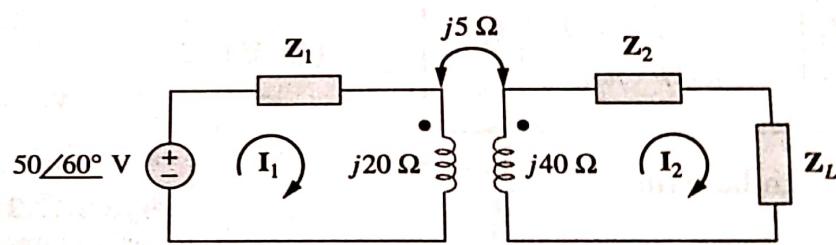
Find \mathbf{V}_o in the circuit of Fig. 13.40.

Figure 13.40
For Practice Prob. 13.9.

Answer: 24 V.

Example 13.4

In the circuit of Fig. 13.24, calculate the input impedance and current I_1 . Take $Z_1 = 60 - j100 \Omega$, $Z_2 = 30 + j40 \Omega$, and $Z_L = 80 + j60 \Omega$.

**Figure 13.24**

For Example 13.4.

Solution:

From Eq. (13.41),

$$\begin{aligned}
 Z_{in} &= Z_1 + j20 + \frac{(5)^2}{j40 + Z_2 + Z_L} \\
 &= 60 - j100 + j20 + \frac{25}{110 + j140} \\
 &= 60 - j80 + 0.14 \angle -51.84^\circ \\
 &= 60.09 - j80.11 = 100.14 \angle -53.1^\circ \Omega
 \end{aligned}$$

Thus,

$$I_1 = \frac{V}{Z_{in}} = \frac{50 / 60^\circ}{100.14 / -53.1^\circ} = 0.5 / 113.1^\circ \text{ A}$$

Find the input impedance of the circuit in Fig. 13.25 and the current from the voltage source.

Practice Problem 13.4

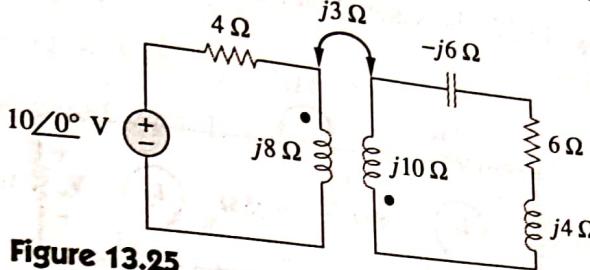


Figure 13.25
For Practice Prob. 13.4.

Answer: $8.58 / 58.05^\circ \Omega$, $1.165 / -58.05^\circ \text{ A}$.

Example 13.5

Determine the T-equivalent circuit of the linear transformer in Fig. 13.26(a).

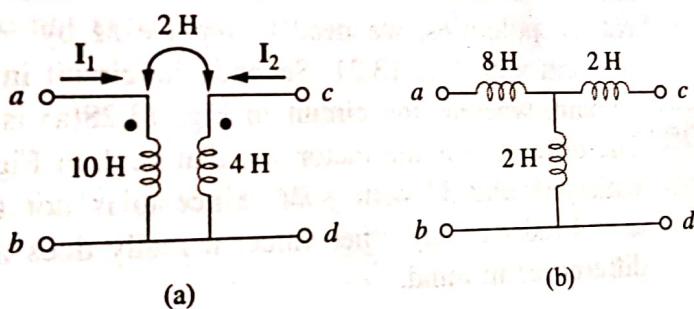


Figure 13.26
For Example 13.5: (a) a linear transformer, (b) its
T-equivalent circuit.

Solution:

Given that $L_1 = 10$, $L_2 = 4$, and $M = 2$, the T-equivalent network has the following parameters:

$$L_a = L_1 - M = 10 - 2 = 8 \text{ H}$$

$$L_b = L_2 - M = 4 - 2 = 2 \text{ H}, \quad L_c = M = 2 \text{ H}$$

The T-equivalent circuit is shown in Fig. 13.26(b). We have assumed that reference directions for currents and voltage polarities in the primary and secondary windings conform to those in Fig. 13.21. Otherwise, we may need to replace M with $-M$, as Example 13.6 illustrates.

Practice Problem 13.5

For the linear transformer in Fig. 13.26(a), find the Π equivalent network.

Answer: $L_A = 18 \text{ H}$, $L_B = 4.5 \text{ H}$, $L_C = 18 \text{ H}$.

Example 13.6

Solve for I_1 , I_2 , and V_o in Fig. 13.27 (the same circuit as for Practice Prob. 13.1) using the T-equivalent circuit for the linear transformer.

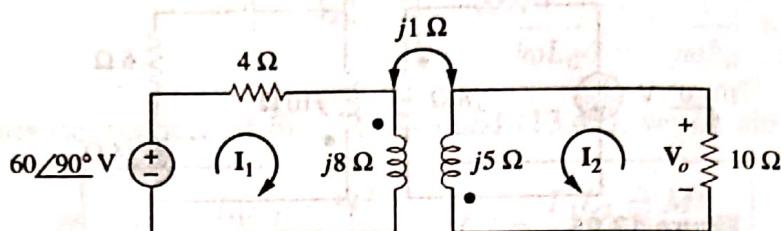


Figure 13.27
For Example 13.6.

Solution:

Notice that the circuit in Fig. 13.27 is the same as that in Fig. 13.10 except that the reference direction for current I_2 has been reversed, just to make the reference directions for the currents for the magnetically coupled coils conform with those in Fig. 13.21.

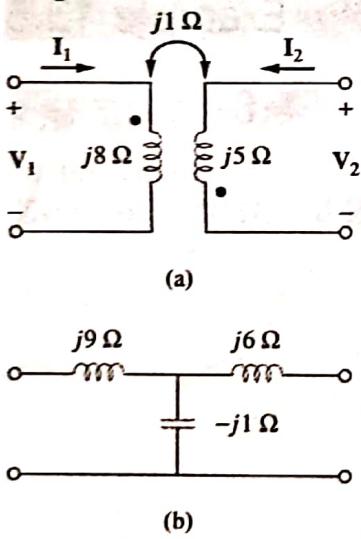


Figure 13.28

For Example 13.6: (a) circuit for coupled coils of Fig. 13.27, (b) T-equivalent circuit.

We need to replace the magnetically coupled coils with the T-equivalent circuit. The relevant portion of the circuit in Fig. 13.27 is shown in Fig. 13.28(a). Comparing Fig. 13.28(a) with Fig. 13.21 shows that there are two differences. First, due to the current reference directions and voltage polarities, we need to replace M by $-M$ to make Fig. 13.28(a) conform with Fig. 13.21. Second, the circuit in Fig. 13.21 is in the time-domain, whereas the circuit in Fig. 13.28(a) is in the frequency-domain. The difference is the factor $j\omega$; that is, L in Fig. 13.21 has been replaced with $j\omega L$ and M with $j\omega M$. Since ω is not specified, we can assume $\omega = 1 \text{ rad/s}$ or any other value; it really does not matter. With these two differences in mind,

$$L_a = L_1 - (-M) = 8 + 1 = 9 \text{ H}$$

$$L_b = L_2 - (-M) = 5 + 1 = 6 \text{ H}, \quad L_c = -M = -1 \text{ H}$$

Thus, the T-equivalent circuit for the coupled coils is as shown in Fig. 13.28(b).

Inserting the T-equivalent circuit in Fig. 13.28(b) to replace the two coils in Fig. 13.27 gives the equivalent circuit in Fig. 13.29, which can be solved using nodal or mesh analysis. Applying mesh analysis, we obtain

$$j6 = I_1(4 + j9 - j1) + I_2(-j1) \quad (13.6.2)$$

and

$$0 = I_1(-j1) + I_2(10 + j6 - j1) \quad (13.6.3)$$

From Eq. (13.6.2),

$$I_1 = \frac{(10 + j5)}{j} I_2 = (5 - j10) I_2 \quad (13.6.3)$$

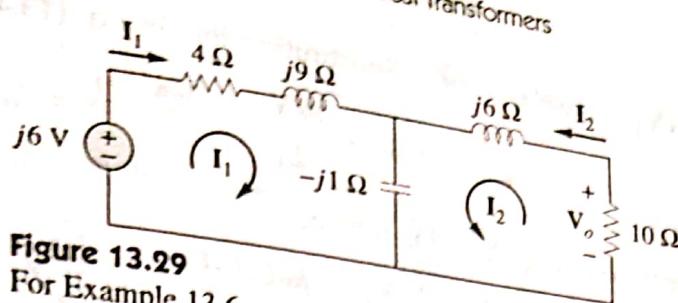


Figure 13.29
For Example 13.6.

Substituting Eq. (13.6.3) into Eq. (13.6.1) gives

$$j6 = (4 + j8)(5 - j10)\mathbf{I}_2 - j\mathbf{I}_2 = (100 - j)\mathbf{I}_2 \approx 100\mathbf{I}_2$$

Since 100 is very large compared with 1, the imaginary part of $(100 - j)$ can be ignored so that $100 - j \approx 100$. Hence,

$$\mathbf{I}_2 = \frac{j6}{100} = j0.06 = 0.06 \angle 90^\circ \text{ A}$$

From Eq. (13.6.3),

$$\mathbf{I}_1 = (5 - j10)j0.06 = 0.6 + j0.3 \text{ A}$$

and

$$\mathbf{V}_o = -10\mathbf{I}_2 = -j0.6 = 0.6 \angle -90^\circ \text{ V}$$

This agrees with the answer to Practice Prob. 13.1. Of course, the direction of \mathbf{I}_2 in Fig. 13.10 is opposite to that in Fig. 13.27. This will not affect \mathbf{V}_o , but the value of \mathbf{I}_2 in this example is the negative of that of \mathbf{I}_2 in Practice Prob. 13.1. The advantage of using the T-equivalent model for the magnetically coupled coils is that in Fig. 13.29 we do not need to bother with the dot on the coupled coils.

Practice Problem 13.6

Solve the problem in Example 13.1 (see Fig. 13.9) using the T-equivalent model for the magnetically coupled coils.

Answer: $13 \angle -49.4^\circ \text{ A}$, $2.91 \angle 14.04^\circ \text{ A}$.