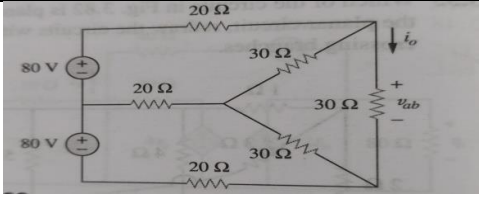
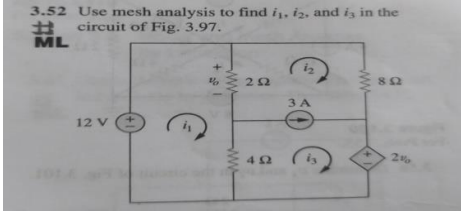
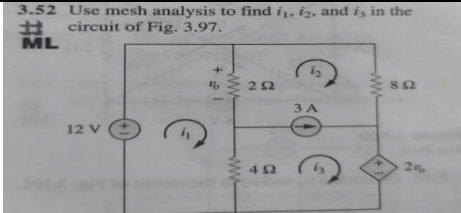
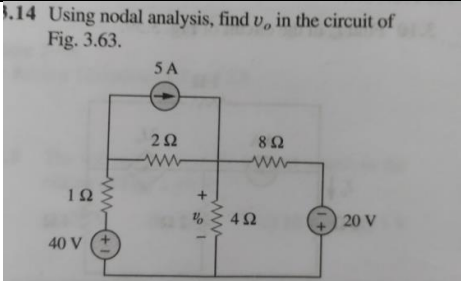
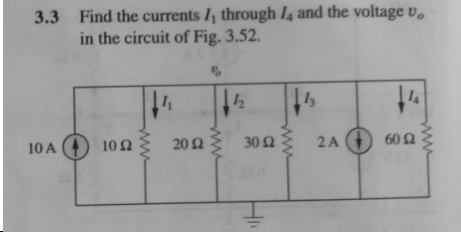
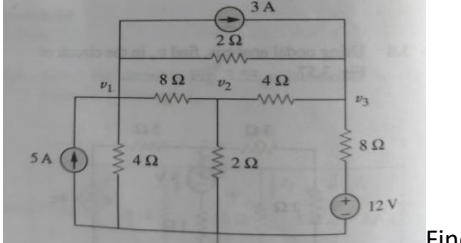


Course Code/Name : EC 3251 Circuit Analysis
Regulation : 2021










Unit I - V Slot Questions

QNo	Unit .No.	Questions	Status	Marks	Sign
				8	
1	I	 <p style="text-align: right;">Find V_{ab} and I_o using Mesh</p>		8	
2	I	<p>3.52 Use mesh analysis to find i_1, i_2, and i_3 in the circuit of Fig. 3.97.</p> 		8	
3	I	<p>3.52 Use mesh analysis to find i_1, i_2, and i_3 in the circuit of Fig. 3.97.</p> 		8	
4	I	<p>1.14 Using nodal analysis, find v_o in the circuit of Fig. 3.63.</p> 		8	
5	I	<p>3.3 Find the currents I_1 through I_4 and the voltage v_o in the circuit of Fig. 3.52.</p> 		8	
6	I	 <p style="text-align: right;">Find V_1, V_2, V_3 using Nodal Analysis</p>		8	

7	I	<p>3.23 Use nodal analysis to find V_o in the circuit of Fig. 3.72.</p>		8	
8	I			8	
9	I			8	
10	I	<p>2.31 For the circuit in Fig. 2.95, determine i_1 to i_5.</p>		8	

Unit II Slot Questions

1	II	<p>Find i_o using Super Position Theorem</p>	8	
2	II	<p>Find i using Super Position Theorem</p>	8	

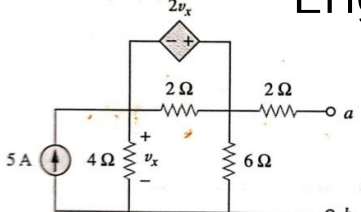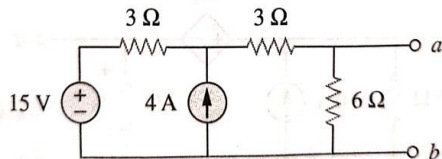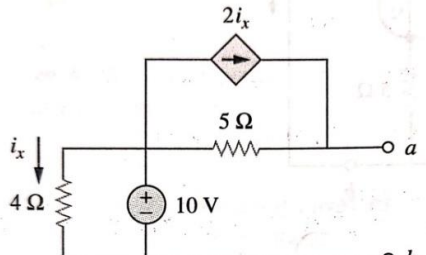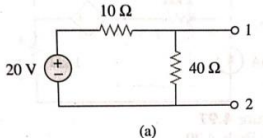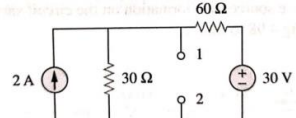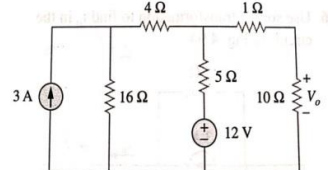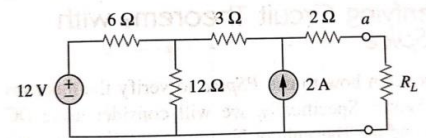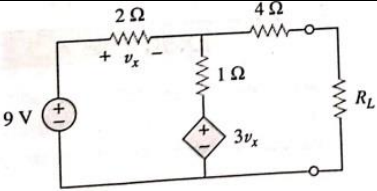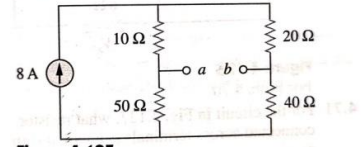3	II	 <p>Draw the thevenins equivalent ckt</p>	8	
4	II	 <p>Draw Nortons Equivalent ckt</p>	8	
5	II	 <p>Draw Nortons Equivalent</p>	8	
6	II	<p>4.33 Determine R_{Th} and V_{Th} at terminals 1-2 of each of the circuits in Fig. 4.101.</p>  	8	
7	II	 <p>Draw Thevenins and Nortons ckt</p>	8	
8	II	<p>Find the value of R_L for maximum power transfer in the circuit in Fig. 4.50. Find the maximum power.</p> 	8	
9	II	 <p>Find R_L for P_{max} also P_{max}</p>	8	
10	II	<p>Determine the Thevenin and Norton equivalents at terminals $a-b$ of the circuit in Fig. 4.125.</p> 	8	

Unit III

EnggTree.com

1	III		8
---	-----	--	---

Find V1 and V2 using Nodal Analysis

2	III		8
---	-----	--	---

Find V1 and V2 using Nodal Analysis

3	III		8
---	-----	--	---

Find i1, i2 and i2 using Mesh Analysis

4	III		8
---	-----	--	---

Find I0 using Mesh Analysis

5	III		8
---	-----	--	---

Find I0 using Mesh Analysis

6	III	<p>The voltage across a load is $v(t) = 60 \cos(\omega t - 10^\circ) \text{ V}$ and the current through the element in the direction of the voltage drop is $i(t) = 1.5 \cos(\omega t + 50^\circ) \text{ A}$. Find: (a) the complex and apparent powers, (b) the real and reactive powers, and (c) the power factor and the load impedance.</p>	8
---	-----	---	---

7	III	<p>For a load, $V_{\text{rms}} = 110/85^\circ \text{ V}$, $I_{\text{rms}} = 0.4/15^\circ \text{ A}$. Determine: (a) the complex and apparent power, the real and reactive powers, and (c) the power factor and the load impedance.</p>	8
---	-----	--	---

8	III		8
---	-----	--	---

Find Zin

9	III		8
---	-----	--	---









Find I using star to delta or delta to star








10	III	<p>A series-connected load draws a current $i(t) = 4 \cos(100\pi t + 10^\circ) \text{ A}$ when the applied voltage is $v(t) = 120 \cos(100\pi t - 20^\circ) \text{ V}$. Find the apparent power and the power factor of the load. Determine the element values that form the series-connected load.</p>	8
----	-----	---	---

Unit IV

1	IV		8
---	----	--	---

find I0 , vx, vc (assume vc is fully charged initially)

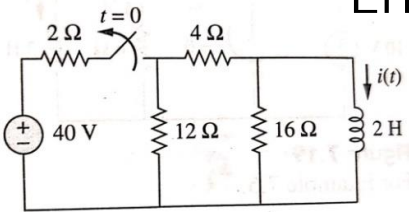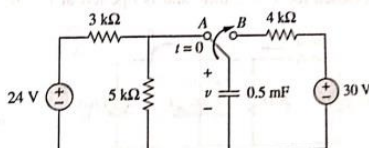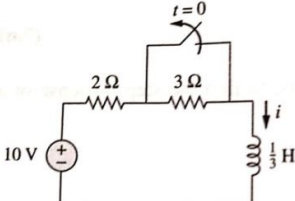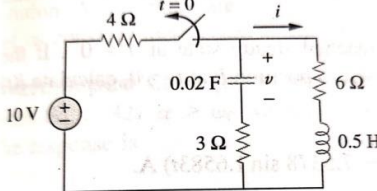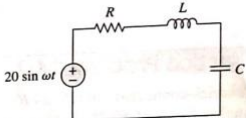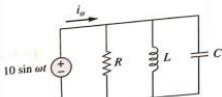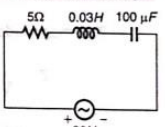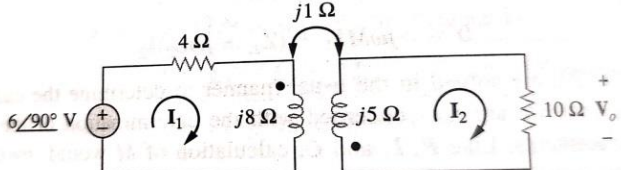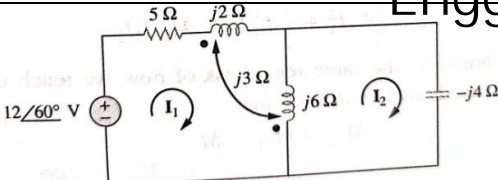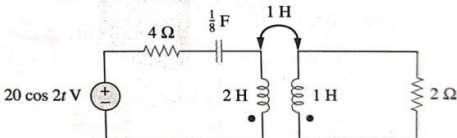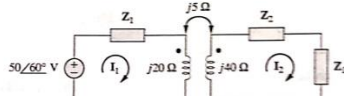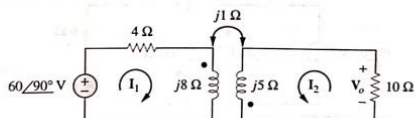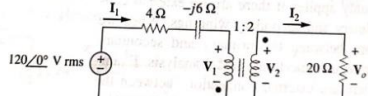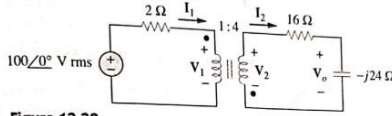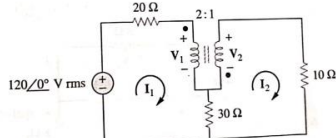2	IV	 <p>find $i(t)$ at $t > 0$</p>	8	
3	IV	<p>The switch in Fig. 7.43 has been in position A for a long time. At $t = 0$, the switch moves to B. Determine $v(t)$ for $t > 0$ and calculate its value at $t = 1$ s and 4 s.</p> 	8	
4	IV	 <p>find $I(t)$ for $t > 0$</p>	8	
5	IV	 <p>find $i(t)$ for $t > 0$ (Series RLC)</p>	8	
6	IV	<p>Example 8.5 In the parallel circuit of Fig. 8.13, find $v(t)$ for $t > 0$, assuming $v(0) = 5$ V, $i(0) = 0$, $L = 1$ H, and $C = 10$ mF. Consider these cases: $R = 1.923 \Omega$, $R = 5 \Omega$, and $R = 6.25 \Omega$.</p>	8	
7	IV	<p>In the circuit of Fig. 14.24, $R = 2 \Omega$, $L = 1$ mH, and $C = 0.4 \mu\text{F}$. (a) Find the resonant frequency and the half-power frequencies. (b) Calculate the quality factor and bandwidth. (c) Determine the amplitude of the current at ω_0, ω_1, and ω_2.</p>  <p>Solution:</p>	8	
8	IV	<p>Example 14.8 In the parallel RLC circuit of Fig. 14.27, let $R = 8$ kΩ, $L = 0.2$ mH, and $C = 8 \mu\text{F}$. (a) Calculate ω_0, Q, and B. (b) Find ω_1 and ω_2. (c) Determine the power dissipated at ω_0, ω_1, and ω_2.</p>  <p>Solution:</p>	8	
9	IV	<p>A series-connected circuit has $R = 4 \Omega$ and $L = 25$ mH. (a) Calculate the value of C that will produce a quality factor of 50. (b) Find ω_1, ω_2, and B. (c) Determine the average power dissipated at $\omega = \omega_0$, ω_1, ω_2. Take $V_m = 100$ V.</p>	8	
		<p>EXAMPLE 3.7 For the circuit shown in Fig. 1, determine the frequency at which the circuit resonates. Also find the quality factor, voltage across inductance and voltage across capacitance at resonance.</p>  <p>SOLUTION</p>	8	
Unit V				
1	V	 <p>Find i_1 and i_2</p>	8	

2	V	 <p>find i_1 and i_2</p>	8	
3	V	 <p>find i_1 and i_2</p>	8	
4	V	<p>In the circuit of Fig. 13.24, calculate the input impedance and current I_1. Take $Z_1 = 60 - j100 \Omega$, $Z_2 = 30 + j40 \Omega$, and $Z_L = 80 + j60 \Omega$.</p> 	8	
5	V	<p>Solve for I_1, I_2, and V_o in Fig. 13.27 (the same circuit as for Practice Prob. 13.1) using the T-equivalent circuit for the linear transformer.</p> 	8	
6	V	<p>An ideal transformer is rated at 2400/120 V, 9.6 kVA, and has 50 turns on the secondary side. Calculate (a) the turns ratio, (b) the number of turns on the primary side, and (c) the current ratings for the primary and secondary windings.</p>	8	
7	V	<p>For the ideal transformer circuit of Fig. 13.37, find: (a) the source current I_1, (b) the output voltage V_o, and (c) the complex power supplied by the source.</p> 	8	
8	V	<p>In the ideal transformer circuit of Fig. 13.38, find V_o and the complex power supplied by the source.</p>  <p>Figure 13.38</p>	8	
9	V	<p>Calculate the power supplied to the 10-Ω resistor in the ideal transformer circuit of Fig. 13.39.</p> 	8	
10	V	<p>Cut Set and Tie set Problem</p>	8	

Prepared By

Verified By

Approved By